

King Fahd University of Petroleum & Minerals
Department of Electrical Engineering

Quiz # 5

EE360 Power Electronics

November 2007

Name: _____ ID: _____ Grade: _____

A 220-V DC shunt motor has armature and field winding resistances of 0.15Ω and 110Ω , respectively. The motor draws a line current of 5 A while running at 1200 rpm on no load. When driving a load, the input to the motor is 12 kW. Calculate:

- (a) The speed of the motor.
- (b) The developed torque.
- (c) The efficiency of the motor at this load.

(Hint: $P_{\text{rotational}} = \text{power developed at no load}$)