

Problem 3-1

$$V_m = 170 \text{ V}, R = 10 \ \Omega, f = 60 \text{ Hz}$$

$$\text{From Eq. (3-21), } V_d = 0.6366 V_m = 0.6366 \times 170 = 113.32 \text{ V}$$

Problem 3-5

$$R = 100 \ \Omega, V_s = 280 \text{ V}, f = 60 \text{ Hz}$$

$$V_m = 280 \times \sqrt{2}/\sqrt{3} = 228.6 \text{ V}$$

$$\text{From Eq. (3-40), } V_{dc} = 1.6542 \times 228.6 = 378.15 \text{ V}$$

Problem 3-7

$$V_{dc} = 400 \text{ V}, R = 10 \ \Omega$$

$$\text{From Eq. (3-21), } V_{dc} = 400 = 0.6366 V_m \quad \text{or } V_m = 628.34 \text{ V}$$

$$\text{The rms phase voltage is } V_s = V_m/\sqrt{2} = 628.34/\sqrt{2} = 444.3 \text{ V}$$

$$I_{dc} = V_{dc}/R = 400/10 = 40 \text{ A}$$

Diodes:

$$\text{Peak current, } I_p = 628.34/10 = 62.834 \text{ A}$$

$$\text{Average current, } I_d = I_{dc}/2 = 40/2 = 20 \text{ A}$$

$$\text{RMS current, } I_R = 62.834/2 = 31.417 \text{ A}$$

Transformer:

$$\text{RMS voltage, } V_s = V_m/\sqrt{2} = 444.3 \text{ V}$$

$$\text{RMS current, } I_s = I_m/\sqrt{2} = 44.43 \text{ A}$$

$$\text{Volt-amp, } VI = 444.3 \times 44.43 = 19.74 \text{ kVA}$$

$$P_{dc} = (0.6366 V_m)^2/R \text{ and } P_{ac} = V_s I_s = V_m^2 / 2R$$

TUF = $P_{dc}/P_{ac} = 0.6366^2 \times 2 = 0.8105$ and the de-rating factor of the transformer is $1/\text{TUF} = 1.2338$.

Problem 3-9

$V_m = 170 \text{ V}$, $f = 60 \text{ Hz}$, $R = 15 \ \Omega$ and $\omega = 2\pi f = 377 \text{ rad/s}$

From Eq. (3-22), the output voltage is

$$v_L(t) = \frac{2V_m}{\pi} - \frac{4V_m}{3\pi} \cos(2\omega t) - \frac{4V_m}{15\pi} \cos(4\omega t) - \frac{4V_m}{35\pi} \cos(6\omega t) - \dots$$

The load impedance, $Z = R + j(n\omega L) = \sqrt{R^2 + (n\omega L)^2} \angle \theta_n$

and $\theta_n = \tan^{-1}(n\omega L / R)$

and the load current is given by

$$i_L(t) = I_{dc} - \frac{4V_m}{\pi \sqrt{R^2 + (n\omega L)^2}} \left[\frac{1}{3} \cos(2\omega t - \theta_2) - \frac{1}{15} \cos(4\omega t - \theta_4) - \frac{1}{35} \cos(6\omega t - \theta_6) - \dots \right]$$

where $I_{dc} = \frac{V_{dc}}{R} = \frac{2V_m}{\pi R}$

The rms value of the ripple current is

$$I_{ac}^2 = \frac{(4V_m)^2}{2\pi^2 [R^2 + (2\omega L)^2]} \left(\frac{1}{3}\right)^2 + \frac{(4V_m)^2}{2\pi^2 [R^2 + (4\omega L)^2]} \left(\frac{1}{15}\right)^2 + \frac{(4V_m)^2}{2\pi^2 [R^2 + (6\omega L)^2]} \left(\frac{1}{35}\right)^2 + \dots$$

Considering only the lowest order harmonic ($n = 2$) and neglecting others,

$$I_{ac} = \frac{4V_m}{\sqrt{2}\pi \sqrt{R^2 + (2\omega L)^2}} \left(\frac{1}{3}\right)$$

Using the value of I_{dc} and after simplification, the ripple factor is

$$RF = \frac{I_{ac}}{I_{dc}} = \frac{0.481}{\sqrt{1 + (2\omega L / R)^2}} = 0.04$$

$$0.481^2 = 0.04^2 [1 + (2 \times 377 L / 15)^2] \text{ or } L = 238.4 \text{ mH}$$

Problem 3-11

$$E = 20 \text{ V}, I_{dc} = 10 \text{ A}, V_p = 120 \text{ V}, V_s = V_p/n = 120/2 = 60 \text{ V}$$

$$V_m = \sqrt{2} V_s = \sqrt{2} \times 60 = 84.85 \text{ V}$$

$$(i) \text{ From Eq. (3-17), } \alpha = \sin^{-1} (20/84.85) = 15.15^\circ \text{ or } 0.264 \text{ rad}$$

$$\beta = 180 - 15.15 = 164.85^\circ$$

The conduction angle is $\delta = \beta - \alpha = 164.85 - 15.15 = 149.7^\circ$

(ii) Equation (3-18) gives the resistance R as

$$R = \frac{1}{2\pi I_{dc}} [2V_m \cos \alpha + 2\alpha E - \pi E]$$

$$R = \frac{1}{2\pi \times 10} [2 \times 84.85 \times \cos 15.15^\circ + 2 \times 20 \times 0.264 - \pi \times 20] = 1.793 \Omega$$

(iii) Equation (3-19) gives the rms battery current I_{rms} as

$$I_{rms}^2 = \frac{1}{2\pi R^2} \left[\left(\frac{V_m^2}{2} + E^2 \right) (\pi - 2\alpha) + \frac{V_m^2}{2} \sin 2\alpha - 4V_m E \cos \alpha \right] = 272.6$$

$$\text{or } I_{rms} = \sqrt{272.6} = 16.51 \text{ A}$$

The power rating of R is $P_R = 16.51^2 \times 1.793 = 488.8 \text{ W}$

(iv) The power delivered P_{dc} to the battery is

$$P_{dc} = E I_{dc} = 20 \times 10 = 200 \text{ W}$$

$$h P_{dc} = 100 \quad \text{or} \quad h = 200/P_{dc} = 200/200 = 1 \text{ hr}$$

(v) The rectifier efficiency η is

$$\eta = \frac{P_{dc}}{P_{dc} + P_R} = \frac{200}{200 + 488.8} = 29\%$$

(vi) The peak inverse voltage PIV of the diode is

$$\text{PIV} = V_m + E = 84.85 + 20 = 104.85 \text{ V}$$

Problem 3-15

RF = 5%, R = 200 Ω, and f = 60 Hz

(a) For a half-wave rectifier, the frequency of output ripple voltage is the same as the supply frequency. Thus, the constant 4 in Eq. (3-62) should be changed to 2.

Solving for C_e in Eq. (3-62),


$$C_e = \frac{1}{2 \times 60 \times 200} \left[1 + \frac{1}{\sqrt{2} \times 0.05} \right] = 630.92 \mu\text{F}$$

(b) From Eq. (3-61), the average load voltage V_{dc} is

$$V_{dc} = 169.7 - \frac{169.7}{2 \times 60 \times 200 \times 415.46 \times 10^{-6}} = 169.7 - 22.42 = 147.28 \text{ V}$$

Problem 3-21

(a)

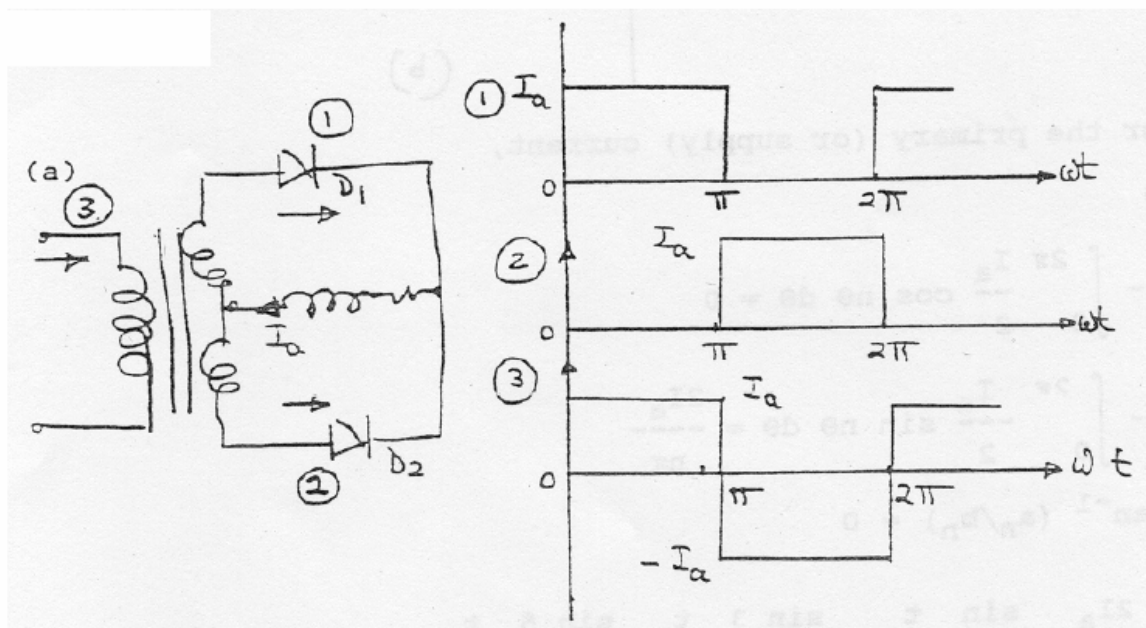

(b) For the primary (or supply) current: From Eq. (3-23), the primary current is

$$i_s(t) = \frac{4I_a}{\pi} \left[\frac{\sin \omega t}{1} + \frac{\sin 3\omega t}{3} + \frac{\sin 5\omega t}{5} + \dots \right]$$

$$I_1 = 4I_a/(\pi\sqrt{2})$$

The rms current is $I_s = I_a$. $PF = I_1/I_s = 2\sqrt{2}/\pi = 0.9$ and $HF = \sqrt{(I_s/I_1)^2 - 1} = 0.4834$.

(c) For the rectifier input (or secondary) current:

$$a_0/2 = I_a/2$$

$$a_n = \frac{1}{\pi} \int_0^\pi I_a \cos(n\theta) d\theta = 0$$

$$b_n = \frac{1}{\pi} \int_0^\pi I_a \sin(n\theta) d\theta = \frac{I_a}{n\pi} (1 - \cos n\theta)$$

$$\varphi_n = \tan^{-1} (a_n/b_n) = 0$$

$$C_n = \sqrt{(a_n^2 + b_n^2)} \text{ and } I_1 = C_1/\sqrt{2} = \sqrt{2}I_a/\pi$$

$$\text{and } I_s = I_a/\sqrt{2}$$

$$PF = I_1/I_s = 2/\pi = 0.6366 \text{ and } HF = \sqrt{(I_s/I_1)^2 - 1} = 1.211$$