

### Problem 5-2

$V_s = 220 \text{ V}$ ,  $R = 10 \ \Omega$ ,  $L = 15.5 \text{ mH}$ ,  $E = 20 \text{ V}$ ,  $k = 0.5$  and  $f = 5000 \text{ Hz}$

From Eq. (5-15),  $I_2 = 0.9375 I_1 + 1.2496$

From Eq. (5-16),  $I_1 = 0.9375 I_2 - 1.2496$

(a) Solving these two equations,  $I_1 = 8.6453 \text{ A}$

(b)  $I_2 = 9.3547 \text{ A}$

(c)  $\Delta I = I_2 - I_1 = 9.35475 - 8.6453 = 0.7094 \text{ A}$

From Eq. (5-21),  $\Delta I_{\max} = 0.7094 \text{ A}$

and Eq. (5-22) gives the approximately value,  $\Delta I_{\max} = 0.7097 \text{ A}$

(d) The average load current is approximately,

$$I_a = (I_2 + I_1)/2 = (9.35475 + 8.6453)/2 = 9 \text{ A}$$

(e) From Eq. (5-24),

$$I_o = \left[ I_1^2 + \frac{(I_2 - I_1)^2}{3} + I_1(I_2 - I_1) \right]^{-1/2} = 9.002 \text{ A}$$

(f)  $I_s = k I_a = 0.8 \times 9 = 7.2 \text{ A}$

and the input resistance is  $R_i = V_s/I_s = 220/7.2 = 30.56 \ \Omega$

(g) From Eq. (5-25),  $I_R = \sqrt{k} I_o = \sqrt{0.8} \times 22.1 = 15.63 \text{ A}$

### Problem 5-3

$V_s = 220 \text{ V}$ ,  $R = 0.2 \ \Omega$ ,  $E = 10 \text{ V}$ ,  $f = 200 \text{ Hz}$ ,  $T = 1/f = 0.005 \text{ s}$

$$\Delta i = 200 \times 0.5 = 10 \text{ A.}$$

$$V_a = k V_s = R I_a$$

The voltage across the inductor is given by

$$L \frac{di}{dt} = V_s - R I_a = V_s - k V_s = (1-k) V_s$$

For a linear rise of current,  $dt = t_1 = kT$  and  $di = \Delta i$

$$\Delta i = \frac{(1-k) V_s}{L} k T$$

For worst case ripple condition:  $\frac{d(\Delta i)}{dk} = 0$

and this gives,  $k = 0.5$

$$\Delta i L = 10 \times L = 220 (1 - 0.5) 0.5 \times 0.005 \text{ or } L = 27.5 \text{ mH}$$

#### Problem 5-4

$$V_s = 110 \text{ V}, E = 220 \text{ V}, P_o = 30 \text{ kW} = 30000 \text{ W}$$

(c) Since the input power must be the same as the output power,

$$V_s I_s = P_o \text{ or } 110 \times I_s = 30000 \text{ or } I_s = \text{A}$$

(a) The battery current,  $I_b = P_o/E = 30000/220 = 136.36 \text{ A}$

$$I_b = (1 - k) I_s \text{ or } k = 136.36/272.73 - 1 = 0.5$$

$$(b) R_{ch} = (1 - k) E/I_s = (1 - 0.5) \times 220/272.73 = 0.4033 \ \Omega$$

#### Problem 5-6

$$V_s = 600 \text{ V}, R = 0.25 \ \Omega, L = 20 \text{ mH}, E = 150 \text{ V}, k = 0.1 \text{ to } 0.9 \text{ and } f = 250$$

Hz

For  $k=0.1$ , the load current is discontinuous

$$\text{From Eq. (5-15), } I_2 = 8.977$$

$$\text{From Eq. (5-16), } I_1 = 0, \Delta I = 8.977 \text{ A and } I_a = 4.4885 \text{ A}$$

For  $k=0.2$ , the load current is discontinuous

$$I_2 = 17.9103 \text{ A}, I_1 = 0 \text{ A}, \Delta I = 17.9103 \text{ A and } I_a = 8.955 \text{ A}$$

For  $k = 0.3$

$$I_2 = 0.9851 I_1 + 26.7985, I_1 = 0.9656 I_2 - 20.6367$$

$$I_2 = 132.64 \text{ A}, I_1 = 107.44 \text{ A}, \Delta I = 25.2 \text{ A and } I_a = 120.04 \text{ A}$$

For  $k = 0.4$

$$I_2 = 0.9802 I_1 + 35.64, I_1 = 0.97044 I_2 - 17.733$$

$$I_2 = 374.42 \text{ A}, I_1 = 345.62 \text{ A}, \Delta I = 28.8 \text{ A and } I_a = 360.02 \text{ A}$$

For  $k = 0.5$

$$I_2 = 0.9753 I_1 + 44.44, I_1 = 0.97045 I_2 - 14.814$$

$$I_2 = 615 \text{ A}, I_1 = 585 \text{ A}, \Delta I = 30 \text{ A and } I_a = 600 \text{ A}$$

For  $k = 0.6$

$$I_2 = 0.97044 I_1 + 53.2, I_1 = 0.9802 I_2 - 11.881$$

$$I_2 = 854.38 \text{ A}, I_1 = 825.58 \text{ A}, \Delta I = 28.8 \text{ A and } I_a = 840 \text{ A}$$

For  $k = 0.7$

$$I_2 = 0.9656 I_1 + 61.91, I_1 = 0.9851 I_2 - 8.933$$

$$I_2 = 1092.6 \text{ A}, I_1 = 1067.4 \text{ A}, \Delta I = 25.2 \text{ A and } I_a = 1080 \text{ A}$$

For  $k = 0.8$

$$I_2 = 0.9608 I_1 + 70.58, I_1 = 0.99 I_2 - 5.97$$

$$I_2 = 1329.6 \text{ A}, I_1 = 1310.4 \text{ A}, \Delta I = 19.2 \text{ A and } I_a = 1320 \text{ A}$$

For  $k = 0.9$

$$I_2 = 0.956 I_1 + 79.2, I_1 = 0.995 I_2 - 2.99$$

$$I_2 = 1565.4 \text{ A}, I_1 = 1554.6 \text{ A}, \Delta I = 10.8 \text{ A and } I_a = 1560 \text{ A}$$