

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

DEPARTMENT OF ELECTRICAL ENGINEERING

EE460-01 POWER ELECTRONICS

EXAM : II
DATE : January 2008
PLACE : BLDG. 59-1010
TIME : 5:30-7:00 PM

Student Name: _____

Student ID : _____




Instructors : Dr. Mahmoud Kassas

Problem 1	
Problem 2	
Problem 3	
Total	

Problem 1 (10 points)

Three-phase bridge controlled rectifier has a highly inductive load. $V_s = 220V$ is the rms phase voltage, $f = 50Hz$, If $V_{0(rms)} = 158.5V$, Determine:


- (a) The delay angle α . (2 points)
- (b) The average output voltage. (2 points)
- (c) Draw the secondary transformer input current i_b and find the rms current. (4 points)
- (d) Draw the voltage across T_5 and the current through T_6 . (2 points)

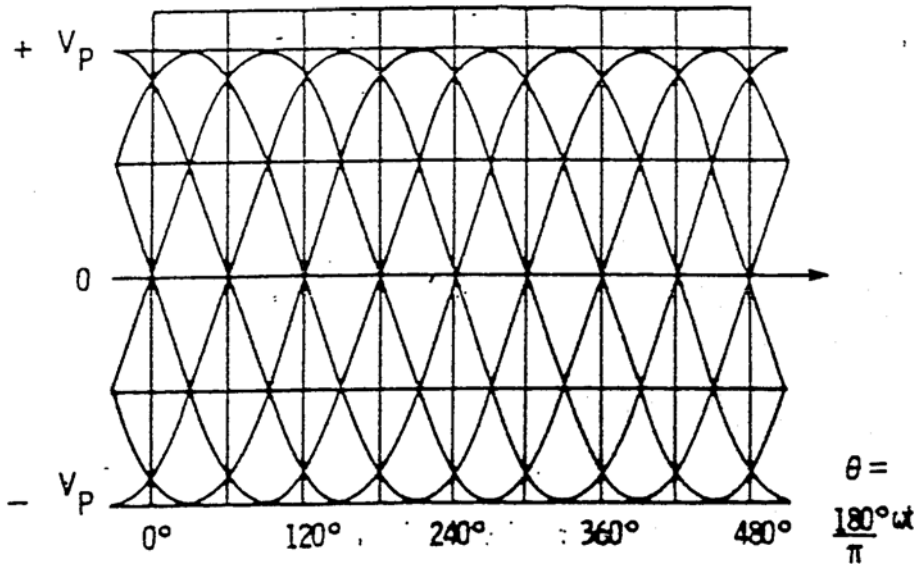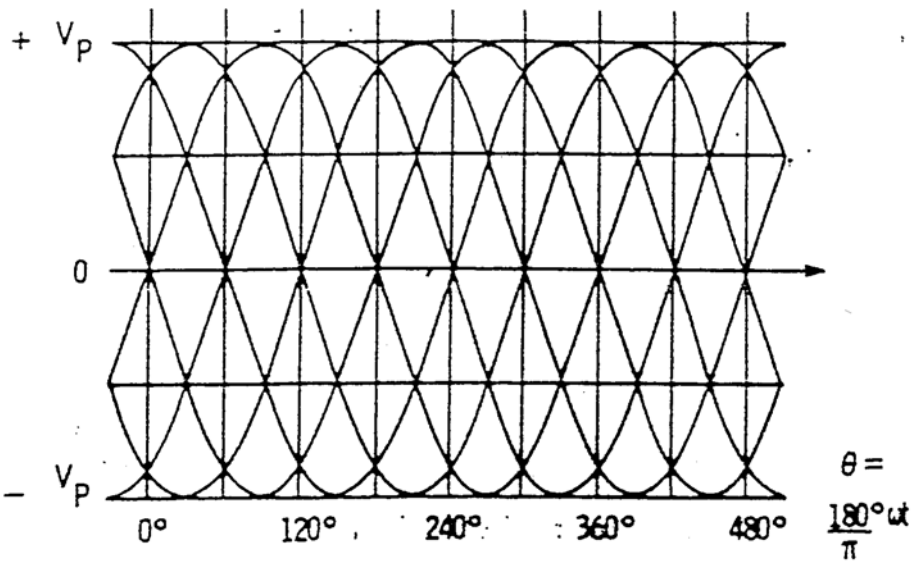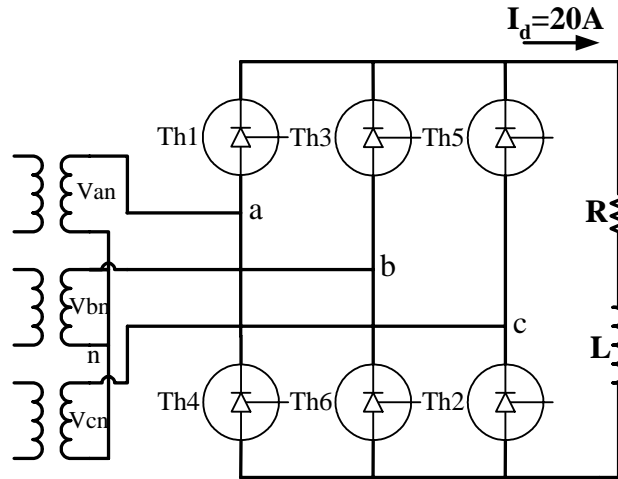

Problem 2: (10 Points)

The single-phase full-wave ac-controller in Fig. 2 supplies an RL-load. The input rms is voltage 220-V, 50 Hz. The load such that $L = 31.83 \text{ mH}$ & $R = 10\text{-}\Omega$. If $I_R = 8.25\text{-A}$, calculate:

- (a) The conduction angle γ . (3 points)
- (b) Calculate the rms output voltage. (1 point)
- (c) The input power factor. (2 points)
- (d) Draw the voltage across the thyristor T2 and calculate the peak inverse voltage. (2 points)
- (e) Draw the input current and calculate the average thyristor current. (2 points)

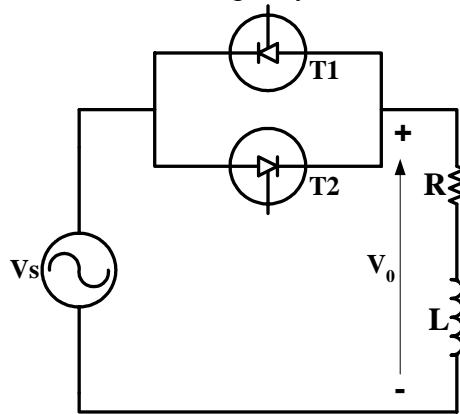

Problem 3: (10 Points)

The dc chopper in Fig. 1 has inductive load of $R = 10\Omega$ and $L = 20\text{mH}$. The input voltage value is $V_s = 220\text{V}$, $f = 5\text{ kHz}$, $E=100\text{V}$, and $k = 0.50$. Calculate:

- (a) the average load current I_a . (3 points)
- (b) the rms load current I_0 . (3 points)
- (c) the rms value of the chopper current I_R . (2 points)
- (d) the effective input resistance R_i . (1 points)
- (e) draw the voltage across the diode D_m . (1 points)

