

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
DEPARTMENT OF ELECTRICAL ENGINEERING

EE 200 EXAMINATION

DIGITAL LOGIC CIRCUIT DESIGN

EXAMINATION TYPE: Major Examination II

DATE: December 17, 2005

Student's name:	
I. D. #:	
Section:	03

Q # 1	/ 20
Q # 2	/ 30
Q # 3	/ 25
Q # 4	/ 25
Total	/ 100

Instructor: Dr. Mahmoud M. Dawoud

Q.1)

Design a combinational circuit that implements the following Boolean functions using a decoder and OR gates.

$$F_1(w, x, y, z) = w'xy + wy'z' + wx'$$

$$F_2(w, x, y, z) = \Pi(0,1,2,3,5,6,7,8,9,13)$$

Q.2)

- Design a logic circuit that will add one to the decimal equivalent of a 3 bit input binary number(x,y,z) if the number is even. If the number is odd, three will be added. Determine the required number of outputs and call them (A, B, ...etc.). Obtain a minimal expression for each output and draw the logic circuit using only NAND gates. Use Karnaugh maps for simplification.
- Design the circuit in (a) using a ROM. Determine the size of the ROM and its truth table. Do not include any output that is equal to an input.

Q.3)

Construct the PLA program table to implement the following functions:

$$f_1(A, B, C, D) = \sum m(0,1,4,5,8,9,13)$$

$$f_2(A, B, C, D) = \sum m(2,3,6,7,8,10,11,12)$$

Realize the functions such that the number of product terms is minimised.

Q.4)

Analyse the clocked sequential circuit below, by finding:

- The flip-flop input functions
- The output functions
- The state table
- The state diagram

