

King Fahd University of Petroleum & Minerals
Department of Electrical Engineering

EE200-03 (062)

Homework # 4

1. Simplify the following Boolean function, which is given in a product of maxterms form, together with the don't care conditions, first in SOP, then in POS forms. Implement the function using two level NAND-NAND.

$$F(w, x, y, z) = \Pi(0, 2, 3, 4, 6, 7, 11, 15)$$

$$\text{with don't care conditions } d(w, x, y, z) = \Sigma(5, 12, 13, 14)$$

2. Design a combinational circuit with three inputs (x, y, z) and one output (F). The output is 1 when the binary value of the inputs is greater than 3. The output is 0 otherwise.
3. Design a combinational circuit that converts a 4-bit Gray code (Table 1-6 of the textbook) to a 4-bit binary number. Implement the circuit with exclusive-OR gates. (Use the letters w, x, y, z to represent the inputs and A, B, C, D to represent the outputs).