

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

King Fahd University of Petroleum and Minerals  
Department of Electrical Engineering

Semester I 2005/2006

EE303 Electronics II

Quiz (1)

ATTEMPT ALL QUESTIONS  
TIME ALLOWED 10 Minutes

Find the poles of the circuit shown in Fig. 1.

