

بسم الله الرحمن الرحيم

King Fahd University of Petroleum and Minerals  
Department of Electrical Engineering

Semester II 2005/2006


EE445 Industrial Electronics

Major Test (3)

ATTEMPT ALL QUESTIONS  
TIME ALLOWED ONE HOUR

You have a load of  $10 \Omega$  (say a heater of a boiler). It is required to provide this load with the waveform shown in Fig. 1. Of course the shape of this waveform should be controllable so that you can control the power consumed, and hence the temperature, of the load.

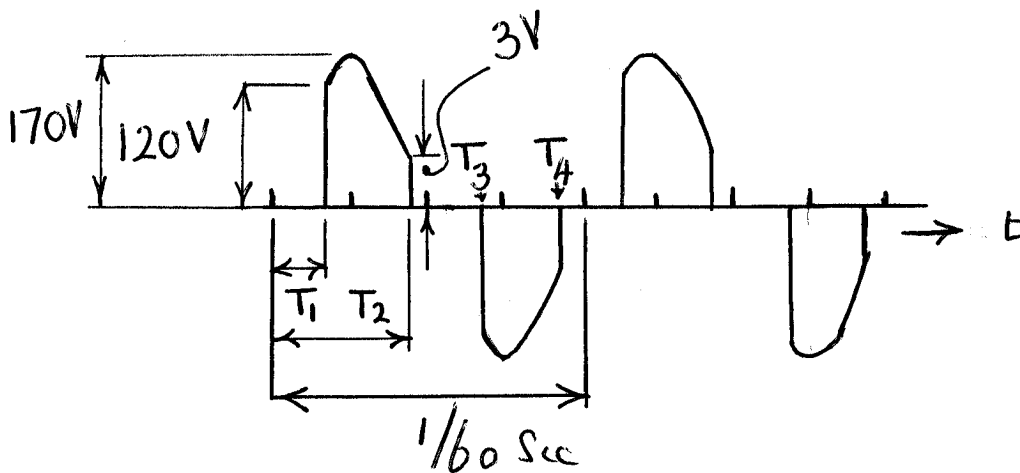You are requested to design a circuit that can provide this waveform. **Draw a complete circuit for your proposal and write down the specifications of each component.**



$$T_1 = 1/250 \text{ Sec}$$

$$T_2 = 1/125 \text{ Sec}$$

$$T_3 = T_1 + 1/120 \text{ Sec}$$

$$T_4 = T_2 + 1/120 \text{ Sec}$$

$$\omega = 2\pi f, \quad f = 60 \text{ Hz}, \quad V_{\text{rms of mains}}$$

$$\text{Supply} = 110V$$