

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

King Fahd University of Petroleum and Minerals
 Department of Electrical Engineering

Semester I 2006/2007

EE303 Electronics II

Quiz (1)

ATTEMPT ALL QUESTIONS
 TIME ALLOWED 10 MINUTES

Find the poles of the circuit shown in Figure 1.

