

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

King Fahd University of Petroleum and Minerals
Department of Electrical Engineering

Semester I 2006/2007 EE303 Electronics II

Quiz (3)

ATTEMP ALL QUESTIONS
TIME ALLOWED 10 MINUTES

Consider the circuit shown in Fig. This is a filter with input current and output voltage. Obtain the transfer function of this filter. Identify this filter.

