

بسم الله الرحمن الرحيم

King Fahd University of Petroleum and Minerals
Department of Electrical Engineering

Semester II 2006/2007

Electronics II EE303

Quiz (1)

ATTEMPT ALL QUESTIONS
TIME ALLOWED 10 MINUTES

Q1. Find the poles of the circuit shown below.

