

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

King Fahd University of Petroleum and Minerals
Department of Electrical Engineering

Semester II 2006/2007

Electronics II EE303

Quiz (4)

ATTEMPT ALL QUESTIONS
TIME ALLOWED 10 MINUTES

The operational amplifier in the circuit of Fig. 1 has the gain-frequency characteristic shown in Fig. 2. Calculate the approximate bandwidth of the circuit shown in Fig. 1.

