

بسم الله الرحمن الرحيم

King Fahd University of Petroleum and Minerals  
 Department of Electrical Engineering

Semester I 2007/2008

Electronics II EE303

Quiz (3)

ATTEMPT ALL QUESTIONS  
 TIME ALLOWED 10 MINUTES

Identify the global feedback in the circuit shown.

