

بسم الله الرحمن الرحيم

King Fahd University of Petroleum and Minerals
Department of Electrical Engineering

Semester I 2007/2008

Electronics II EE303

Quiz (4)

ATTEMPT ALL QUESTIONS
TIME ALLOWED 10 MINUTES

Q1. Identify the feedback configuration in the circuit shown.

Q2. Can we obtain a sinusoidal oscillator from this circuit? If your answer is YES, then show how?

