

King Fahd University of Petroleum & Minerals

Electrical Engineering Department

EE205: Electric Circuits II

Dr. Ali Muqaibel

HW 4: Resonant Circuits


Problem 1:

For the circuit shown in the figure

$$R=10, L=2 \text{ H, and } C=\frac{1}{50} \text{ F}$$

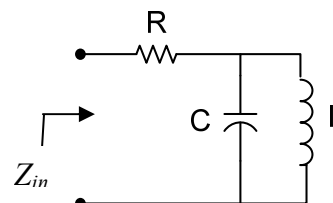- 1) Find the input impedance $Z_{in}(j\omega)$ (3 points)
- 2) Find the input admittance $Y_{in}(j\omega)$ (4 points)
- 3) Find the resonance frequency. (3 points)
- 4) Find the quality factor of the circuit. (2 bonus)

(Hint : assume that you have a voltage test source and then use source transformation)



Simplify $Z_{in}(j\omega)$ & $Y_{in}(j\omega)$ as real +j imaginary

Problem 2:

A 10Ω resistor and a 2 H inductor are connected in parallel and $\omega= 50 \text{ rad/s}$.


- (a) What is the Q of this parallel connection?
- (b) What series RL connection has the same impedance as the parallel connection at the given frequency?
- (c) What is the Q of this series connection?

- (d) A circuit has the following transfer function, $H(j\omega) = \frac{V_{out}}{V_{input}} = \frac{1}{2 + j\omega}$, find the cutoff frequency for this circuit.

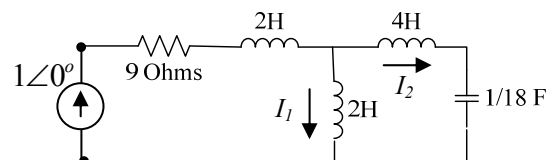Problem 3:

For the circuit shown in the figure, the resonance frequency is $6/\sqrt{10} \text{ rad/s}$, to find the quality factor we have applied a test current source of value $1\angle 0^\circ \text{ A}$, and we have found that the current through the 4H inductor is $I_2= 2\angle 0^\circ \text{ A}$, the voltage across the capacitor can be found to be $6\sqrt{10}\angle -90^\circ \text{ V}$. Find the quality factor

Hint: continue to find the current in the other inductors.



$$\cos^2 \theta = \frac{1}{2}(1 + \cos 2\theta)$$