


Problem 1:

For the op-amp circuit given in the

figure, find the transfer function

$H(s) = V_2 / V_1$ and draw the pole-zero

plot for the case that $C = \frac{1}{5} F$

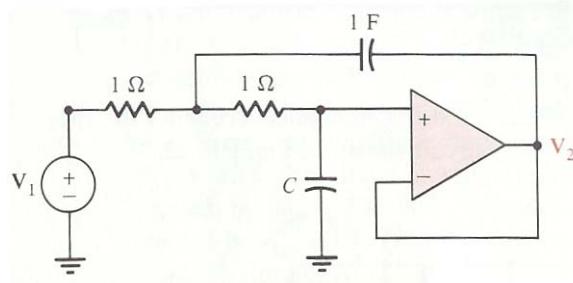

Problem 2:

For the shown circuit,

- Find the transfer function, $H(s) = V_2 / V_1$.
- Draw the pole-zero plot of $H(s)$.
- If $v_1(t) = 10e^{-17.5t} \cos 7.5t$, Find $v_2(t)$.

