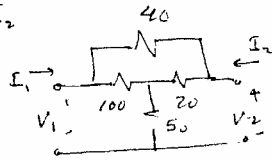


18-4


$$V_1 = b_{11}V_2 - b_{12}I_2$$

$$I_1 = b_{21}V_2 - b_{22}I_2$$



$$b_{11} = \frac{V_1}{V_2} \Big|_{I_2=0} \rightarrow \text{port 2 open circuit}$$

So

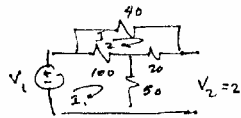

$$V_1 = 150I_1 - 100I_2 \quad \text{--- (1)}$$

$$0 = 150I_2 - 100I_1 \quad \text{--- (2)}$$

$$\downarrow$$

$$\therefore I_1 = 1.5I_2$$

Subst. in (1):

$$V_1 = (150 \times 1.5 - 100)I_2 = 140I_2$$

$$\therefore I_2 = \frac{V_1}{140} \quad I_1 = \frac{1.5}{140}V_1$$

$$\therefore V_2 = 20I_2 + 50I_1$$

$$V_2 = \left(\frac{20}{140} + \frac{50 \times 1.5}{140} \right) V_1 \quad I_1 = \frac{1.5}{140}V_1$$

$$V_2 = \frac{100}{140}V_1 \quad \therefore \frac{V_1}{V_2} \Big|_{I_2=0} = 1.4$$

$$\therefore b_{11} = 1.4$$


Also $b_{21} = \frac{I_1}{V_2} \Big|_{I_2=0}$ $I_{in} \text{ here} = I_1$

$$\therefore b_{21} = \frac{1.5}{140} \frac{V_1}{V_2} = \frac{1.5}{140} \times 1.4 = 1.5 \times 10^{-2} = 0.015$$

f. (1)

Next:

$$b_{12} = -\frac{V_1}{I_2} \Big|_{V_2=0} \rightarrow \text{port 2 short circuit}$$

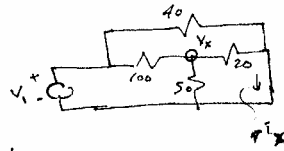

KCL at V_x :

$$\frac{V_x - V_1}{100} + \frac{V_x}{50} + \frac{V_x}{20} = 0$$

$$V_x \left(\frac{1}{100} + \frac{1}{50} + \frac{1}{20} \right) = \frac{V_1}{100}$$

$$V_x \frac{1+2+5}{100} = \frac{V_1}{100} \rightarrow 8V_x = V_1$$

$$\therefore V_x = (V_1/8)$$

$$\therefore I_x = \frac{V_x}{20} + \frac{V_1}{40} = V_1 \left(\frac{1}{160} + \frac{1}{40} \right)$$

$$I_x = V_1 \frac{5}{160} \quad \text{but } I_x = -I_2$$

$$\therefore b_{12} = +\frac{160}{5} = +32$$

Finally, since the circuit is reciprocal


$$\therefore b_{11}b_{22} - b_{12}b_{21} = 1$$

$$\therefore 1.4b_{22} - 16 \times 10^{-3} \times 32 = 1$$

$$1.4b_{22} = 1.512 \quad \therefore b_{22} = 1.08$$

Also, b_{22} may be obtained from the relation:

$$b_{22} = -\frac{I_1}{I_2} \Big|_{V_2=0} \rightarrow \text{port 2 short circuit}$$

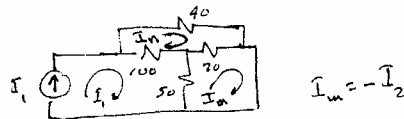

$$\text{KVL } (I_m): 70I_m - 20I_n = 50I_1 \quad \text{--- (1)}$$


$$160I_n - 20I_m = 100I_1 \quad \text{--- (2)}$$

Solve (1) & (2):

$$540I_m = 500I_1$$

$$\therefore \frac{I_1}{I_m} = -\frac{I_1}{I_2} = b_{22} = \frac{540}{500} = 1.08$$

18-10

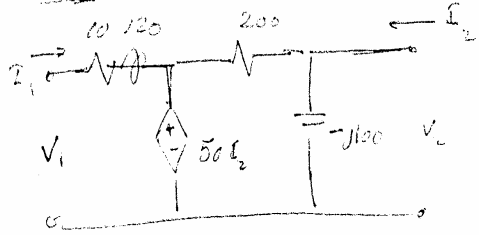


h-parameters:

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \rightarrow \text{port 2 is short circuit}$$

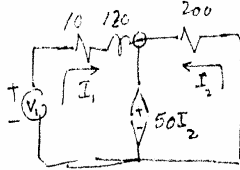

KVL (left Ryk h-loop)

$$\therefore 50I_2 = -200I_2$$

$$\therefore I_2 = 0$$


$$\therefore I_1 = \frac{V_1}{10+20} \quad \therefore \left. \frac{V_1}{I_1} \right|_{V_2=0} = (10+20)$$

Next,

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad \text{but } I_2 = 0 \text{ when } V_2 = 0 \text{ as shown earlier}$$

$$\therefore h_{21} = 0$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \rightarrow \text{port 1 open circuit}$$

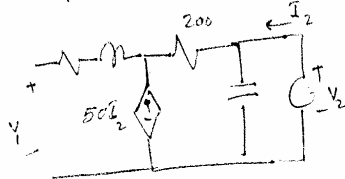

obviously $V_1 = 50I_2 \dots$ (1)

Using KCL:

$$\frac{V_2}{-j100} + \frac{V_2 - 50I_2}{200} = I_2$$

$$\therefore V_2 \left(\frac{1}{200} - \frac{1}{j100} \right) = (1.25) I_2$$

$$\therefore I_2 = \frac{V_2}{1.25} \left(\frac{1}{200} - \frac{1}{j100} \right) \dots$$
 (2)

Subst. (2) into (1):

$$V_1 = V_2 \frac{50}{1.25} \left(\frac{1}{200} - \frac{1}{j100} \right)$$

$$\therefore \left. \frac{V_1}{V_2} \right|_{I_1=0} = 0.2 + j0.4 = h_{12}$$

Notice that the circuit is NOT reciprocal due to the dependent source

therefore $h_{12} \neq -h_{21}$

Finally, to obtain h_{22} :

$$\left. \frac{I_2}{V_2} \right|_{I_1=0} \rightarrow \text{port 1 open circuit}$$


same configuration as in the case of h_{12}

there $h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$ which is directly equation (2) above (see \leftarrow)

$$\begin{aligned} \therefore \left. \frac{I_2}{V_2} \right|_{I_1=0} &= h_{22} = \frac{1}{1.25} \left(\frac{1}{200} + j\frac{1}{100} \right) \\ &= (4 + j8) \times 10^{-3} \\ &= (0.004 + j0.008) \end{aligned}$$

P. 2

18-11, 18-12

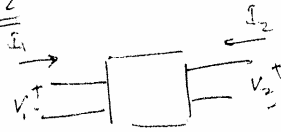

Port ② open $I_2 = 0$

$$V_1 = 20 \times 10^{-3}$$

$$V_2 = -5$$

$$I_1 = 0.25 \times 10^{-6}$$

Port ② SC $V_2 = 0$

$$I_1 = 200 \times 10^{-6}$$

$$I_2 = 50 \times 10^{-6}$$

$$V_1 = 10$$

Find the g parameters and the Y -parameters

$$I_1 = g_{11} V_1 + g_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = g_{21} V_1 + g_{22} I_2 \quad \text{--- (2)}$$

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0} \quad \therefore g_{11} = \frac{25 \times 10^{-8}}{20 \times 10^{-3}} = 1.25 \times 10^{-5}$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0} \quad \therefore g_{21} = -\frac{5}{20} \times 10^3 = -250$$

Next

as $V_2 = 0$ from (2): $\rightarrow g_{21} V_1 = -g_{22} I_2$

subst. in (1):

$$I_1 = g_{11} \frac{-g_{22} I_2 + g_{12} I_2}{g_{21}}$$

subst $g_{21} = -250$

$$V_1 = 10, \quad I_2 = 50 \times 10^{-6}$$

$$\therefore -250 \times 10 = -g_{22} \times 50 \times 10^{-6}$$

$$\therefore g_{22} = \frac{2500 \times 10^6}{50} = 50 \times 10^6$$

Also from (1):

$$I_1 = g_{11} V_1 + g_{12} I_2 \quad \text{independent from } V_2$$

$$\therefore 200 \times 10^{-6} = 1.25 \times 10^{-5} \times 10 + g_{12} \times 50 \times 10^{-6}$$

$$75 \times 10^{-6} = g_{12} \times 50 \times 10^{-6}$$

$$g_{12} = \frac{75}{50} = 1.50$$

Y -parameters:

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (3)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (4)}$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{200 \times 10^{-6}}{10} = 20 \times 10^{-6}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{50 \times 10^{-6}}{10} = 5 \times 10^{-6}$$

Next, regardless of I_2 , equate (3) holds true all the time: from the condition $I_2 = 0$, subst. in (4):

$$0.25 \times 10^{-6} = Y_{11} \times 20 \times 10^{-3} + Y_{12} \times (-5)$$

$$\therefore 0.25 \times 10^{-6} = 20 \times 10^{-6} \times 20 \times 10^{-3} + 5 Y_{12}$$

$$0.15 \times 10^{-6} = 5 Y_{12} \quad \Rightarrow Y_{12} = 0.03 \times 10^{-6}$$

Finally from (4), at $I_2 = 0$

$$Y_{21} V_1 = -Y_{22} V_2$$

$$5 \times 10^{-6} \times 20 \times 10^{-3} = +Y_{22} \times 5$$

$$Y_{22} = \frac{10^{-7}}{5} = 2 \times 10^{-8}$$

Check:

$$Y_{12} = \frac{g_{12}}{g_{22}} = \frac{1.5 \times 10^{-6}}{50} = 3 \times 10^{-8}$$

$$Y_{21} = -\frac{g_{21}}{g_{22}} = -\frac{(-250 \times 10^6)}{50} = 5 \times 10^{-6}$$

$$Y_{22} = \frac{1}{g_{22}} = \frac{1}{50 \times 10^6} = 2 \times 10^{-8}$$

$$Y_{11} = \frac{g_{11} g_{22} - g_{12} g_{21}}{g_{22}} = \frac{625 + 375}{50 \times 10^6} = 20 \times 10^{-6}$$