

KFUPM-EE DEPT.
EE205: Circuits II-082
HW # 1 : Solution

Problem 1:

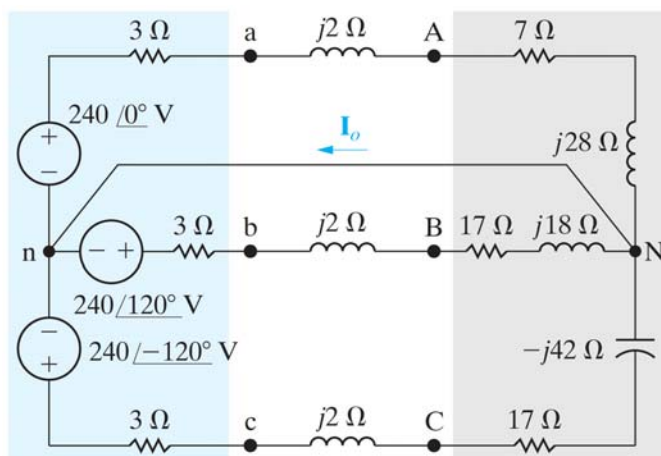


Figure: 11-22-01P11.05
Copyright © 2008 Pearson Prentice Hall, Inc.

- a) For the circuit in the above figure, is it a balanced or unbalanced three-phase system? Explain why.
b) Find I_o

[a] The circuit is unbalanced, because the impedance in each phase of the load is not the same.

$$[b] \mathbf{I}_{aA} = \frac{240/0^\circ}{10 + j30} = 2.4 - j7.2 \text{ A}$$

$$\mathbf{I}_{bB} = \frac{240/120^\circ}{20 + j20} = 2.2 + j8.2 \text{ A}$$

$$\mathbf{I}_{cC} = \frac{240/-120^\circ}{20 - j40} = 2.96 - j4.48 \text{ A}$$

$$\mathbf{I}_o = \mathbf{I}_{aA} + \mathbf{I}_{bB} + \mathbf{I}_{cC} = 7.55 - j3.48 = 8.32/\underline{-24.75^\circ} \text{ A}$$

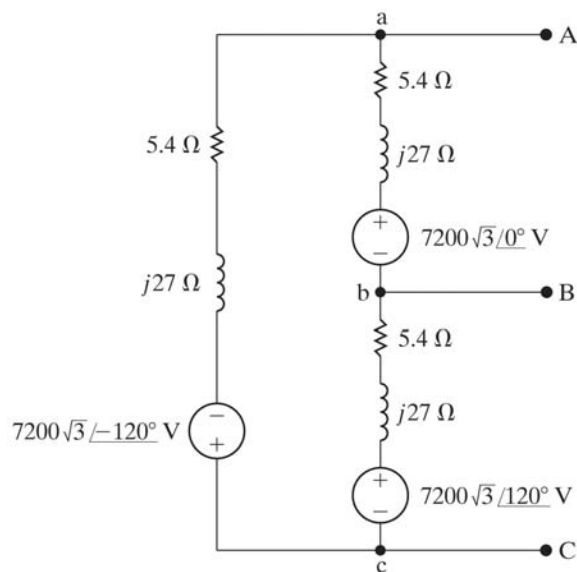
Problem 2:

Figure: 11-22-04P11.17

Copyright © 2008 Pearson Prentice Hall, Inc.

The above figure shows a balanced three-phase Δ -connected source.

- Find the Y-connected equivalent circuit.
- Show that the Y-connected equivalent circuit delivers the same open-circuit voltage as the original Δ -connected source.
- Apply an external short circuit to the terminals A, B, and C. Use the Δ -connected source to find the three line currents \mathbf{I}_{aA} , \mathbf{I}_{bB} , and \mathbf{I}_{cC} .
- Repeat (c) but use the Y-equivalent source to find the three line currents.

Answer P2:


[a] Since the phase sequence is acb (negative) we have:

$$\mathbf{V}_{an} = 7200/\underline{30^\circ} \text{ V}$$

$$\mathbf{V}_{bn} = 7200/\underline{150^\circ} \text{ V}$$

$$\mathbf{V}_{cn} = 7200/\underline{-90^\circ} \text{ V}$$

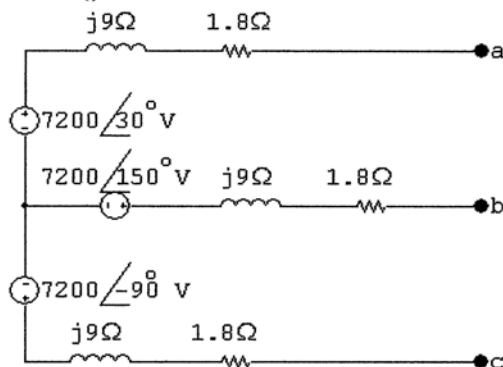
$$Z_Y = \frac{1}{3}Z_\Delta = 1.8 + j9.0 \Omega/\phi$$



[b] $\mathbf{V}_{ab} = 7200/\underline{30^\circ} - 7200/\underline{150^\circ} = 7200\sqrt{3}/\underline{0^\circ} \text{ V}$

Since the phase sequence is negative, it follows that
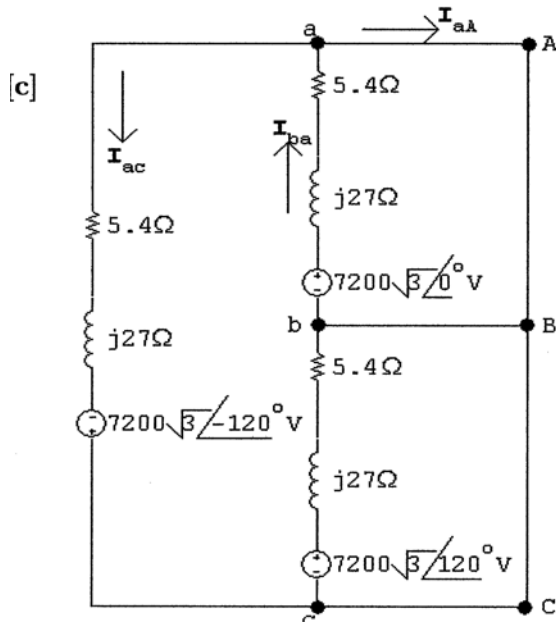
$$\mathbf{V}_{bc} = 7200\sqrt{3}/\underline{120^\circ} \text{ V}$$



$$\mathbf{I}_{ba} = \frac{7200\sqrt{3}}{5.4 + j27} = 452.91/\underline{-78.69^\circ} \text{ A}$$

$$\mathbf{I}_{ac} = \frac{7200\sqrt{3}/-120^\circ}{5.4 + j27} = 452.91/\underline{-198.69^\circ} \text{ A}$$


$$\mathbf{I}_{aA} = \mathbf{I}_{ba} - \mathbf{I}_{ac} = 784.46/\underline{-48.69^\circ} \text{ A}$$

Since we have a balanced three-phase circuit and a negative phase sequence we have:

$$\mathbf{I}_{bB} = 784.46/71.31^\circ \text{ A}$$

$$\mathbf{I}_{cC} = 784.46/\underline{-168.69^\circ} \text{ A}$$

[d]

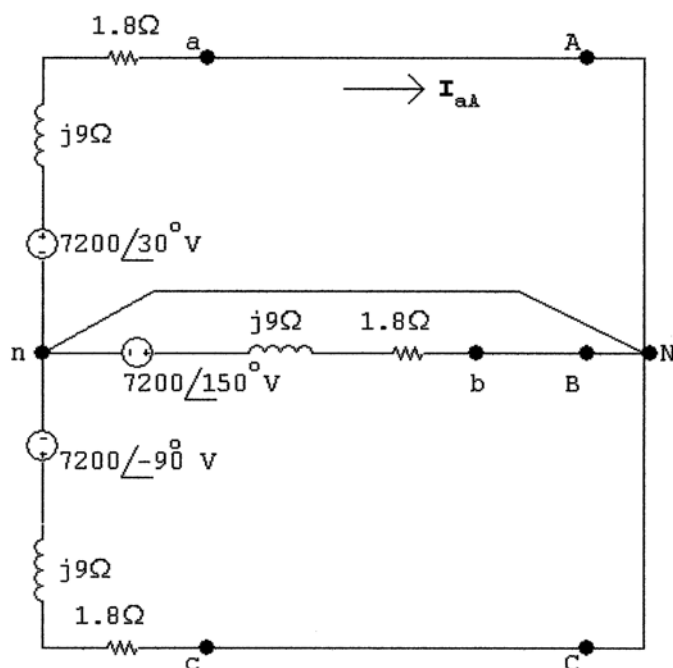


$$\mathbf{I}_{aA} = \frac{7200\angle 30^\circ}{1.8 + j9} = 784.46/\underline{-48.69^\circ} \text{ A}$$

Problem 3:

The Δ -connected source of Problem 2 is connected to a Y-connected load by means of a balanced three-phase distribution line. The load impedance is $957+j259 \Omega$ per phase. And the line impedance is $1.2+j12 \Omega$ per phase.

- Construct a single-phase equivalent circuit of the system.
- Determine the magnitude of the line voltage at the terminals of the load.
- Determine the magnitude of the phase current in the Δ -source.
- Determine the magnitude of the line voltage at the terminals of the source.

[a]

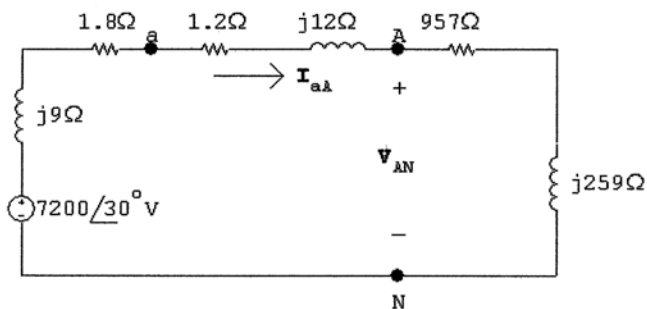

$$[b] \mathbf{I}_{aA} = \frac{7200/30^\circ}{960 + j280} = 7.2/13.74^\circ \text{ A}$$

$$\mathbf{V}_{AN} = (957 + j259)(7.2/13.74^\circ) = 7138.28/28.88^\circ \text{ V}$$

$$|\mathbf{V}_{AB}| = \sqrt{3}(7138.28) = 12,363.87 \text{ V}$$

$$[c] |\mathbf{I}_{ba}| = \frac{7.2}{\sqrt{3}} = 4.16 \text{ A}$$

$$[d] \mathbf{V}_{an} = (958.2 + j271)(7.20/13.74^\circ) = 7169.65/29.54^\circ \text{ V}$$

$$|\mathbf{V}_{ab}| = \sqrt{3}(7169.65) = 12,418.20 \text{ V}$$

Problem 4:

A three-phase positive sequence Y-connected source supplies 14kVA with a power factor of 0.75 lagging to a parallel combination of a Y-connected load and a Δ -connected load. The Y-connected load used 9 kVA at a power factor of 0.6 lagging and has an a-phase current of $10\angle -30^\circ$ A.

- Find the complex power per phase of the Δ -connected load.
- Find the magnitude of the line voltage.

$$[\mathbf{a}] S_{T\Delta} = 14,000\angle 41.41^\circ - 9000\angle 53.13^\circ = 5.5\angle 22^\circ \text{ kVA}$$

$$S_{\Delta} = S_{T\Delta}/3 = 1833.46\angle 22^\circ \text{ VA}$$

$$[\mathbf{b}] |\mathbf{V}_{an}| = \left| \frac{3000\angle 53.13^\circ}{10\angle -30^\circ} \right| = 300 \text{ V(rms)}$$

$$|\mathbf{V}_{line}| = |\mathbf{V}_{ab}| = \sqrt{3}|\mathbf{V}_{an}| = 300\sqrt{3} = 519.62 \text{ V(rms)}$$