

EE205 Two-Ports Networks

Properties and Analysis

Dr. Ali Muqaibel

Reciprocal Two-Port Circuits

- A two-port circuit is reciprocal if the interchange of an ideal voltage source at one port with an ideal ammeter at the other port produces the same ammeter reading.

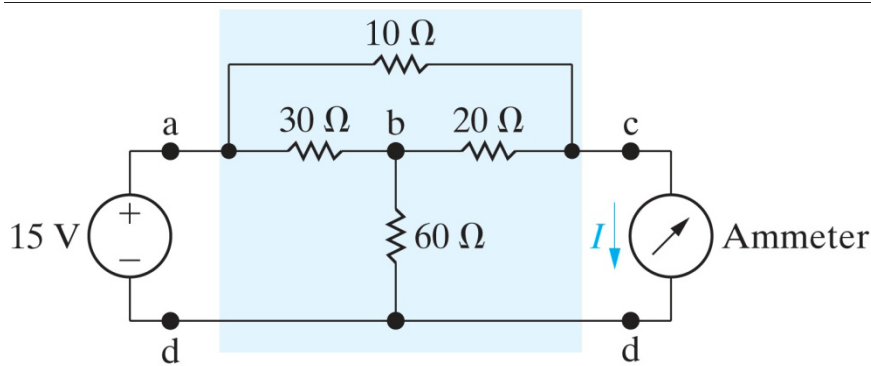


Figure: 18-04

Copyright © 2008 Pearson Prentice Hall, Inc.

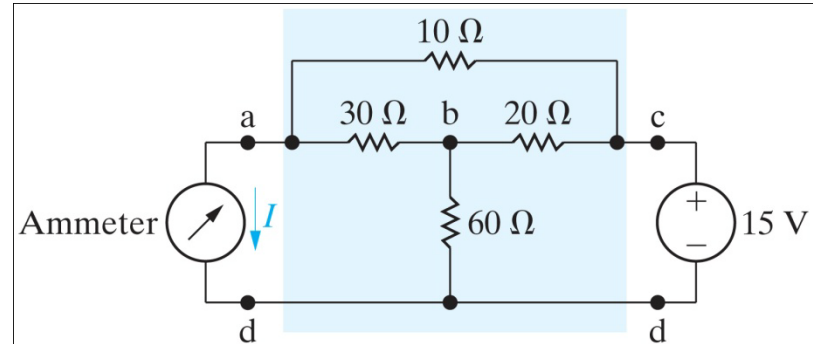


Figure: 18-05

Copyright © 2008 Pearson Prentice Hall, Inc.

$$I = 1.75 \text{ A}$$

Cont... Reciprocal Networks

- A two-port circuit is also reciprocal if the interchange of an ideal current source at one port with an ideal voltmeter at the other port produces the same voltmeter reading.
- Only three calculations or measurements can be made to determine the parameters.
- For a reciprocal network, the following is true:

$$z_{12} = z_{21}$$

$$y_{12} = y_{21}$$

$$\Delta a = 1$$

$$\Delta b = 1$$

$$h_{12} = -h_{21}$$

$$g_{12} = -g_{21}$$

Symmetric Networks

- A reciprocal two-port circuit is symmetric if its ports can be interchanged without disturbing the values of the terminal currents and voltages.
- For symmetric networks, the following additional features are true:

$$z_{11}=z_{22}$$

$$y_{11}=y_{22}$$

$$a_{11}=a_{22}$$


$$b_{11}=b_{22}$$

$$\Delta h=1$$


$$\Delta g=1$$

- Only two measurements or calculations are required.

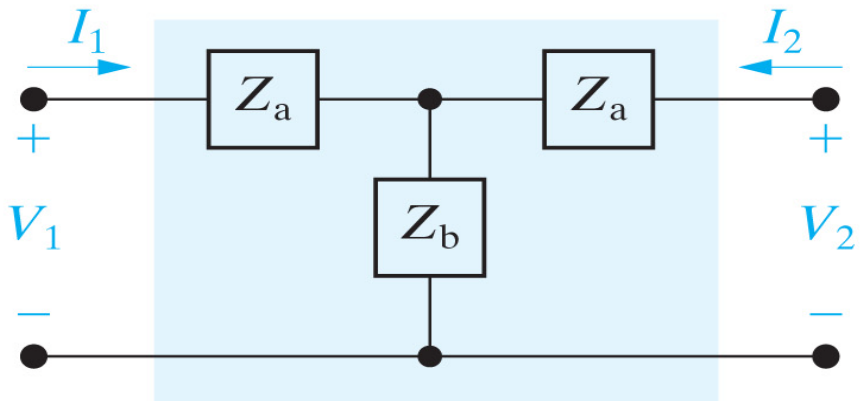
Symmetric two port networks: (a) Tee (b) pi (c) bridged tee (d) lattice




(a)

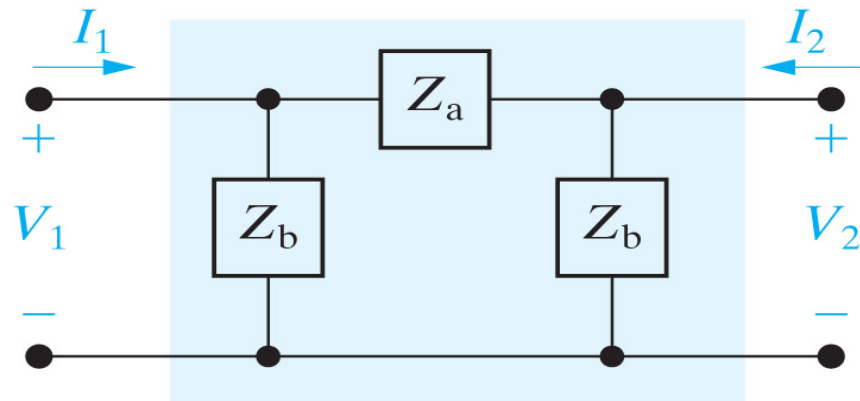

(b)

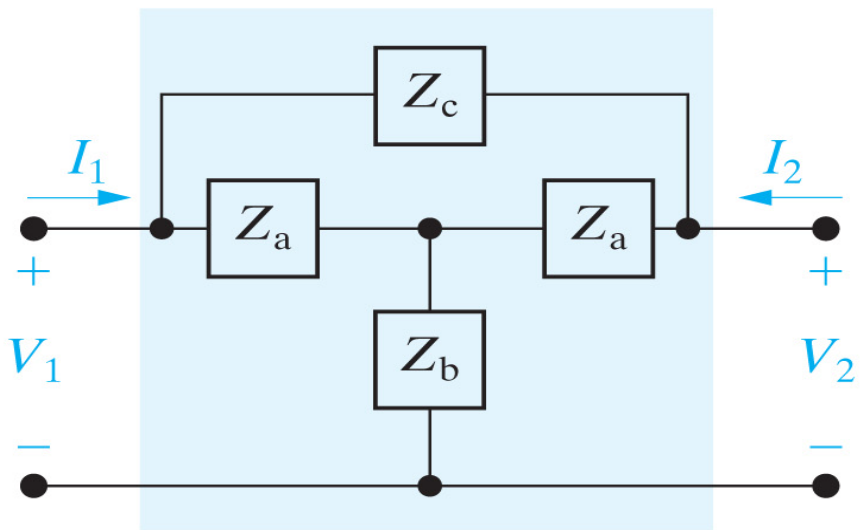

(c)

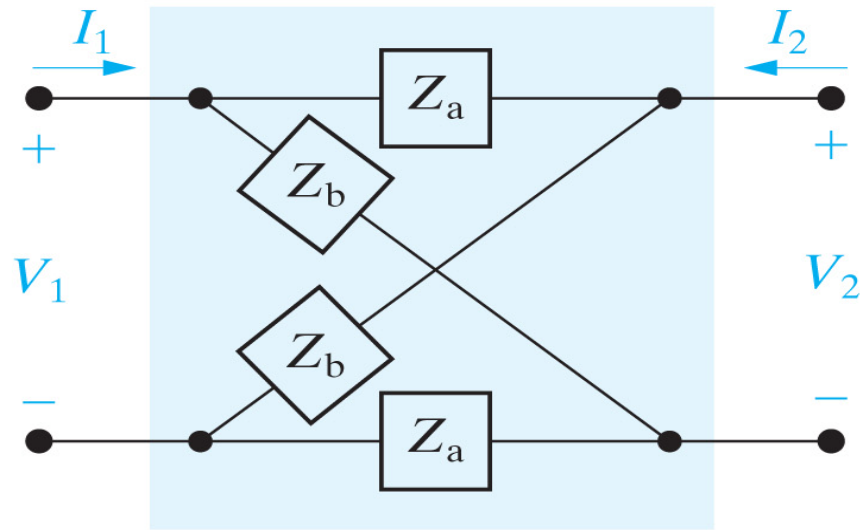

(d)

Figure: 18-06a-d

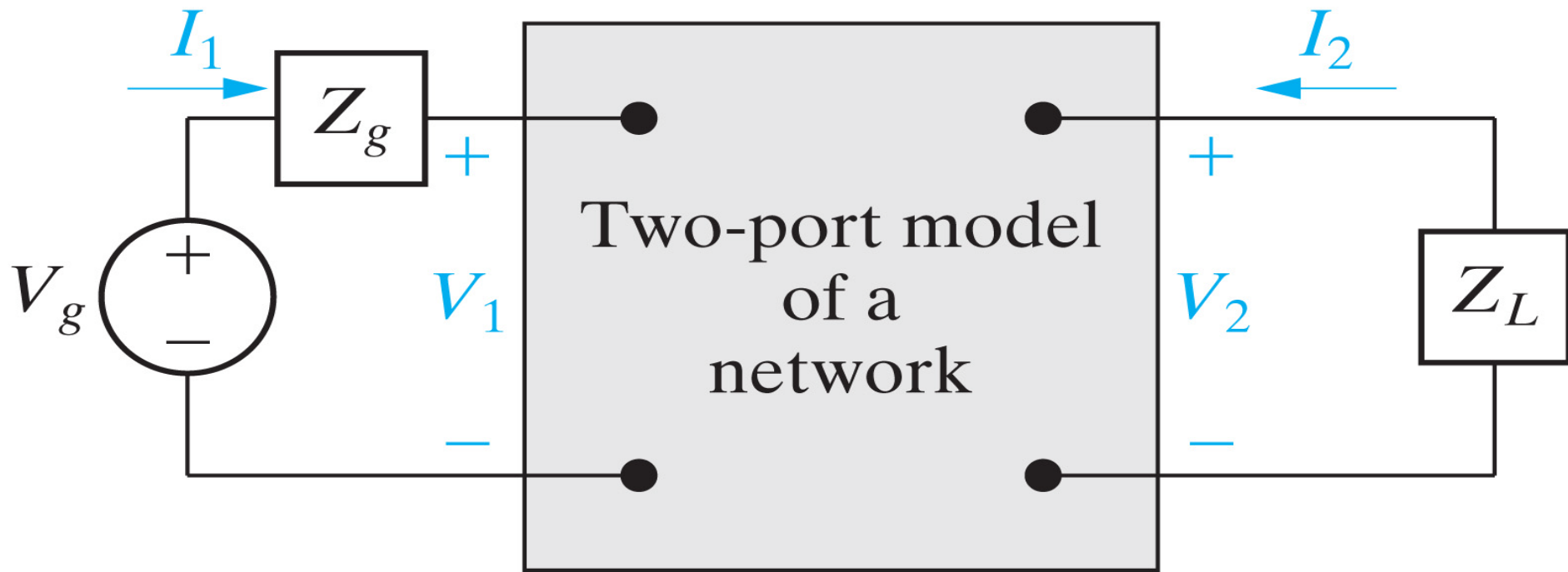


Figure: 18-07

Copyright © 2008 Pearson Prentice Hall, Inc.

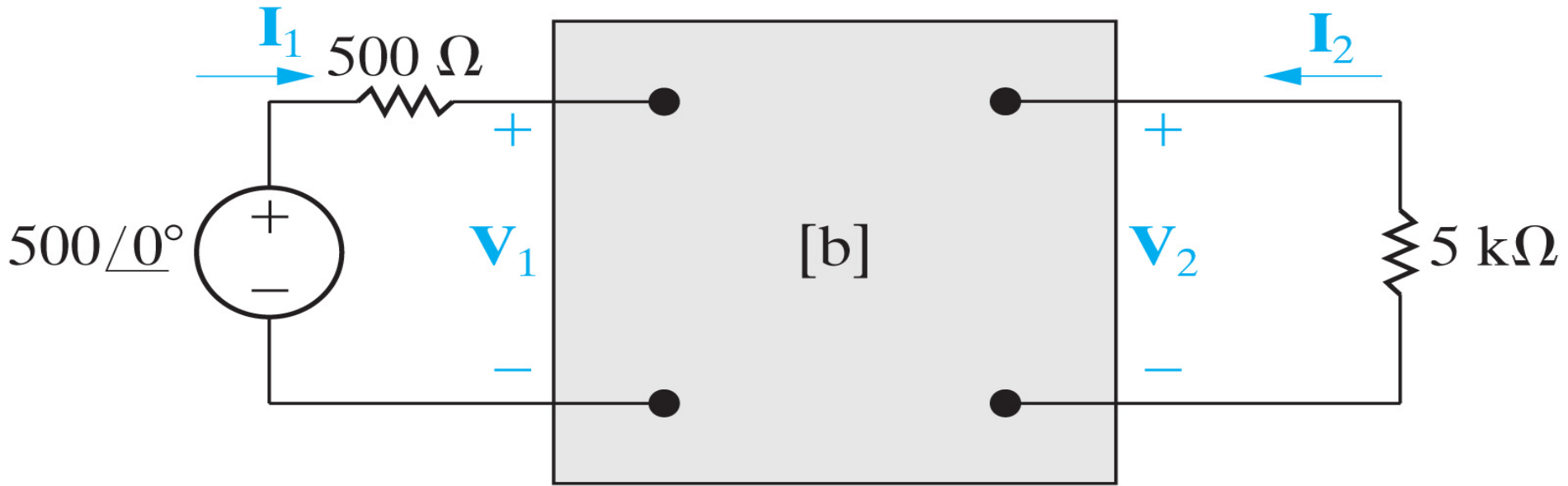


Figure: 18-08Ex18.4

Copyright © 2008 Pearson Prentice Hall, Inc.