


KEY

Major Exam I EE2025 031

Q1) a)

1. Supports voltage level control.
2. Reduces the amount of power loss in the lines.

b)

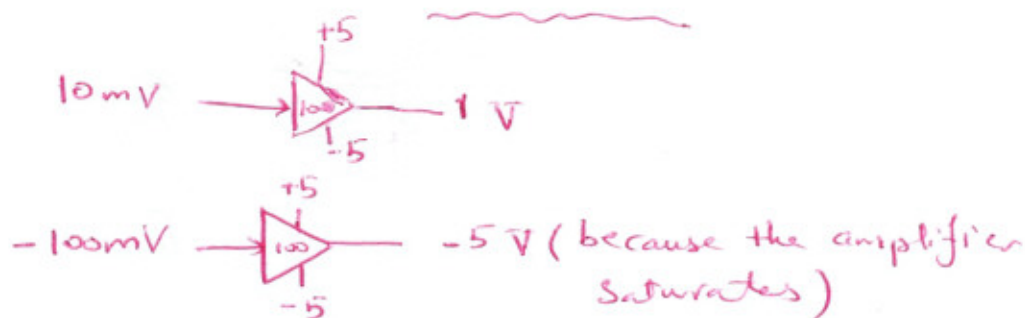

c) Overdamped.

d) Good, because the torque developed at the shaft of a three-phase motor is constant, which in turns means less vibration.

Dr. Ali Mugeibet

Q 2)

$$a) \quad I_{AB} = \frac{V_{AB} \angle 0^\circ}{Z_{AB}} = \frac{13800 \angle 0^\circ}{480 + j135} = \frac{13800 \angle 0^\circ}{498.62 \angle 15.71^\circ}$$

$$= 27.68 \angle -15.71^\circ \quad (\text{-ve seq.})$$

$$I_{BC} = 27.68 \angle 104.29^\circ, \quad I_{CA} = 27.68 \angle -135.71^\circ$$

$$b) \quad \cos \theta = \cos \theta_{r,i} = 0.963 \quad \text{lagging.}$$

$$c) \quad P_T = \sqrt{3} V_L I_L \cos \theta_p = 3 V_p I_p \cos \theta_p = 3 (13.8k) (27.68) (0.963) = 1.10355 \text{ MW}$$

$$Q_T = \sqrt{3} V_L I_L \sin \theta_p = 3 V_L I_L \sin \theta_p = 3 (13.8k) (27.68) (0.27) = 309.407 \text{ KVAR}$$

$$d) \quad I_{aA} = I_{AB} * \sqrt{3} \angle +30^\circ = 47.94 \angle 14.29^\circ$$

$$I_{bB} = 47.94 \angle 134.29^\circ, \quad I_{cC} = 47.94 \angle -105.71^\circ$$

e) We have to convert to Y


$$Z_Y = \frac{Z_\Delta}{3} = \frac{160 + j45}{3} = 166.21 \angle -15.71^\circ$$

$$V_{an} = I_{aA} (Z_{line} + Z_{load})$$

$$= 47.94 \angle 14.29^\circ (161 + j47)$$

$$|V_{an}| = 8040.5 \text{ V}$$

$$|V_{ab}| = 13.926 \text{ kV}$$

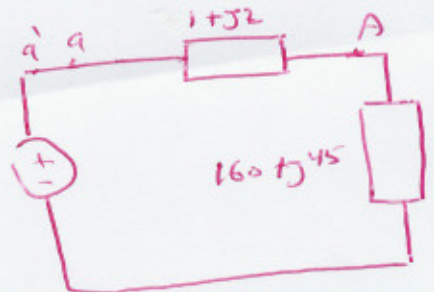

$$f) \text{ losses} = 3 I_{\text{line}}^2 R_{\text{line}} = 3 (47.94)^2 (1) = 6.894 \text{ kW}$$

$$\eta = \frac{1.10355 \times 10^6}{1.10355 \times 10^6 + 6.894 \text{ k}} = 99.37\%$$


---

Q3)

a)  $V_o(0^-) = 20 \text{ V}$


$i_o(0^-) = \frac{+48}{16\text{k}} = 3 \text{ mA}$

$V_c(0^-) = 20 - 3(12) = -16 \text{ V}$

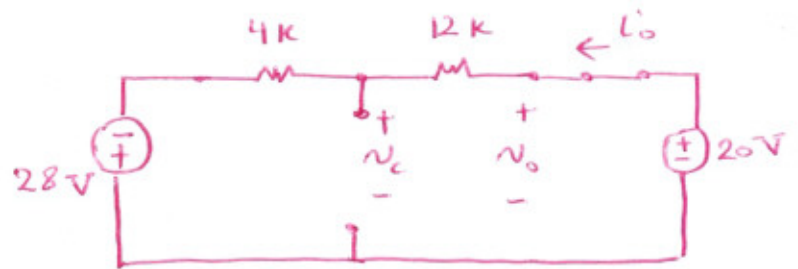

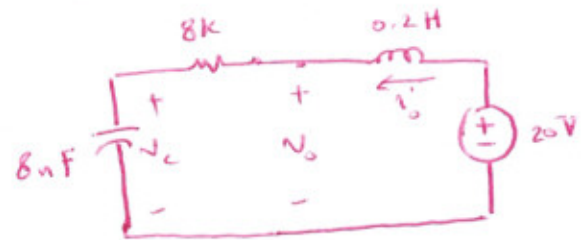b)  $24\text{k} // 12\text{k} = 8\text{k}$

$\frac{dV_c(0^+)}{dt} = \frac{i_o(0^+)}{C} = \frac{3\text{m}}{8\text{n}} = 375000 \text{ V/s}$



By KVL

$L \frac{di_o}{dt} + 8ki_o + V_c - 20 = 0$

$\Rightarrow \frac{di_o(0^+)}{dt} = \frac{1}{0.2} (20 - V_c(0^-) - 8ki_o) = 5(20 + 16 - 24) = 60 \text{ A/s}$

$V_o(0^+) = V_c(0^+) + 8k i_o(0^+) = -16 + 24 = 8 \text{ V}$

c)  $\alpha = \frac{R}{2L} = \frac{8000}{2 \times 0.2} = 20000 \quad \alpha^2 = 400 \times 10^6$

$\omega_c^2 = \frac{1}{LC} = \frac{10^9}{1.6} = 625 \times 10^6 \quad \alpha^2 < \omega_c^2 \text{ underdamped.}$

$s_{1,2} = -20000 \pm j 15000 \text{ rad/s}$

d)  $V_c(t) = V_f + B_1 e^{-20000t} \cos 15000t + B_2 e^{-20000t} \sin 15000t$

$V_f = V_c(\infty) = 20 \text{ V}$

$-16 = 20 + B_1 \Rightarrow B_1 = -36 \text{ V}$

$-20000 B_1 + 15000 B_2 = 375000$

$-20(-36) + 15 B_2 = 375 \Rightarrow B_2 = -23 \text{ V}$

e)

$$\dot{I}_0 = c \frac{dV}{dt}$$

by taking the derivative and \* by c.

---

f)

$$N_0 = N_c + (8K) \dot{I}_0$$

---

Q4) a) By KVL (dependent source, C, L<sub>1</sub>)

$$6i_x + v_c - \frac{1}{4} \frac{di_1}{dt} = 0$$

$$\frac{di_1}{dt} = 24i_x + 4v_c \quad \text{--- (1)}$$

By KVL (dependent source, 2Ω, L<sub>2</sub>)

$$\frac{1}{2} \frac{di_2}{dt} - 6i_x - 2i_x = 0$$

$$\frac{di_2}{dt} = 16i_x \quad \text{--- (2)}$$

By KCL

$$\frac{1}{8} \frac{dv_c}{dt} + i_1 = i_x + i_2$$

$$\Rightarrow \frac{dv_c}{dt} = -8i_1 + 8i_2 + 8i_x \quad \text{--- (3)}$$

By KVL

$$-v_s + 2i_x + 6i_x + v_c = 0$$

$$\Rightarrow 8i_x = -v_c + v_s \Rightarrow i_x = \frac{1}{8}(v_s - v_c) \quad \text{--- (4)}$$

Substitut  $i_x$  in (1), (2) & (3)

$$\frac{di_1}{dt} = 3v_s - 3v_c + 4v_c = 3v_s + v_c$$

$$\frac{di_2}{dt} = 2v_s - 2v_c$$

$$\frac{dv_c}{dt} = -8i_1 + 8i_2 + v_s - v_c$$

$$\frac{d}{dt} \begin{bmatrix} i_1 \\ i_2 \\ v_c \end{bmatrix} = \begin{bmatrix} 0 & 0 & 1 \\ 0 & 0 & -2 \\ -8 & 8 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ v_c \end{bmatrix} + \begin{bmatrix} 3 \\ 2 \\ 1 \end{bmatrix} v_s$$

$$b) \quad x_i([k+1]\Delta t) \approx x_i(k\Delta t) + [a_{i1}x_1(k\Delta t) + a_{i2}x_2(k\Delta t) + a_{i3}x_3(k\Delta t) + b_i v(k\Delta t)] \Delta t$$

$$\Delta t = 0.001 \text{ s} \quad k=1$$

$$i_1(0.001) \approx i_1(0) + [v_c(0) + 3 v_s(0)] \Delta t$$

$$= 0.9 + [10 + 90] 0.001$$

$$= 0.9 + 0.1 = 1 \text{ A}$$