

**King Fahd University of Petroleum & Minerals**  
Electrical Engineering Department  
EE205: Electric Circuits II (031)

**Major Exam II**

Dec 17, 2003

7:0PM-8:30PM

Building 19-416

Serial #

Name: K E Y

ID: \_\_\_\_\_

Sec. (1) 8:00-8:50 (2) 9:00-9:50

<b>Question</b>	<b>Mark</b>
1	/10
2	/10
3	/10
Total	/30

**Good luck**

Dr. Ali Muqaibel

$$\begin{aligned}\cos(\theta - 90^\circ) &= \sin \theta \\ \sin^2 \theta &= \frac{1}{2} [1 - \cos(2\theta)] \\ \cos^2 \theta &= \frac{1}{2} [1 + \cos(2\theta)] \\ \sin \theta - \cos \theta &= \sqrt{2} \sin(\theta - 45^\circ)\end{aligned}$$

Problem 1:



For the circuit shown :

1. Find the resonance frequency. (3 points)

2. Find the Quality factor given that  $R = 12\Omega$ ,  $L = 2H$ , and  $C = \frac{1}{36}F$ . (6 points)

- (Hint: you may assume that you have a current source  $i(t) = \cos(\omega t)$  or  $1\angle 0^\circ$ )  
 3. Frequency scaling: what values of  $R$ ,  $L$ , and  $C$  will result in doubling the (1 point)  
 resonance frequency of the same circuit.

1.  $Z_{in}$

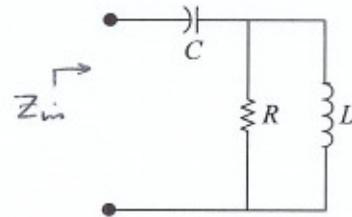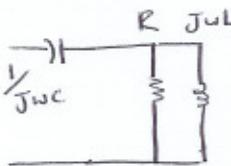

$$\begin{aligned}Z_{in} &= \frac{1}{J\omega C} + \frac{J\omega L R}{R + J\omega L} \\ &= \frac{-J}{\omega C} + \frac{J\omega L R (R - J\omega L)}{R^2 + \omega^2 L^2} \\ &= \frac{-J}{\omega C} + \frac{J\omega L R^2}{R^2 + \omega^2 L^2} + \text{real}\end{aligned}$$

at resonance  $\text{imag}(Z_{in}) = 0$

$$\frac{-1}{\omega_r^2} + \frac{\omega_r^2 L R^2}{R^2 + \omega_r^2 L^2} = 0$$


$$R^2 + \omega_r^2 L^2 = \omega_r^2 L C R^2$$

$$\omega_r^2 (-L^2 + L C R^2) = R^2$$

$$\omega_r^2 = \frac{R^2}{-L^2 + L C R^2}$$

$$\omega_r = \frac{1}{\sqrt{LC - \frac{L^2}{R^2}}}$$

2. In the frequency domain

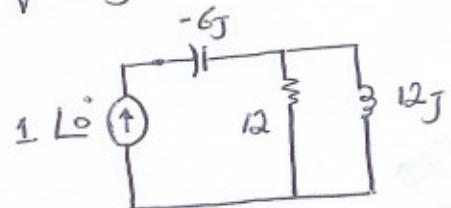

the quality factor is calculated at resonance.

$$\omega_r = \frac{1}{\sqrt{2\left(\frac{1}{36}\right) - \left(\frac{1}{12}\right)^2}} = 6 \text{ rad/s}$$

$$Z_c = \frac{1}{J\omega C} = -6j$$

$$Z_L = J\omega L = 12j$$

$$V_C = 1 L^o (-6j) = 6 L^{-90^\circ}$$

By current divider.

$$I_R = \frac{12j}{12 + 12j} 1 L^o = \frac{1}{\sqrt{2}} L^{+45^\circ}$$

$$I_L = \frac{12}{12 + 12j} 1 L^o = \frac{1}{\sqrt{2}} L^{-45^\circ}$$

continue #1.2

$$\omega_c = \frac{1}{2} C V_c^2 = \frac{1}{2} \frac{1}{36} (6)^2 \cos^2(6t - 90^\circ)$$
$$= \frac{1}{2} \sin^2(6t) = \frac{1}{4} [1 - \cos 12t]$$

$$\omega_L = \frac{1}{2} L I_i^2 = \frac{1}{2} (2) \left(\frac{1}{\sqrt{2}}\right)^2 \cos^2(6t - 45^\circ)$$
$$= \frac{1}{4} [1 + \cos(12t - 90^\circ)]$$
$$= \frac{1}{4} [1 + \sin 12t]$$

$$\omega_c + \omega_L = \frac{1}{4} [2 + \sin 12t - \cos 12t]$$
$$= \frac{1}{4} [2 + \sqrt{2} \sin(12t - 45^\circ)]$$

$$[\omega_c + \omega_L]_{\max} = \frac{1}{4} [2 + \sqrt{2}] \quad .5$$

Power in the resistor.

$$P_R = \frac{1}{2} |I_e|^2 R = \frac{1}{2} \left(\frac{1}{\sqrt{2}}\right)^2 (12) = 3 \text{ W}$$

$$T = \frac{2\pi}{\omega} = \frac{2\pi}{6} = \frac{\pi}{3} \text{ s}$$

$$P_R T = (3) \left(\frac{\pi}{3}\right) = \pi \text{ J}$$

$$Q = 2\pi \left(\frac{\omega_{\max}}{P_R T}\right) = 2\pi \left(\frac{\frac{1}{4}[2+\sqrt{2}]}{\pi}\right)$$
$$= \frac{1}{2}[2+\sqrt{2}] = 1 + \frac{1}{\sqrt{2}}$$

3. Frequency scaling.

$$k_f = 2 \text{ (double)}$$

$$R \rightarrow R \quad R = 12 \Omega$$

$$L \rightarrow \frac{L}{k_f} \quad L = 1 \text{ H}$$

$$C \rightarrow \frac{C}{k_f} \quad C = \frac{1}{72} \text{ F}$$

**Problem 2:**

For the following circuit:

- 1) Find the transfer function  $H(s) = \frac{V_2}{V_1}$  (5 points)
- 2) Draw the pole-zero plot of  $H(s)$  (3 points)
- 3) If the input voltage is  $v_1(t) = 10e^{-6t} \cos 3t$  V, what is the output voltage  $v_2(t)$  (2 points)

1)

By KVL in loop ②

$$-V_x - 2V_x + V_2 = 0$$

$$\Rightarrow V_2 = 3V_x \Rightarrow \boxed{V_x = \frac{V_2}{3}}$$

By KCL at node ③

$$\frac{V_1 - V_x}{1} = \frac{V_x}{1/5s} + \frac{V_2}{3+3s}$$

$$V_1 - \frac{1}{3}V_2 = 5s\left(\frac{V_2}{3}\right) + \left(\frac{V_2}{3}\right) \frac{1}{1+s}$$

\*3

$$3V_1 = \left(5s + \frac{1}{1+s} + 1\right)V_2$$

$$\frac{3V_1}{V_2} = \frac{5s + 5s^2 + 1 + 1 + s}{1 + s}$$



$$\frac{V_2}{V_1} = \frac{3(s+1)}{5s^2 + 6s + 2}$$

2) one zero  $s = -1$

two poles

$$s_1, s_2 = \frac{-6 \pm \sqrt{36 - 40}}{10}$$
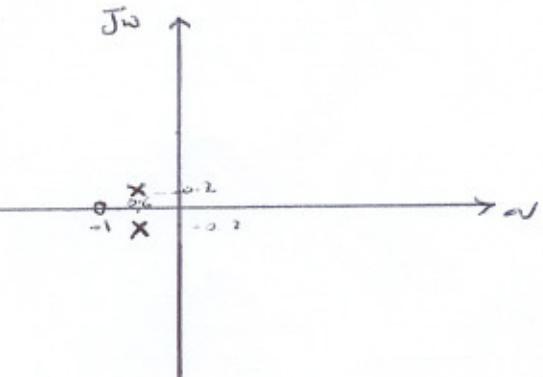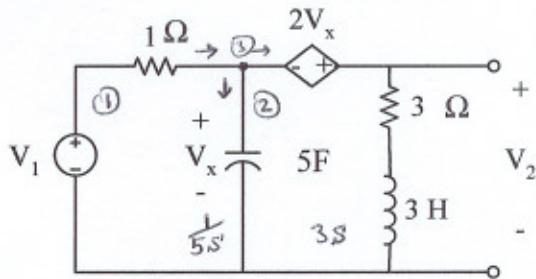
$$= \frac{-6 \pm j2}{10} = -0.6 \pm j0.2$$



3)  $s = -6 + 3j$   $V_1 = 10 L^\circ$

$$\frac{V_2}{V_1} = \frac{3(3j - 5)}{5(-6 + 3j)^2 + 18j - 36 + 2}$$

$$= \frac{9j - 15}{5(36 - 9 - 36j) + 18j - 34}$$

$$= \frac{9j - 15}{185 - 180j + 18j - 34}$$

$$= \frac{9j - 15}{101 - 162j} = \frac{17.49}{190.9} \frac{L149}{L-58.06}^\circ$$

$$= 0.0916 L207.1^\circ$$

if  $V_1 = 10 L^\circ$


$$\Rightarrow V_2 = 10 * 0.0916 L207.1^\circ = 0.916 L207.1^\circ$$

$$\Rightarrow v_2(t) = 0.916 e^{-6t} \cos(3t + 207.1) V$$

### Problem 3:

The parameters of a certain linear transformer are  $R_1=200\Omega$ ,  $R_2=100\Omega$ ,  $L_1=16\text{ H}$ ,  $L_2=4\text{ H}$ , and  $k=0.75$ . The transformer couples an impedance consisting of an  $800\Omega$  resistor in series with a  $1\mu\text{F}$  capacitor to a sinusoidal voltage source. The  $200\text{ V}$  (rms) source has an internal impedance of  $400+j100\Omega$  and a frequency of  $400\text{ rad/s}$ .

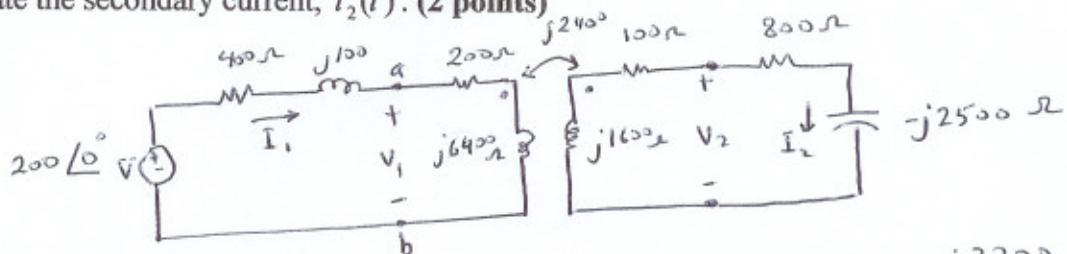- 1) Construct the frequency-domain equivalent circuit of the system. (2 points)
- 2) Calculate the self-impedance of the primary circuit. (0.5 point)
- 3) Calculate the self-impedance of the secondary circuit. (0.5 point)
- 4) Calculate the impedance reflected into the primary winding. (2 points)
- 5) Calculate the impedance seen into the primary terminals of the transformer. (1 point)
- 6) Calculate the primary current,  $i_1(t)$ . (2 points)
- 7) Calculate the secondary current,  $i_2(t)$ . (2 points)



$$j\omega L_1 = j(400)(16) = j6400\Omega$$

$$j\omega L_2 = j(400)(4) = j1600\Omega$$

$$M = 0.75 \sqrt{(18)(4)} = 6\text{ H}$$

$$j\omega M = j(400)(6) = j2400\Omega$$

$$\frac{1}{j\omega C} = \frac{10^6}{j400} = -j2500\Omega$$

$$2) Z_{11} = 400 + j100 + 200 + j6400 = 600 + j6500\Omega$$

$$3) Z_{22} = 100 + 800 + j1600 - j2500 = 900 - j900\Omega$$

$$4) Z_Y = \frac{\omega^2 M^2}{|Z_{22}|^2} Z_{22}^* = \frac{(400)^2(6)^2}{|900-j900|^2} (900+j900) = \frac{32}{9} (900+j900) = 3200 + j3200\Omega$$

$$5) Z_{ab} = 200 + j6400 + j3200 + j3200 = 3400 + j9600\Omega$$

$$6) I_1 = \frac{200\angle 0^\circ}{400 + j100 + Z_{ab}}$$

$$I_1 = \frac{200\angle 0^\circ}{3800 + j9700} = 19.2 \angle -68.61^\circ \text{ mA}$$

$$I_{\text{amplitude}} = \sqrt{2} I_{\text{rms}} = 27.15 \text{ mA}$$

$$\Rightarrow i_1(t) = 27.15 \cos(400t - 68.61^\circ) \text{ mA}$$

7) By KVL in the secondary.

$$I_2 Z_{22} - I_1 j\omega M = 0$$

$$\Rightarrow I_2 = \frac{I_1 j\omega M}{Z_{22}} = \frac{(400)(6)\angle 90^\circ}{900 - j900} I_1$$

$$I_2 = 1.886 \angle 90^\circ + 45^\circ I_1$$

$$I_2 = 36.2 \angle 66.39^\circ \text{ mA}$$

$$I_{2\text{ amplitude}} = \sqrt{2} I_{2\text{ rms}} = 51.2 \text{ mA}$$

$$\Rightarrow i_2(t) = 51.2 \cos(400t + 66.39^\circ) \text{ mA}$$