

Quiz 2

Name:

KEY

ID#

Sec. 01

A balanced three-phase distribution line has an impedance of $1+j5 \Omega/\emptyset$. This line is used to supply a three-phase induction motor. This motor output 300 hp, with 96% efficiency and power factor of 0.90 lag. The magnitude of the line voltage at the terminal of the motor is 2080V (1 hp = 746 W)

- a) What is the magnitude of the line current drawn from the 2080V outlet?

$$P_{out} = 300 \text{ hp} \times \frac{746 \text{ W}}{1 \text{ hp}} = 223800 \text{ W}$$

$$\eta_{eff} = \frac{P_{out}}{P_{in}} \rightarrow P_{in} = \frac{223800}{0.96} = 233125 \text{ W}$$

$$\sqrt{3} V_L I_L \cos \theta = 233125$$

$$I_L = \frac{233125}{\sqrt{3} (2080)(0.9)} = 71.899 \text{ A}$$

- b) Calculate the reactive power supplied to the motor.

$$1 = \sin^2 \theta_\phi + \cos^2 \theta_\phi \Rightarrow \sin \theta_\phi = 0.436$$

$$Q = \sqrt{3} V_L I_L \sin \theta_\phi = \sqrt{3} (2080)(71.899)(0.436) = 112936.234 \text{ VAR}$$

- c) What is the total average power loss in the three-phase line?

$$P_{loss} = 3 I_L^2 R = 3 (71.899)^2 (1) = 15508.399 \text{ Watts}$$