

King Fahd University of Petroleum & Minerals
 Electrical Engineering Department
 EE205: Electric Circuits II (031)


Quiz 4

Name: **KEY**


ID#

Sec. 02

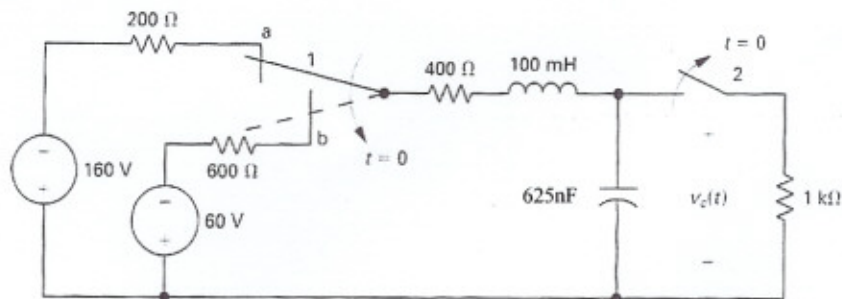The two switches in the circuit seen in the figure below operate synchronously. When switch 1 is in position a, switch 2 is closed. When switch 1 is in position b, switch 2 is open. Switch 1 has been in position a for a long time. At $t = 0$, it moves instantaneously to position b. Find $v_c(t)$ for $t \geq 0$.




for $t < 0$

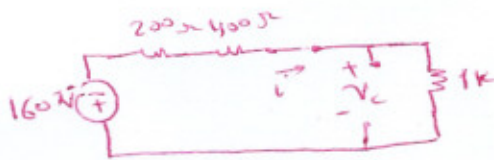

$$i_L(0) = \frac{-160}{1800} = -100 \text{ mA}$$

$$V_c = R_{L_{eq}} i_L = (1k)(-100m) = -100V$$

$t > 0$

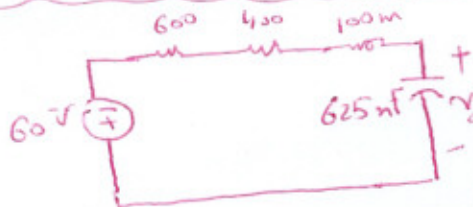

$$\alpha = \frac{R}{2L} = \frac{1000}{200m} = 5000 \text{ nepers}$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{100m \cdot 625n} = 16000000$$

$\omega_0^2 < \alpha^2$ over damped response

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -5000 + 3000 = -2000$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -5000 - 3000 = -8000$$

$$v_c(t) = V_f + A_1 e^{-2000t} + A_2 e^{-8000t}$$

$$V_f = v_c(\infty) = -60V$$

Using the initial conditions.

$$-100 = -60 + A_1 + A_2$$

$$\Rightarrow \boxed{-40 = A_1 + A_2} \quad \text{--- ①}$$

for the capacitor

$$\frac{dv_c(0)}{dt} = \frac{L(s)}{C} = \frac{-100m}{625n} = -160000 \text{ V/s}$$

$$+160000 = +2000 A_1 + 8000 A_2 \quad \text{--- ②}$$

$$\boxed{80 = A_1 + 4 A_2} \quad \text{--- ②}$$

$$\text{②} - \text{①} \Rightarrow 120 = 3 A_2 \Rightarrow \begin{cases} A_2 = 40 \\ A_1 = -80 \end{cases}$$

$$v_c(t) = -60 - 80 e^{-2000t} + 40 e^{-8000t} \text{ V}$$

$t \geq 0$