

**King Fahd University of Petroleum & Minerals**

Electrical Engineering Department  
EE205: Electric Circuits II (031)

**Quiz 6**

Name: **KEY**


ID#

Sec 01

For the op-amp circuit given in the figure, find the Transfer function

$H(s) = V_2/V_1$  and draw the pole-zero

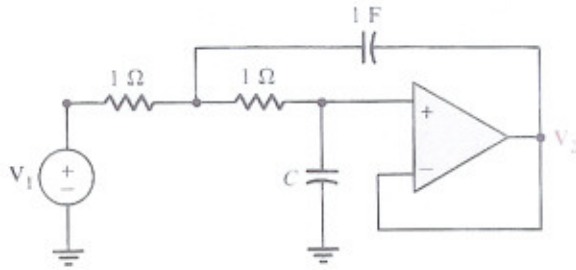plot for the case that  $C = \frac{4}{3} F$




By KCL at node v

$$\frac{V - V_1}{1} + \frac{V - V_2}{1} + \frac{V - V_2}{1/s} = 0$$

$$V - V_1 + V - V_2 + sV - sV_2 = 0$$

$$(s+2)V - V_1 - (s+1)V_2 = 0$$

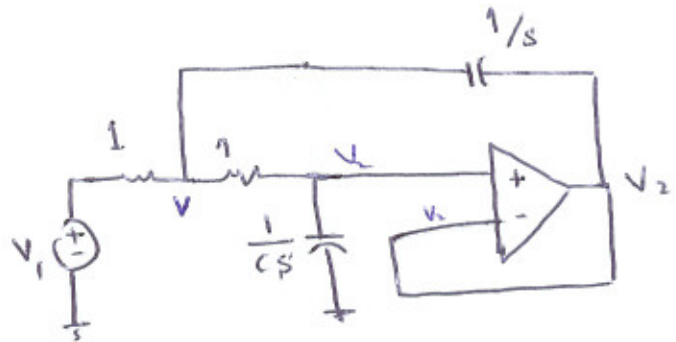

By KCL at node  $V_2$  (voltage divider)

$$V_2 = \frac{1/s}{1/s + 1} v = \frac{1}{1 + Cs} v \Rightarrow v = (1 + Cs)V_2$$


$$\Rightarrow (s+2)(Cs+1)V_2 - (s+1)V_2 = V_1$$

$$(Cs^2 + 2Cs + s + 2 - s - 1)V_2 = V_1 \Rightarrow H(s) = \frac{V_2}{V_1} = \frac{1}{Cs^2 + 2Cs + 1} = \frac{1/c}{s^2 + 2s + 1/c}$$

$$c = \frac{4}{3} \Rightarrow H(s) = \frac{3/4}{s^2 + 2s + 3/4}$$

No zeros. poles..
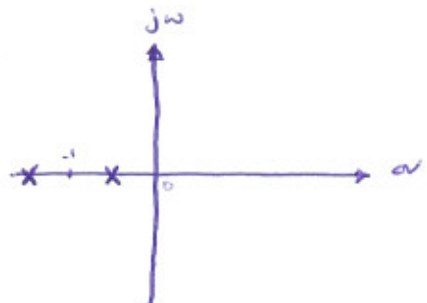
$$\frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{-2 \pm \sqrt{4 - 3}}{2} = -1 \pm \frac{1}{2} = -\frac{1}{2}, -1\frac{1}{2}$$



Good Luck,  
**Dr. Ali Muqaibel**