


Quiz 7

Name: KEY

Sec 02

a) What is the coefficient of coupling?

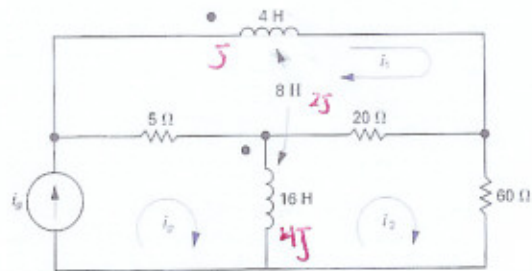b) Assume that the physical structure of these coupled coils is such that $P_1 = P_2$, (permeance 1 = permeance 2). What is the turns ratio N_2/N_1 , if N_1 is the number of turns on the 4H coil?



c) Write a set of mesh-current equations that describe the circuit in terms of the currents i_1 and i_2 in the frequency domain, where the source current, i_g , is known and it has $\omega = 0.25$ rad/s. (Hint: first represent in the $j\omega$ domain)

$$a) M = k \sqrt{L_1 L_2} \Rightarrow k = \frac{M}{\sqrt{L_1 L_2}} = \frac{8}{\sqrt{4 * 16}} = 1$$

$$b) L_1 = N_1^2 \mu, \quad L_2 = N_2^2 \mu$$

$$\frac{L_1}{L_2} = \frac{N_1^2 \mu}{N_2^2 \mu} \Rightarrow \frac{N_2}{N_1} = \sqrt{\frac{L_2}{L_1}} = \sqrt{\frac{16}{4}} = \sqrt{4} = 2$$

$$c) \begin{aligned} j\omega L_1 &= j(0.25)(4) = j \\ j\omega L_2 &= j(0.25)(16) = 4j \\ j\omega M &= j(0.25)(8) = 2j \end{aligned}$$

$$20(i_1 - i_2) + 5(i_1 - i_g) + j i_1 + 2j(i_g - i_2) = 0$$

$$60 i_2 + 4j(i_2 - i_g) - 2j i_1 + 20(i_2 - i_1) = 0$$