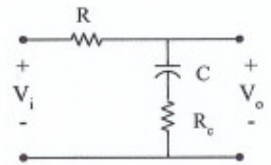


Name: KEY

For the circuit shown:



a) Derive an expression for the transfer function $H(s)$ where $H(s) = V_o/V_i$ (3 points)

b) At what frequency will the magnitude of $H(j\omega)$ be maximum. (1 point)

c) What is the maximum value of $H(j\omega)$? (1 point)

d) At what frequency will the magnitude of $H(j\omega)$ equal its maximum value divided by $\sqrt{2}$? (4 points)

e) what is the minimum value of the magnitude of $H(j\omega)$ and at what frequency does it occur?

a) By voltage divider.

$$H(s) = \frac{V_o}{V_i} = \frac{R_c + \frac{1}{sC}}{R_c + \frac{1}{sC} + R} = \frac{R_c C s + 1}{(R_c + R) C s + 1}$$

$$b) |H(j\omega)| = \frac{\sqrt{(R_c C \omega)^2 + 1}}{\sqrt{(R_c + R)^2 C^2 \omega^2 + 1}} = \frac{\sqrt{R_c^2 C^2 \omega^2 + 1}}{\sqrt{(R_c + R)^2 C^2 \omega^2 + 1}}$$

c) at $\omega = 0$ $|H(j\omega)| = 1$ max

other-wise always $(R_c + R)^2 C^2 \omega^2 > R_c^2 C^2 \omega^2$
 $\& |H(j\omega)| < 1$

$$d) \frac{C^2 R_c^2 \omega^2 + 1}{(C^2 R_c^2 + 2 R_c R C^2 + C^2 R^2) \omega^2 + 1} = \frac{1}{2} \Rightarrow 2 C^2 R_c^2 \omega^2 + 2 = C^2 R_c^2 \omega^2 + 2 R_c R C^2 \omega^2 + C^2 R^2 \omega^2 + 1$$

$$\Rightarrow C^2 R_c^2 \omega^2 - 2 R_c R C^2 \omega^2 - C^2 R^2 \omega^2 = -1$$

$$\omega^2 = \frac{-1}{C^2 (R_c^2 - 2 R_c R - R^2)} \Rightarrow \omega = \frac{1}{C \sqrt{R^2 + 2 R R_c - R_c^2}}$$

e) $|H(j\omega)_{min}| = \frac{R_c}{R_c + R}$ voltage divider as $\omega \rightarrow \infty$