

King Fahd University of Petroleum & Minerals



Excellent
 $\frac{5.0}{5.0}$

EE- 205

Project #1


Transient Response of Second Order RLC Circuits

Prepared for:
Dr. Ali Muqaibel

➤ Designing the value of R_1 :

If we want to design a value of R_1 to achieve a full charge of 10V across the capacitor, we have to consider the capacitor as an open circuit and the voltage across the R_2 is 10V. Then, using voltage divider rule we can obtain the value of R_1 :

 
$$V_{R_2} = \frac{R_2}{R_1 + R_2} V_S \implies 10 = \frac{1000}{1000 + R_1} 12 \implies R_1 = 200 \Omega$$



➤ Designing the time of closing the switch:

Actually if we want to close the switch when the capacitor is fully charged, this means it will close at ∞ . But because this is a parallel RC circuit, we can say that the capacitor is fully charged at about 7τ which is $7 \cdot R \cdot C$.

 So, $7\tau = 11.667$ ms. Then the switch will close at 11.667 ms.



➤ Designing the value of the inductor:


To achieve the final current value as fast as possible with an overshoot of 20%, we consider the under-damp situation. The final value is 60 mA (short-circuit so the whole current will pass) and with 20% it means 72 mA as maximum. But first we can obtain the value of L by considering the critical situation where: $\omega_n = \alpha$:

$$\frac{1}{\sqrt{LC}} = \frac{1}{2RC} \longrightarrow L = 4R^2C \longrightarrow L = 1.11 \text{ H}$$

To achieve the under-damped situation, ω_n must be greater than α . So we can decrease the value of L until we reach the maximum current of 72 mA. Using PSpice, I found that the best value I could have of L is: 354.75 mH and it takes 14.399 ms to achieve 60 mA which is the final value.

(PSpice specification: Transient analysis: print step = 20 ns, final time = 50 ms, step ceiling = 100 μ s)

Final Circuit Design:

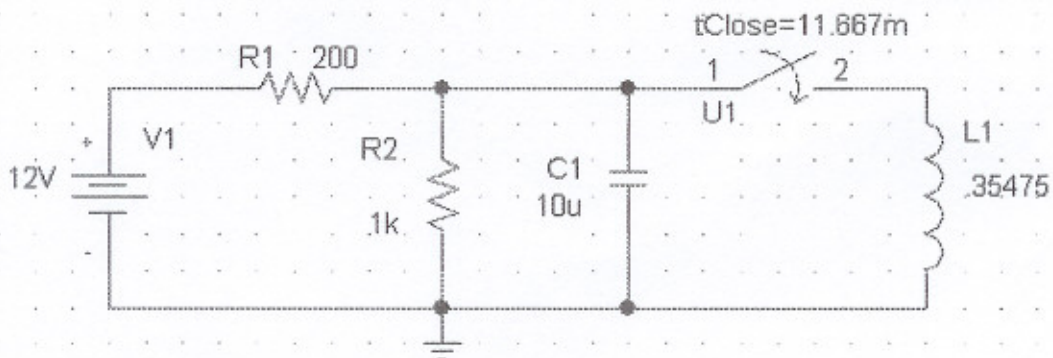

$V_s = 12 \text{ V dc}$


$R_1 = 200 \ \Omega$

$R_2 = 1 \text{ k}\Omega$


$C_1 = 10 \ \mu\text{F}$

$L_1 = 354.75 \text{ mH}$


Final circuit

 


(A) project1 (active) The RC circuit

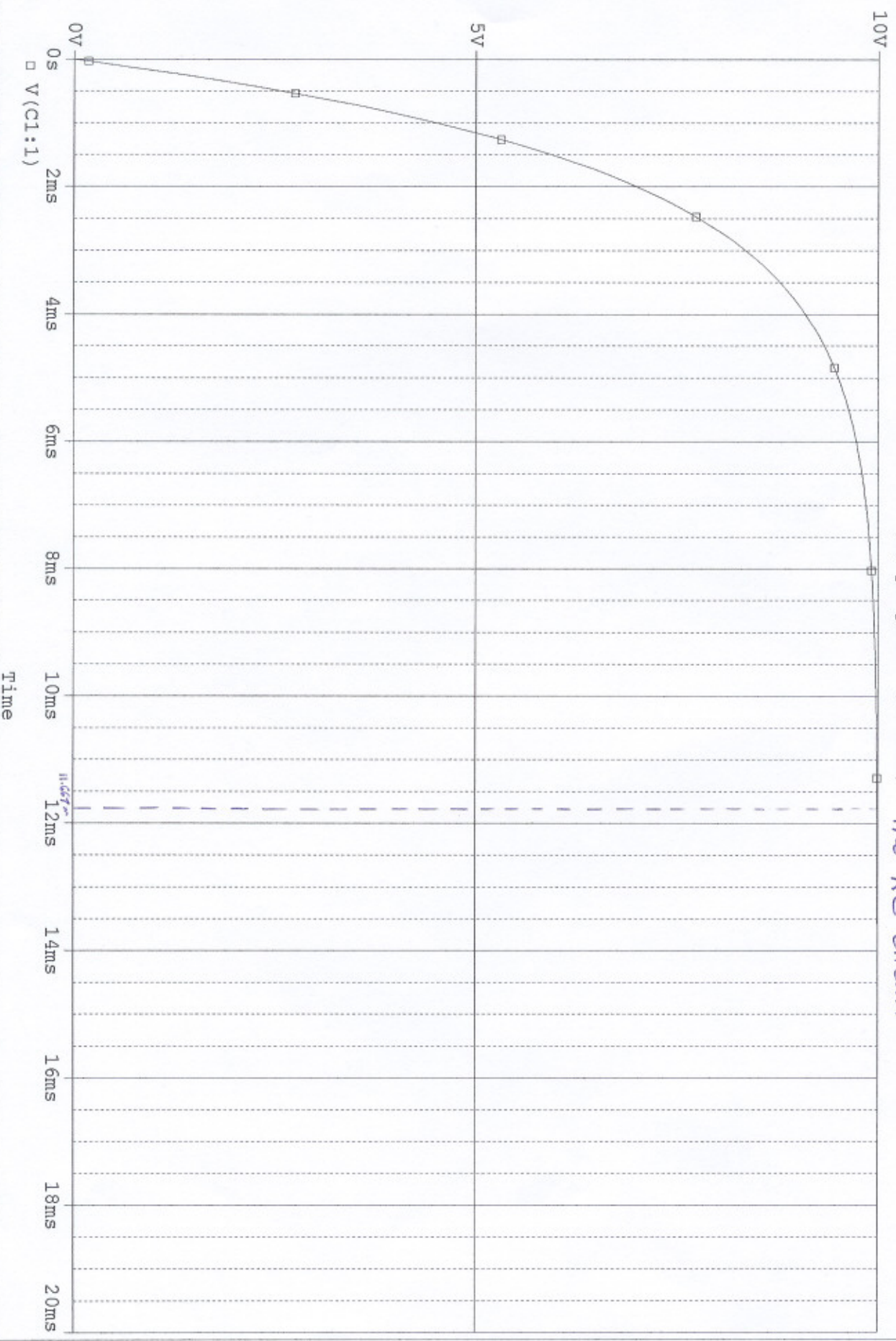


(A) project1 (active) Final circuit

 


(A) project1 (active) Final circuit

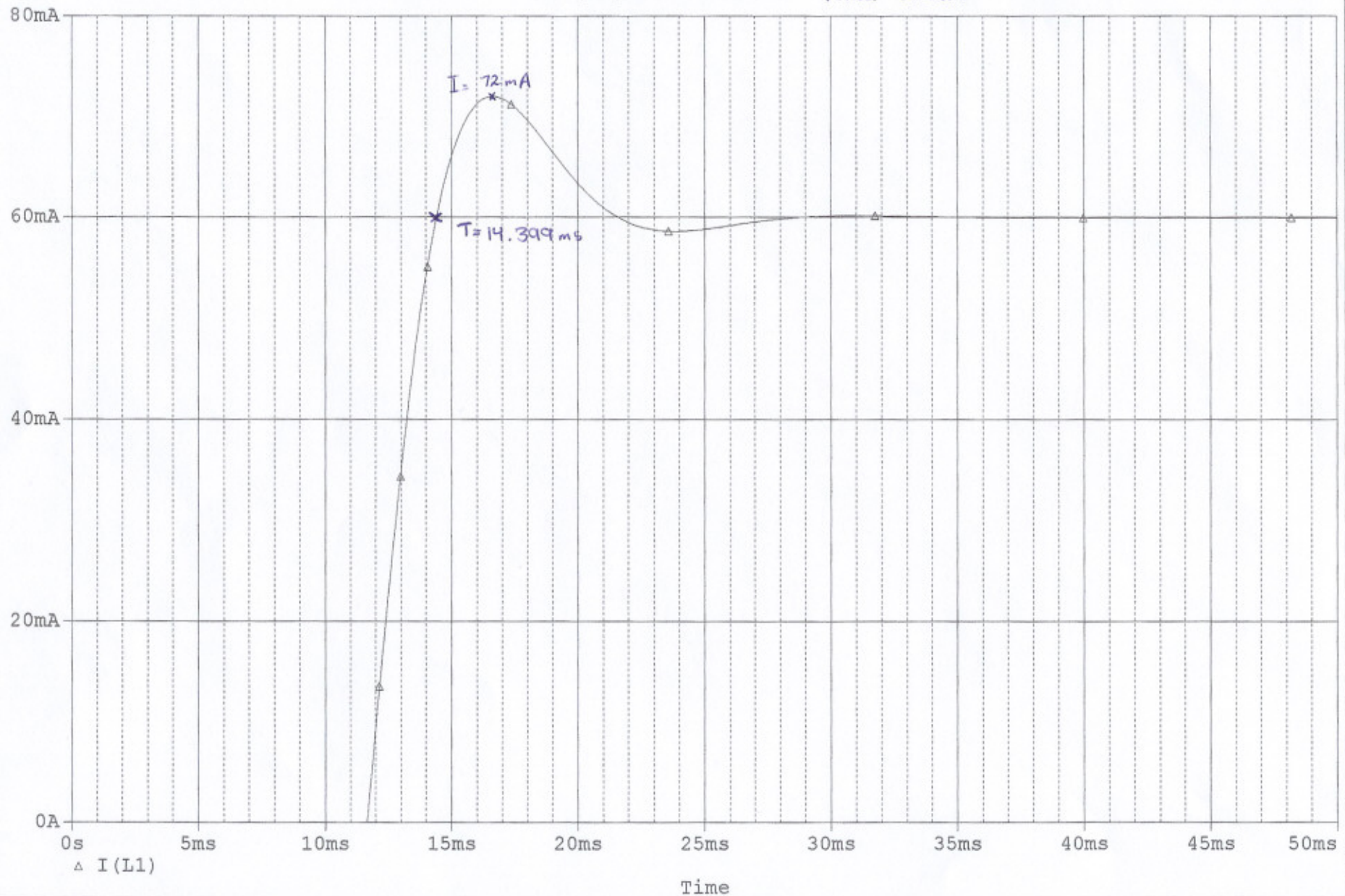

(A) project1 (active) Final circuit

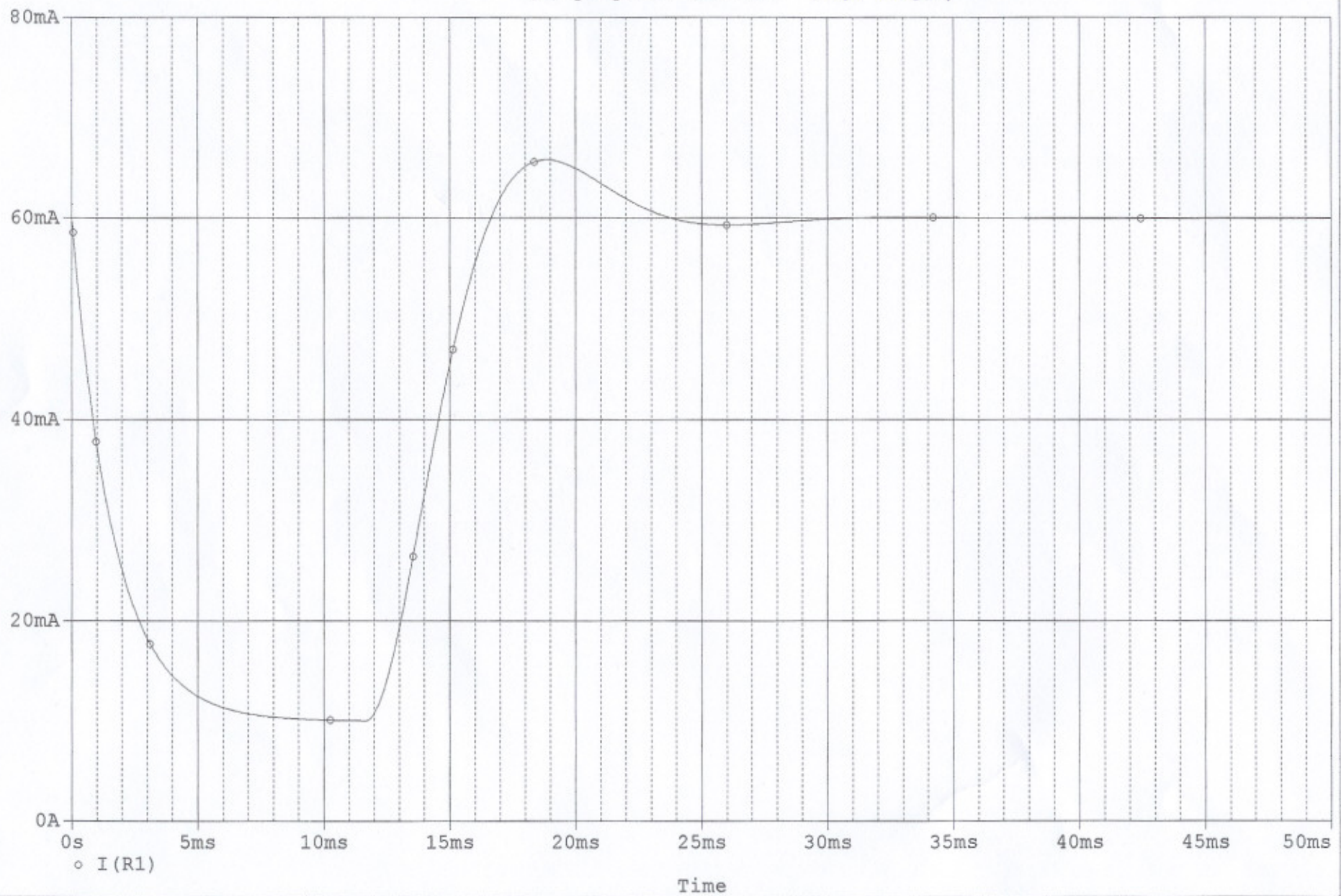

(A) project1 (active) Final circuit

 

(A) project1 (active) ALL currents - Final circuit

