

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS**Electrical Engineering Department****EE-205 Electric Circuits II****Spring 2009/2010(092) First Major Exam****Duration : 90 min.****Dr. E. Hassan,****Dr. A. Muqaibel,****Dr. S. Al-Ghadban,****Dr. H. Masoudi (Coordinator)**

Name :

ID #

Section #

Key

Question	Grade
1 (10 points)	
2 (10 points)	
3 (10 points)	
Total (30 points)	

Notes :

- 1) Read the question very carefully.
- 2) Use a sketch to help you understand the question.
- 3) Write neatly.

Final

Question 1

Write the correct answer in the box shown. Only answers in the box below will be graded

Answers' Box

1. a	2. d	3. e	4. c
5. d	6. b	7. b	

Do NOT Circle or Mark the answer in the questions. If you do so, it is considered cheating.

(Parts 1 to 4: 1 points each; Parts: 5 to 7 two points each)

(only one answer is correct)

1) In a three-phase balanced system, if I_{aA} is $17+j10$ A, then for a negative sequence I_{cC} will be:

- a) $19.72 \angle -89.53^\circ$
- b) $17-j10$
- c) $19.72 \angle 30.46^\circ$
- d) $-17+j10$
- e) None of the above is correct

2) In a three phase balanced positive sequence Y-Y connected system, if V_{AN} is $120 \angle 0^\circ$ V at the load, then (for a negligible line impedance) V_{bc} at the source will be:


- a) $1/\sqrt{3}$ times in magnitude but leading by 90°
- b) $\sqrt{3}$ times in magnitude but lagging by 150°
- c) $\sqrt{3}$ times in magnitude but leading by 120°
- d) $\sqrt{3}$ times in magnitude but lagging by 90°
- e) None of the above is correct

3) The complete solution for the voltage across the capacitor in a series RLC circuit of the step response with a DC source consists of:

- a) The function of the same form as the natural response
- b) The final value of the response function
- c) The function of the same form as the natural response and the final value of the response function if R is greater than C
- d) The function of the same form as the natural response and the final value of the response function if R is equal to C
- e) None of the above is correct


4) Assume the parallel RLC circuit of the step response shown, with $I = 24$ mA. The solution for $i_l(t)$ is

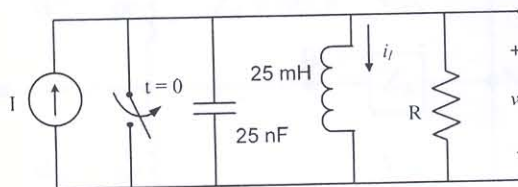- a) Over damped if $R = 625 \Omega$
- b) Under-damped if $R = 400 \Omega$
- c) Critically-damped if $R = 500 \Omega$
- d) All of the above are correct
- e) None of the above is correct




5) For the ideal Op-Amp circuit shown assume no energy in the capacitor before the switch is closed at $t = 0$. For $t \geq 0$, the Op-Amp

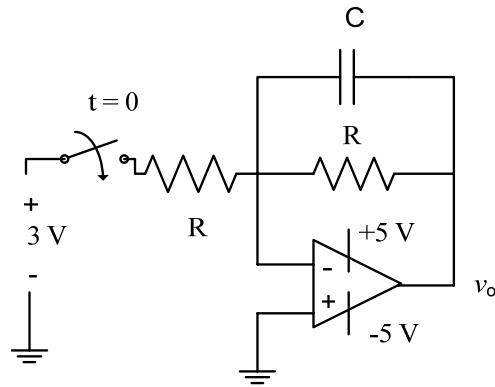- a) will saturate in 3 seconds
- b) will saturate in 5 seconds
- c) will saturate only if R is greater than C
- d) will never saturate
- e) None of the above is correct




6) Assume two balanced 3-phase systems. System A is a delta source with a phase voltage of V connected to a Y-load with a phase impedance of R. System B is a Y source of phase voltage V connected to a delta load of phase impedance of R. Comparing the total power absorbed by Load A and B, the following is true:

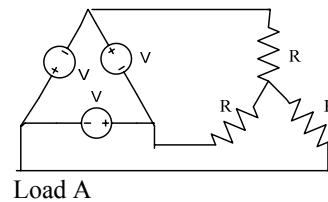- a) The power absorbed by load B is 18 times the power absorbed by load A
- b) The power absorbed by load B is 9 times the power absorbed by load A
- c) The power absorbed by load B is 6 times the power absorbed by load A
- d) The power absorbed by load B is 3 times the power absorbed by load A
- e) The power absorbed by load B is the same as the power absorbed by load A.



Load A

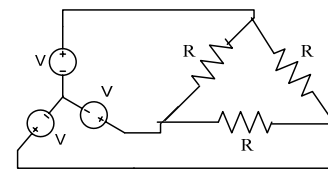

Load B

7) Using the two-wattmeter method, calculate the reading of each wattmeter in the given circuit if the phase voltage at the load is 120 V and $Z_\phi = 8 - j6 \Omega$.

- a) $W_1 = 979.75 \text{ W}$ and $W_2 = 2476.25 \text{ W}$
- b) $W_1 = 2476.25 \text{ W}$ and $W_2 = 979.75 \text{ W}$
- c) $W_1 = 565.66 \text{ W}$ and $W_2 = 1429.7 \text{ W}$
- d) $W_1 = 1429.7 \text{ W}$ and $W_2 = 565.66 \text{ W}$
- e) None of the above is correct

