

# King Fahd University of Petroleum and Minerals

Department of Electrical Engineering  
EE 205 Circuit II,

Major Exam II  
Saturday, 23 May 2009  
6:45 - 8:45 PM

Name: KEY

ID: 000

Serial #: \_\_\_\_\_

Section: \_\_\_\_\_

Instructor: \_\_\_\_\_

Problem	Score	Out of
1		14
2		10
3		10
4		14
Total		48

Good luck,

Dr. Samir Al-Ghadhban, Dr. AbdelMalek Zidouri, Dr. Adnan Al-Andalusi, and Dr. Ali Muqaibel

Grading Guideline

- 1 point for the relation
  - 1 point for the final answer
- (2 points)

**Problem 1: [14 points]**

A. Two parallel RLC Circuits have the same resonant frequency

Circuit 1: has quality factor,  $Q_1 = 30$ ,  $BW_1 = 10$  kHz

Circuit 2: has quality factor,  $Q_2 = 20$ ,  $BW_2 = ?$  Find the unknown bandwidth

$Q = \frac{\omega_r}{BW} \Rightarrow \omega_r = Q \cdot BW$  Since the two circuit have the same resonance frequency  $\omega_{r1} = \omega_{r2} \Rightarrow$

$Q_1 \cdot BW_1 = Q_2 \cdot BW_2 \Rightarrow BW_2 = \frac{Q_1 \cdot BW_1}{Q_2} = \frac{30}{20} \cdot 10 \text{ kHz} = \boxed{15 \text{ kHz}}$

B. Find the resonance frequency for the given circuit in Hz,

Let  $L=1$  H,  $C=10.13$  pF,  $R_1=3$  Ohms,  $R_2=2$  Ohms.

Low or No credit if you do not explain your steps

(6 points)

$Z_1$  is made of  $R_2 \parallel L$  1 point

$Z_1 = \frac{j\omega L R_2}{j\omega L + R_2} = \frac{j2\omega}{j\omega + 2}$   
 ↗ substitute  $R_2 = L$

$Z_2$  is made up of  $Z_1 + R_1$  1 point

$Z_2 = R_1 + \frac{j2\omega}{j\omega + 2}$

$= 3 + \frac{j2\omega}{j\omega + 2} = \frac{3j\omega + 6 + j2\omega}{j\omega + 2}$

$= \frac{6 + j5\omega}{2 + j\omega}$


$Y_2 = \frac{1}{Z_2} = \frac{2 + j\omega}{6 + j5\omega}$  1 point

$Y_{total}$  is made up of  $Y_2 \parallel C$

$Y_{total} = j\omega C + \frac{2 + j\omega}{6 + j5\omega} \cdot \frac{6 - j5\omega}{6 - j5\omega}$

multiply by the conjugate

1 point for the final Expression

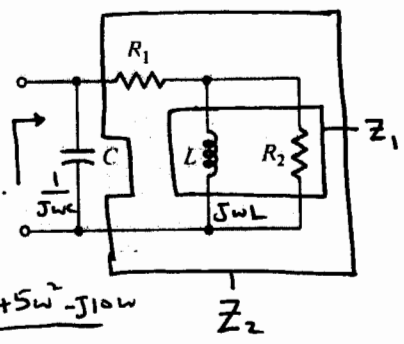

$Y_{total} = j\omega C + \frac{j6\omega + 12 + 5\omega^2 - j10\omega}{25\omega^2 + 36}$

to find the resonance frequency 0.5 p

Imaginary ( $Y_{total}$ ) = 0  $\omega = \omega_r$

$\frac{4}{C} + \frac{6\omega_r - 10\omega_r}{25\omega_r^2 + 36} = 0$

divid by ( $\omega_r \neq 0$ )

$C - \frac{4}{25\omega_r^2 + 36} = 0$  1 point

$\Rightarrow 25\omega_r^2 + 36 = \frac{4}{C}$

$\Rightarrow \omega_r^2 = \frac{1}{25} \left( \frac{4}{C} - 36 \right)$

$\omega_r = \frac{1}{5} \sqrt{\frac{4}{C} - 36} = 125.62 \text{ k rad/sec}$


$f_r = \frac{\omega_r}{2\pi} = 20 \text{ kHz} = 20,000 \text{ Hz}$

0.5 point

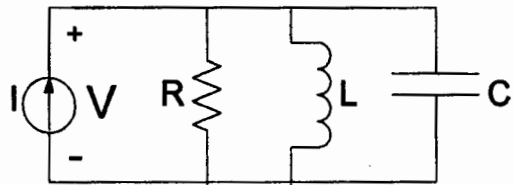1.C

Show that the Quality factor at resonance of the parallel RLC circuit is equal to  $Q = \omega_r RC$ ,

hint  $\left( Q = 2\pi \frac{[w_C(t) + w_L(t)]_{\max}}{P_R T} \right)$  (6 points)



No credit if you do not explain your steps

Let  $i(t) = I \cos \omega_r t$

then the Parallel Voltage is

①  $v(t) = R i(t) = R I \cos \omega_r t$

Thus, the energy stored in the capacitor is

$w_C(t) = \frac{1}{2} C v^2(t)$   
 $= \frac{1}{2} C R^2 I^2 \cos^2 \omega_r t$

The inductor current is

$I_L = \frac{R I \angle 0^\circ}{\omega_r L \angle 90^\circ} = \frac{R I}{\omega_r L} \angle -90^\circ$

$\Rightarrow i_L(t) = \frac{R I}{\omega_r L} \cos(\omega_r t - 90^\circ)$

①  $= \frac{R I}{\omega_r L} \sin \omega_r t$

$\Rightarrow$  Energy stored in the inductor is  $\frac{1}{2} L i^2$

$w_L(t) = \frac{1}{2} C R^2 I^2 \sin^2 \omega_r t$

$w_C(t) + w_L(t) = \frac{1}{2} C R^2 I^2 \cos^2 \omega_r t + \frac{1}{2} C R^2 I^2 \sin^2 \omega_r t$

①  $[w_C(t) + w_L(t)]_{\max} = \frac{1}{2} C R^2 I^2$

The power absorbed by the resistor is

$P_R = \frac{1}{2} R I^2$

$\Rightarrow P_R T = \frac{1}{2} I^2 R T$   
 $= \frac{1}{2} I^2 R \left( \frac{2\pi}{\omega_r} \right)$

$= \frac{\pi I^2 R}{\omega_r}$

$Q = \frac{2\pi \left( \frac{1}{2} C R^2 I^2 \right)}{\pi I^2 R / \omega_r}$


$Q = \omega_r R C$

Grading Guidelines

- 1 p: Voltage on the capacitor.
- 0.5 p: Energy on " "
- 1 p: Current on the coil.
- 0.5 p: Energy stored in the coil.
- 1 p: max Energy stored.
- 1 p: Power dissipated in a period in R.
- 1 p: Simplifying Q to the required expression.

### Problem 2: [10 points]

Consider the following circuit:

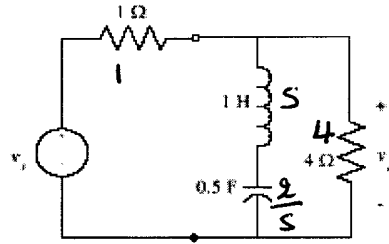

- a) Find the expression of the transfer function  $V_o(s)/V_s(s)$  [4 points]

$$\frac{V_o}{V_s} = \frac{4 \parallel (s + \frac{2}{s})}{1 + \{4 \parallel (s + \frac{2}{s})\}}$$

$$= \frac{4 \times (s + 2/s)}{4 + s + 2/s}$$

$$= \frac{4 \times (s + 2/s)}{4 + s + 2/s}$$

1 pt

$$\frac{V_o}{V_s} = \frac{4s^2 + 8}{5s^2 + 4s + 10}$$


3 pt

- b) Find the poles and zeros of this transfer function, and give their plot in the complex s-plane (use appropriate notation) [2 points]

Zeros:  $4s^2 + 8 = 0 \rightarrow s = \pm j\sqrt{2}$  0.5 pt

poles:  $5s^2 + 4s + 10 = 0 \rightarrow s = -0.4 \pm j1.356$

natural 0.5 pt

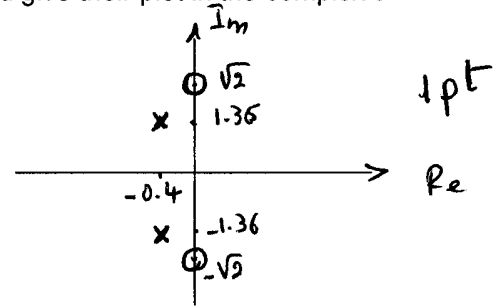

- c) What is the type of the response in the time domain? [1 points]

decaying (damped) sin of the form  $A_1 e^{(-0.4 + j1.36)t} + A_2 e^{(-0.4 - j1.36)t}$  or  $B_1 e^{-0.4t} \cos(1.36t) + B_2 e^{-0.4t} \sin(1.36t)$   
 ↳ stable!

- d) Suppose the input voltage is  $v_s(t) = 10e^{-t} \cos(2t + 30^\circ) V$ . Find the step forced steady state output response  $v_o(t)$ . [3 points]

$$v_s(t) = 10e^{-t} \cos(2t + 30^\circ) \rightarrow V_s = 10 \angle 30^\circ$$

0.25 pt

$$s = -1 + 2j$$

0.25 pt

$$V_o = \frac{4(-1 + 2j)^2 + 8}{5(-1 + 2j)^2 + 4(-1 + 2j) + 10} \times 10 \angle 30^\circ$$

$$= \frac{-4 - 16j}{-9 - 12j} \times 10 \angle 30^\circ$$

$$\approx 1.1 \angle 22.8^\circ \times 10 \angle 30^\circ$$

$$\Rightarrow v_o(t) = 11 \cos(2t + 52.8^\circ)$$

0.5 pt

# Solution

## Problem 3: [10 points]

For the transformer in the figure,

$L_1 = 25 \text{ mH}$  and  $L_2 = 100 \text{ mH}$ .

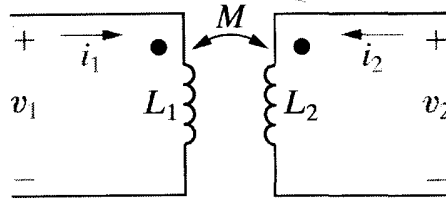


Figure 06-30  
Copyright © 2008 Pearson Prentice Hall, Inc.

### 3.1 If the coefficient of coupling ( $k$ ) is equal to 0.8,

a) Find the mutual inductance  $M$  [1 point]

$$M = k\sqrt{L_1 L_2} = 0.5$$

$$M = 0.8\sqrt{(0.025)(0.1)} = 40 \text{ mH} \quad \text{---} \quad 0.5$$

b) Find the turn ratio  $N_2/N_1$ , assuming that the two coils have the same permeance. [1 point]

$$0.5 \left[ \begin{array}{l} L_1 = \mu N_1^2 \\ L_2 = \mu N_2^2 \end{array} \right] \quad \text{Since } \mu_1 = \mu_2 \Rightarrow \frac{L_2}{L_1} = \frac{N_2^2}{N_1^2} \Rightarrow \frac{N_2}{N_1} = \sqrt{\frac{L_2}{L_1}} = \sqrt{\frac{100}{25}} = 2$$

c) Find the energy stored in the system when  $i_1 = -10 \text{ A}$ ,  $i_2 = 15 \text{ A}$  [3 point]

$$\textcircled{1} \quad W = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

$$= \frac{1}{2}(0.025)(-10)^2 + \frac{1}{2}(0.1)(15)^2 + (0.04)(-10)(15) = \frac{6.5 \text{ J}}{\textcircled{1}}$$

3.2 Find the value of  $k$  that makes the mutual inductance  $M = 112 \text{ mH}$  (justify your answer) [2 point]

$$M = k\sqrt{L_1 L_2} = k(50) \text{ mH} \Rightarrow k \text{ should be } 2.24$$

However since  $0 \leq k \leq 1 \Rightarrow$  we can't have a mutual inductance = 112 mH

3.3 If the coefficient of coupling ( $k$ ) is equal to 1 and if  $i_1 = 10 \text{ A}$ , find the value of  $i_2$  that makes the energy stored in the systems equals zero. [3 point]

$$\text{when } k=1 \Rightarrow M = \sqrt{(0.025)(0.1)} = 50 \text{ mH}, i_1 = 10 \text{ A}$$

$$\textcircled{1} \Rightarrow 50 i_2^2 + 500 i_2 + 1250 = 0$$

$$\Rightarrow i_2^2 + 10 i_2 + 25 = 0$$

$$\Rightarrow i_2 = \frac{-10 \pm \sqrt{10^2 - 4(25)}}{2}$$


$$\textcircled{1} \quad \boxed{i_2 = -5 \text{ A}}$$

### Problem 4: [14 Points]

For the circuit shown in the Figure,

Let  $Z_1 = 60 - j100 \Omega$ ,  $Z_2 = 30 + j40 \Omega$ ,

and  $Z_L = 80 + j60 \Omega$ ,

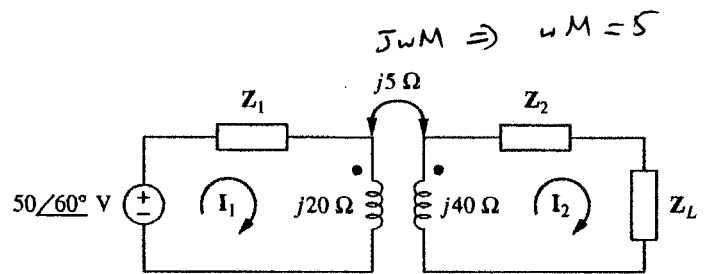

A. Calculate the impedance seen by the ideal source  $\left( Z_{int} = \frac{V_s}{I_1} \right)$  [3 points]

We can do (B) first

$$\begin{aligned} Z_{int} &= Z_1 + j20 + Z_r \\ &= 60 - j100 + j20 + Z_r \\ &= 60 - j80 + 0.0868 - j0.114 \\ &= 60.0868 - j80.114 \end{aligned}$$

B. Find the reflected Impedance ( $Z_r$ ) as seen from the primary side. [3 points]

$$Z_r = \frac{\omega^2 M^2}{|Z_{22}|} Z_{22}^* \quad , \quad \omega M = 5$$

$$\begin{aligned} Z_r &= \frac{(5)^2}{31700} (110 - j140) \\ &= 0.0868 - j0.114 \Omega \\ &= \end{aligned}$$

$$\begin{aligned} Z_{22} &= 30 + j40 + 80 + j60 + j40 \\ &= 110 + j140 \\ &= 178.05 \angle 51.843^\circ \end{aligned}$$

Note:  $Z_r$  little impedance is reflected.  
This due to the low mutual Inductance  $j5$  relatively.

C. Find the mesh currents  $I_1$  and  $I_2$ . [4 points]

$$\begin{aligned} I_1 &= \frac{V_s}{Z_{int}} = \frac{50 \angle 60^\circ}{Z_{int}} \\ &= 0.499 \angle 113.13^\circ \text{ A} \end{aligned}$$

By KVL at loop "secondary".

$$I_2 Z_{22} - j5 I_1 = 0$$

$$\Rightarrow I_1 = \frac{I_2 Z_{22}}{j5}$$

$$I_2 = \frac{j5 I_1}{Z_{22}} = \frac{5 \angle 19^\circ I_1}{178.05 \angle 51.843^\circ}$$

$$= 0.014 \angle 151.287^\circ \text{ A}$$

C. Calculate the power consumed by the load  $Z_L$ . [2 points]

Assuming the given voltage is RMS. | if the given voltage is amplitude

$$I^2 R = (0.014)^2 (80) \\ = 15.68 * 10^{-3} \text{ Watts}$$

$$P = \frac{1}{2} I^2 R \\ = \frac{1}{2} I^2 R = 7.84 * 10^{-3} \text{ Watts}$$

D. If the given circuit is shown for a radian frequency of 5 rad/sec, find the mutual inductance ( $M$ ) and the coupling coefficient ( $k$ ). [2 points]

$$j\omega M = j 5$$

$$\Rightarrow \omega M = 5 \Rightarrow M = \frac{5}{5} = 1 \text{ H}$$

$$\text{Similarly } j\omega L_1 = j 20 \Rightarrow L_1 = 4 \text{ H}$$

$$j\omega L_2 = j 40 \Rightarrow L_2 = 8 \text{ H}$$

$$M = k \sqrt{L_1 L_2} \Rightarrow k = \frac{1}{\sqrt{4 \cdot 8}} = 0.1768$$