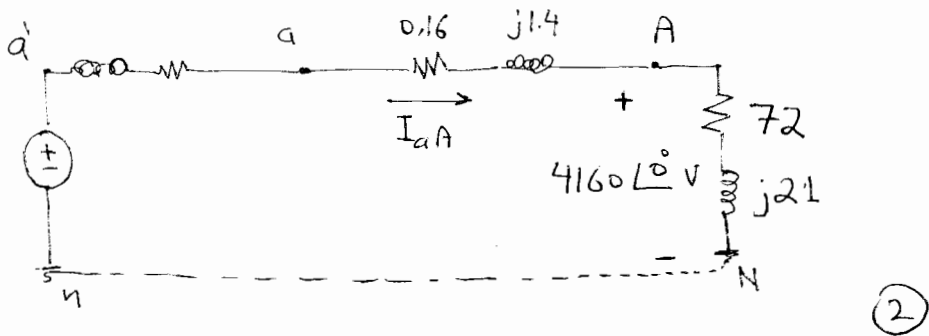


Name: KEY

The phase voltage at a balanced Y-connected three-phase load is 4,160 V. The load impedance is $72+j21 \Omega/\emptyset$. The load is fed from a line that has an impedance of $0.16+j1.4 \Omega/\emptyset$. Use a-phase voltage at the load as a reference.

a) Construct a single phase equivalent circuit. (Show all the known details) (2 points)



b) If the sequence is positive, find the three line-voltages at the source, and illustrate them on the phasor diagram?

$$\vec{I}_{aA} = \frac{4160 \angle 0^\circ}{72 + j21} = 55.47 \angle -16.26^\circ \text{ A} \quad (2)$$

$$\begin{aligned} \vec{V}_{an} &= \vec{I}_{aA} (0.16 + j1.4 + 72 + j21) \\ &= \vec{I}_{aA} (72.16 + j22.4) \\ &= 4190.88 \angle 0.99^\circ \quad (2) \end{aligned}$$

$$\vec{V}_{ab} = \sqrt{3} \vec{V}_{an} \angle 30^\circ = 7258.82 \angle 30.99^\circ \quad (1.5)$$

$$\begin{aligned} \Rightarrow \vec{V}_{bc} &= 7258.82 \angle -89.01^\circ \text{ V} \\ \vec{V}_{ca} &= 7258.82 \angle 150.99^\circ \text{ V} \quad (1) \end{aligned}$$

