

**King Fahd University of Petroleum & Minerals**  
 Electrical Engineering Department  
 EE205: Electric Circuit II (082)  
**Quiz 1: Balanced Three Phase Y-Connected Systems**

**Serial #**  
 0  
 - 1 points for not writing your serial number

Name: KEY

Ver. 1

The magnitude of the line voltage at the terminals of a balanced Y-connected load is 12,800 V. The load impedance is  $216 + j63 \Omega/\emptyset$ . The load is fed from a line that has an impedance of  $0.25 + j2 \Omega/\emptyset$ . Assume the sequence is negative.

a) If  $V_{AB}$  is the reference voltage, what is  $V_{BC}$  and  $V_{CA}$

$$V_{AB} = 12,800 \angle 0^\circ \text{ V}, \quad V_{BC} = 12,800 \angle 120^\circ, \quad V_{CA} = 12,800 \angle -120^\circ$$


b) Find  $V_{AN}$ .

$$V_{AB} = \sqrt{3} V_{AN} \angle -30^\circ$$

$$\Rightarrow V_{AN} = \frac{V_{AB} \angle 30^\circ}{\sqrt{3}} = \frac{12,800 \angle 30^\circ}{\sqrt{3}} = \boxed{7390.08 \angle 30^\circ \text{ V}}$$

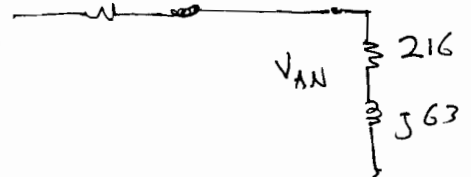c) What is the magnitude of the line current?

$$I_{aA} = \frac{V_{AN}}{216 + j63} = \frac{12,800/\sqrt{3} \angle 30^\circ}{216 + j63}$$



$$\boxed{|I_{aA}| = 32.845 \text{ A}}$$

d) What is the magnitude of the line voltage at the source?

$$|V_{aA}| = |I_{aA} (216 + j63 + 0.25 + j2)| = 7416.61 \text{ V}$$

$$|V_{ab}| = \sqrt{3} |V_{aA}| = \boxed{12,845.94 \text{ V}}$$