

**King Fahd University of Petroleum & Minerals**  
 Electrical Engineering Department  
 EE205: Electric Circuit II (082)  
**Quiz 1: Balanced Three Phase Y-Connected Systems**

**Serial #**  
 ○  
 - 1 points for not writing your serial number

Name: KEY

Ver. 2

The magnitude of the line voltage at the terminals of a balanced Y-connected load is 12,800 V. The load impedance is  $216+j63 \Omega/\emptyset$ . The load is fed from a line that has an impedance of  $0.25+j2 \Omega/\emptyset$ . Assume the sequence is positive.

a) If  $V_{AB}$  is the reference voltage, what is  $V_{BC}$  and  $V_{CA}$

$$V_{AB} = 12,800 \text{ V } \angle 0^\circ \Rightarrow \begin{cases} V_{BC} = 12,800 \angle -120^\circ \text{ V} \\ V_{CA} = 12,800 \angle +120^\circ \text{ V} \end{cases} \quad (2)$$

b) Find  $V_{AN}$ .


$$\vec{V}_{AB} = \sqrt{3} \vec{V}_{AN} \angle 30^\circ \Rightarrow \vec{V}_{AN} = \frac{\vec{V}_{AB}}{\sqrt{3}} \angle -30^\circ = \frac{12,800}{\sqrt{3}} \angle -30^\circ$$

$$\boxed{\vec{V}_{AN} = 7390.08 \angle -30^\circ} \quad (2)$$

c) What is the magnitude of the line current?

$$I_{aA} = \left| \frac{V_{AN}}{216+j63} \right| = \left| \frac{12,800 \angle -30^\circ}{(\sqrt{3})(216+j63)} \right| \checkmark$$

$$\boxed{|I_{aA}| = 32.845 \text{ A}} \quad (2)$$

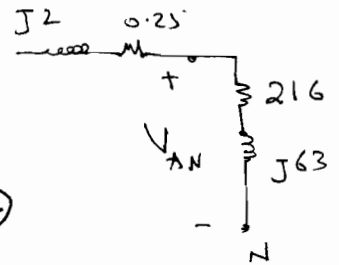

d) What is the magnitude of the line voltage at the source?

$$|V_{an}| = |I_{aA} (j2 + 0.25 + 216 + j63)| \quad (2)$$

$$= |I_{aA} (216.25 + j65)| = 7416.61 \text{ V}$$

$$|V_{ab}| = |\sqrt{3} V_{an} \angle 30^\circ| = \sqrt{3} |V_{an}| \quad (1)$$

$$\boxed{|V_{ab}| = 12,845.94 \text{ V}}$$