


Quiz 2 (Take Home): Balanced 3 Phase Systems 11.4-11.6

Name: KEY "corrected" Sec.

Two balanced three-phase Δ -connected loads are connected in parallel. Load 1 has an impedance per phase of $750+j 240 \Omega/\emptyset$; and load 2 is $112.32+j 95.04 \text{ kVA}$ (hint: load 2 is represented by its 3-phase complex power). The loads are fed from a distribution line with an impedance of $X+j 5 \Omega/\emptyset$. The magnitude of the phase voltage at the load end of the line is 7.2kV. The a-phase voltage at the load is specified as the reference phasor. Assume positive sequence. The total complex power at the sending end of the line is $683419+j 292716 \text{ VA}$

Find the value of X?

Single Phase Equivalent Circuit

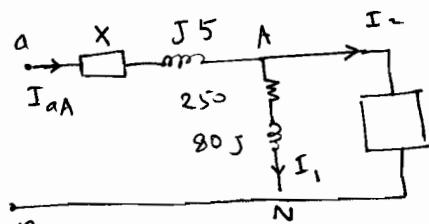

To convert load 1 $\Delta \rightarrow Y$

$$Z_Y = \frac{Z_\Delta}{3} = \frac{750 + j 240}{3} = 250 + j 80$$

Load 2. The perphase S_d

$$S_{d\phi} = \frac{S_{T_d}}{3} = \frac{112.32 + j 95.04}{3} \text{ k} \\ = 37.44 + j 31.68 \text{ kVA}$$

We need I_1 & I_2

$$I_1 = \frac{(7200/\sqrt{3}) [-30^\circ]}{250 + j 80} \\ = 15.83 [-47.75^\circ]$$

for I_2 (in the equivalent Y)

$$S_d = V I_2^* \Rightarrow I_2^*$$

$$\frac{37.44 + j 31.68}{7200/\sqrt{3} [-30^\circ]} = I_2^*$$

$$I_2 = 11.798 [-70.24^\circ]$$

$$\frac{1}{aA} = I_1 + I_2 = 27.11 [-57.32^\circ]$$

Total sent power per phase

$$S_{d\text{send}} = \frac{S_{T\text{send}}}{3}$$

$$= 227206.33 + j 97572$$

$$V_{an} = 9139.68 [-34.13^\circ]$$

$$S = \sqrt{I_{aA}^* V_{an}}$$

V_{an} (voltage drop across the line)

$$= V_{an} - V_{AN}$$

$$= 9139.68 [-34.13^\circ] - \frac{7200}{\sqrt{3}} [-30^\circ]$$

$$= 5002.56 [-37.56^\circ]$$

$$Z_L = \frac{V_{an}}{I_{aA}} = 173.64 + j 62.3$$

$$Z_L = X + j 5 = 173.64 + j 62.3$$

$$\Rightarrow X = 173.64 + j 57.3$$

X is not pure resistive

The use of R was confusing.

$$R + j 5 = X + j 5$$

I have not given nor received any help in solving this quiz

Sign