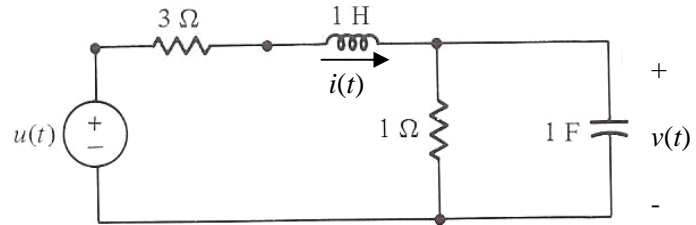



Name: **Key**

ver.

For the circuit in the figure, write the matrix state equation. Clearly state your steps (KVL on loop..., KCL at node....). No or low grade will be given for not detailing the procedure.



There are two state variables

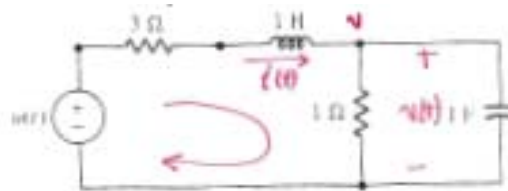

By KCL @ node v:

$$i(t) = \frac{v(t)}{1} + 1 \frac{dv(t)}{dt}$$

rewrite:

$$\frac{dv(t)}{dt} = -v(t) + i(t) = i(t) - v(t) \quad \text{---(1)}$$

By KVL in the left hand loop.

$$-v_s(t) + 3i(t) + 1 \frac{di(t)}{dt} + v(t) = 0$$

$$\frac{di(t)}{dt} = -3i(t) - v(t) + v_s(t) \quad \text{---(2)}$$

$$\frac{d}{dt} \begin{bmatrix} i(t) \\ v(t) \end{bmatrix} = \begin{bmatrix} -3 & -1 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} i(t) \\ v(t) \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} u(t)$$

$v_s(t) = u(t)$   
from

↗ it is possible to start with the voltage & permute the rows.