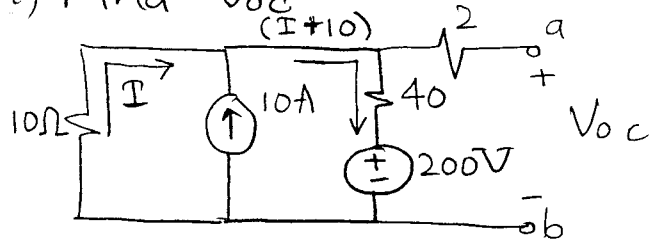


Q1. Find voltage V_{ab} when $R_o = 0, 2, 10, 20, 30, 40, 50\Omega$.

(8 marks)

Since R_o is variable, the best way is to change the circuit to thevenin eq.

i) Find V_{oc}



Apply KVL in the big loop

$$10I + (I+10)40 + 200 = 0$$

$$\Rightarrow 50I + 400 + 200 = 0$$

$$\Rightarrow I = -12A$$


$$V_{oc} = V_{40\Omega} + 200$$

$$= (10+I)40 + 200$$

$$= (10-12)40 + 200$$

$$\Rightarrow V_{oc} = 120V$$



ii) Find R_{th}

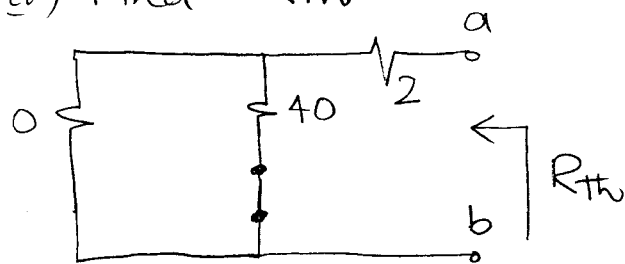

$$R_{th} = [10 // 40] + 2$$

$$= \frac{10 \times 40}{10 + 40} + 2 =$$

$$R_{th} = 10\Omega$$

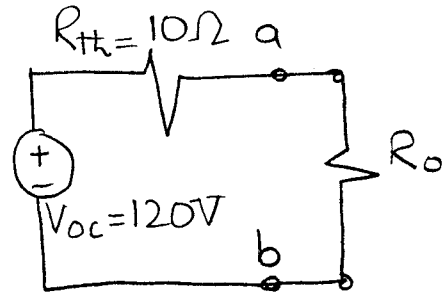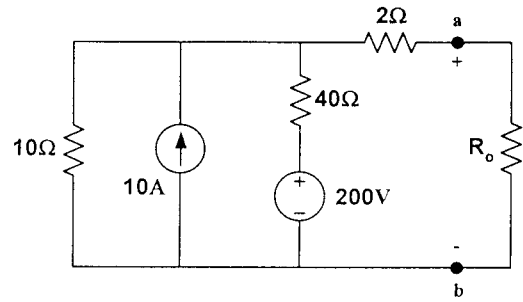

$$\therefore V_{ab} = \frac{R_o}{R_{th} + R_o} \times V_{oc}$$

When $R_o = 0\Omega$

$$V_{ab} = \frac{0}{10+0} \times 120 = 0V$$

When $R_o = 2\Omega$

$$V_{ab} = \frac{2}{10+2} \times 120 = 20V$$

and so on.

Q2. For the following circuit,

(a) Write mesh equations using mesh analysis.

(4 marks)

(b) Solve the equations to find mesh currents.

(1 marks)

(c) Find total power delivered to the circuit.

(3 marks)

a)

$$\boxed{I_3 = 40A}$$

I_1

$$-400 + 5I_1 + 10(I_1 - I_2) + 5(I_1 - I_3) = 0$$

$$\Rightarrow -400 + 5I_1 + 10I_1 - 10I_2 + 5I_1 - 200 = 0$$

$$\Rightarrow 20I_1 - 10I_2 = 600 \quad \text{--- (1)}$$

I_2

$$200 + 15(I_2 - I_3) + 10(I_2 - I_1) + 15I_2 = 0$$

$$\Rightarrow 200 + 15I_2 - 600 + 10I_2 - 10I_1 + 15I_2 = 0$$

$$\Rightarrow -10I_1 + 40I_2 = 400 \quad \text{--- (2)}$$

$$\textcircled{1} \times 1 \Rightarrow 20I_1 - 10I_2 = 600$$

$$\textcircled{2} \times 2 \Rightarrow -20I_1 + 80I_2 = 800$$

$$\hline 70I_2 = 1400$$

$$\Rightarrow \boxed{I_2 = 20A}$$


$$\therefore \textcircled{1} \Rightarrow I_1 = \frac{600 + 10(20)}{20}$$

$$\Rightarrow \boxed{I_1 = 40A}$$

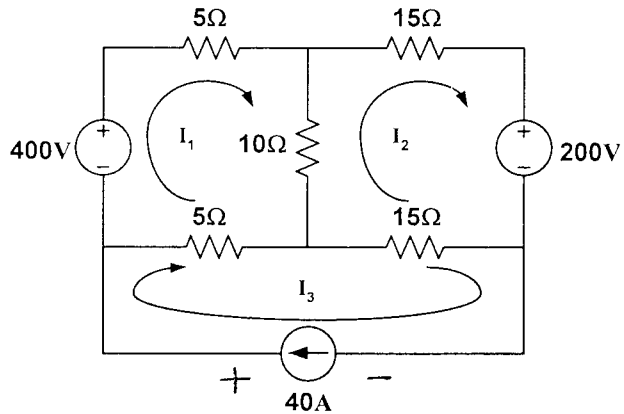b) Since we need power delivered and resistors absorb power \therefore we need to calculate power of sources only.

$$P_{400V} = -(400)(I_1) = -16000W \text{ (delivered)}$$

$$P_{200V} = +(200)(I_2) = +4000W \text{ (absorbed)}$$



To calculate power of 40A we need voltage across it. Apply KVL in outer loop.

$$-V_{40A} - 400 + 5I_1 + 15I_2 + 200 = 0$$

$$\Rightarrow V_{40A} = 300V$$

$$\therefore P_{40A} = -(300)(I_3) = -12000W \text{ (delivered)}$$

\therefore total power delivered to the circuit is

$$P_{\text{delivered}} = 16000 + 12000 = 28000W$$

- Q3. For the following circuit
 (a) Write nodal equations using nodal analysis.
 (b) Solve the equations to find node voltages
 (c) Find current I_x and voltage V_x .

(5 marks)
 (1 marks)
 (3 marks)

① Apply supernode at V_1, V_2

$$\frac{V_2}{2} + \frac{V_2 - 6}{5} + \frac{V_1}{4} + \frac{V_1 - 6}{1} = 0$$

$$\Rightarrow 10V_2 + 4V_2 - 24 + 5V_1 + 20V_1 - 120 = 0$$

$$\Rightarrow 25V_1 + 14V_2 = 144 \quad \text{--- ①}$$

Also $V_1 - V_2 = 12 \quad \text{--- ②}$

$$\text{Dx 1} \Rightarrow 25V_1 + 14V_2 = 144$$

$$\text{Dx 25} \Rightarrow 25V_1 - 25V_2 = 300$$

$$\hline 39V_2 = -156$$

$$\Rightarrow V_2 = -4.0 \text{ V}$$

$$\text{②} \Rightarrow V_1 = 12 + V_2$$

$$\Rightarrow V_1 = +8.0 \text{ V}$$

$$\text{③} V_x = 6 - V_1$$


$$\Rightarrow V_x = -2.0 \text{ V}$$

To find I_x apply KCL at 6V node:


$$\frac{6 - V_2}{5} + \frac{6}{4} + I_x + \frac{6 - V_1}{1} = 0$$

$$\Rightarrow 1.2 + 1.5 + I_x + (-2.0) = 0$$

$$\Rightarrow I_x = -1.5 \text{ A}$$

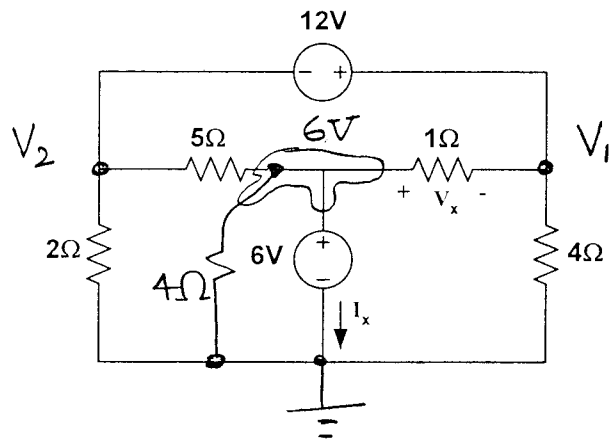

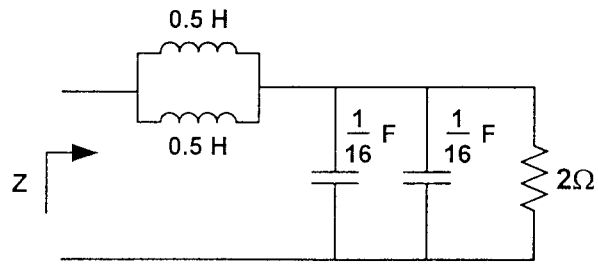Q4. For the following RLC circuit, find total impedance Z when $\omega = 4$ rad/sec. (5 marks)




Combine inductors in parallel

$$L_{eq} = \frac{0.5 \times 0.5}{0.5 + 0.5} = 0.25 \text{ H}$$

Combine capacitors in parallel
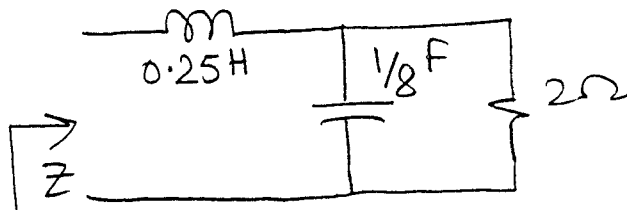
$$C_{eq} = \frac{1}{16} + \frac{1}{16} = \frac{1}{8} \text{ F}$$




Change to Impedance

$$Z_L = j\omega L = j2 \dots$$

$$Z_C = \frac{-j}{\omega C} = -j2 \Omega$$

$$Z_R = R = 2 \Omega$$

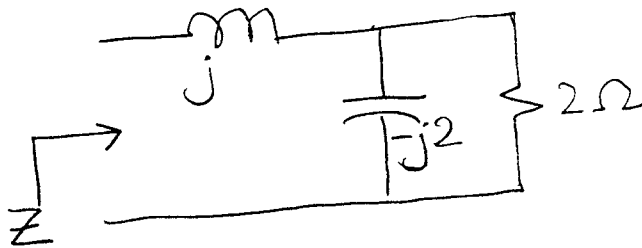

$$Z = \frac{(2)(-j2)}{(2) + (-j2)} + j$$

$$Z = \frac{-4j}{2 - j2} + j$$

$$\Rightarrow Z = \frac{4 \angle -90^\circ}{2.83 \angle 45^\circ} + j = 1.413 \angle -45^\circ + j$$

$$= 1 - j + j = 1 \Omega$$