

EE 204 Fundamentals of Electric Circuits Quiz 1 Solution (Sample Quiz)

ID# KFY

Quiz #2

EE 204-031


Section _____

Name _____

Q

a) Find i_1, i_2, i_3

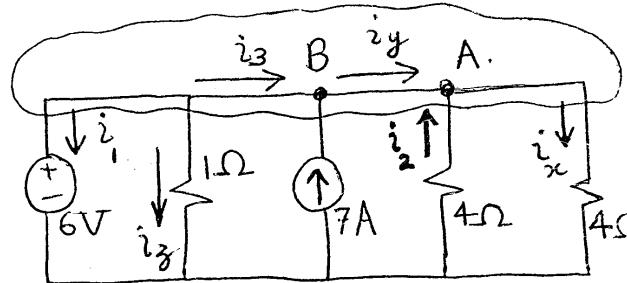b) Find power dissipation of 1Ω resistor and power of $6V$ source. Indicate if power is absorbed or delivered.



a) Since $6V$ source is in parallel to the resistors $\therefore i_2 = -\frac{6}{4} = -\frac{3}{2} = -1.5A$

$$i_x = +\frac{6}{4} = +\frac{3}{2} = +1.5A.$$

Apply KCL at A.

$$i_y + i_2 = i_x \Rightarrow i_y = 3A$$

Apply KCL at B

$$i_3 + 7 = i_y \Rightarrow i_3 = -4A$$

Apply KCL at big node.

$$i_1 + i_3 + i_x = i_2 + 7 \Rightarrow i_1 = -1.5 + 7 - 1.5 - (-4) = 4A$$

$$\Rightarrow i_1 = 4 - 7 = -3A \Rightarrow i_1 = 4 - \frac{6}{1} = -2 \Rightarrow i_1 = -2A$$

b) $P_{1\Omega} = (i_3)^2 R = (6)^2 \times 1 = +36W$ absorbed

$$P_{6V} = +VI_1 = +(6)(-2) = -12W$$
 delivered