



Answers to Selected Problems

Chapter 1

- 1.1 8.85 ms
 1.3 38 m/s
 1.5 $361.934 \mu\text{m}^2$
 1.7 0.962 aJ
 1.9 6480 J
 1.11 a) 400 W, delivering
 b) Entering
 c) Gain
 1.15 a) 3.1 mW
 b) $1.24 \mu\text{J}$
 c) $21.67 \mu\text{J}$
 1.18 a) 0.5 W
 b) 2 mJ
 1.21 a) 1.68 ms
 b) 666 mW
 c) 2.97 mJ
 1.26 1740 W

Chapter 2

- 2.3 yes; 720 W
 2.8 2240 W
 2.11 a) 4 A
 b) 144 V
 c) 768 W

- 2.16 a) 2 A
 b) $p_{5\Omega} = 320 \text{ W}$; $p_{25\Omega} = 400 \text{ W}$; $p_{70\Omega} = 280 \text{ W}$;
 $p_{10\Omega} = 360 \text{ W}$; $p_{8\Omega} = 800 \text{ W}$
 c) 2160 W
 2.21 a) 60Ω
 b) 2000 W
 2.26 a) 0 A
 b) -60 mA
 c) -240 mA
 2.29 $v_1 = -50 \text{ mV}$; $v_g = 6.25 \text{ mV}$

Chapter 3

- 3.3 80 W
 3.6 a) 16Ω
 b) 6Ω
 3.10 33.75 kV
 3.13 $i_g = 12.5 \text{ A}$; $i_o = 2 \text{ A}$
 3.16 26.67Ω
 3.20 a) 66 V
 b) $P_{R_1} = 1.88 \text{ W}$; $P_{R_2} = 1.32 \text{ W}$
 c) $R_1 = 17,672 \Omega$; $R_2 = 12,408 \Omega$
 3.26 $v_x = 16 \text{ V}$; $P = 75.2 \text{ W}$
 3.32 -0.1664%
 3.36 -27.03%
 3.46 300 mW

1012 ■ ANSWERS TO SELECTED PROBLEMS

- 3.51 $2 \text{ k}\Omega$
 3.54 a) 120Ω
 b) 60 W
 3.56 a) 4 A
 b) 1.1 A
 c) 6 V
 d) 2500 W

Chapter 4

- 4.2 40 W (absorbing)
 4.5 10 V
 4.9 $v_1 = 100 \text{ V}; v_2 = 20 \text{ V}$
 4.13 1 A
 4.17 a) 2000 W
 b) $35,000 \text{ W}$
 4.20 26 V
 4.26 602.5 W
 4.30 a) $i_a = 9.8 \text{ A}; i_b = -0.2 \text{ A}; i_c = -10 \text{ A}$
 b) $i_a = -1.72 \text{ A}; i_b = 1.08 \text{ A}; i_c = 2.8 \text{ A}$
 4.33 a) -1.0 mA
 b) 8.5 mW
 c) 0.225 mW
 4.35 98 W
 4.38 600 W
 4.44 2 A
 4.51 a) 3 mA
 b) 345 mW
 4.54 a) 1 A
 b) 1 A
 4.56 $v_{\text{Th}} = 48 \text{ V}; R_{\text{Th}} = 16 \Omega$
 4.59 $v_{\text{Th}} = 52 \text{ V}; R_{\text{Th}} = 6 \Omega$
 4.62 $i_{\text{N}} = 8 \text{ mA}; R_{\text{N}} = 10 \text{ k}\Omega$
 4.65 a) $150 \text{ k}\Omega$
 b) -1.56%
 4.69 $v_{\text{Th}} = 0 \text{ V}; R_{\text{Th}} = 18.75 \Omega$
 4.74 $R_o = 2.5 \Omega, 22.5 \Omega$
 4.77 a) 2.5Ω
 b) 2250 W
 4.80 3.77%
 4.82 a) 35Ω
 b) 505.4 W
 c) $21,364 \text{ W}$
 4.84 25 V
 4.87 $i_o = 2 \text{ A}; v_o = -136 \text{ V}$
 4.90 a) 4 A
 b) 160 W
 4.96 40 W
 4.98 0 A
 4.101 $v_1 = 37.5 \text{ V}; v_2 = 105 \text{ V}$

Chapter 5

- 5.2 $-200 \mu\text{A}$
 5.4 a) -400 mV
 b) -6.8 V
 c) $20 \mu\text{A}$
 d) $111.67 \mu\text{A}$
 5.6 -3.1 mA
 5.8 a) $0 \leq \sigma < 0.2$
 b) $200 \mu\text{A}$
 5.11 a) $415.38 \text{ k}\Omega$
 b) $650.37 \mu\text{A}$
 5.13 $0 \leq R_f \leq 75 \text{ k}\Omega$
 5.17 a) $108 \text{ k}\Omega$
 b) $270 \mu\text{W}$
 5.22 a) 7.56 V
 b) $-3.97 \leq v_g \leq 3.97 \text{ V}$
 c) $35 \text{ k}\Omega$
 5.26 a) 56.3 mV
 b) $114.3 \text{ k}\Omega$
 c) $80 \text{ k}\Omega$
 5.29 $R_b = 1200 \Omega; R_f = 2000 \Omega$
 5.33 $v_{o1} = 15.85 \text{ V}; v_{o2} = 13.6 \text{ V}$

- 5.40 a) -39.997
 b) $4.02 \mu\text{V}$
 c) 8000.644Ω
 d) $v_o/v_g = -40$; $v_n = 0 \text{ V}$; $R_g = 8000 \Omega$
- 5.42 $23.89 \text{ k}\Omega$

Chapter 6

- 6.3 a) $100e^{-10t}(1 - 10t) \text{ mV}$
 b) -18.32 mW
 c) delivering
 d) 1.83 mJ
 e) 3.38 mJ
- 6.5 a) $i = 0,$ $t < 0$
 $i = 16t,$ $0 \leq t \leq 25 \text{ ms}$
 $i = 0.8 - 16t,$ $25 \leq t \leq 50 \text{ ms}$
 $i = 0t,$ $50 \text{ ms} < t$
- b) $v = 0,$ $t < 0$
 $v = 6 \text{ V},$ $0 \leq t \leq 25 \text{ ms}$
 $v = -6 \text{ V},$ $25 \leq t \leq 50 \text{ ms}$
 $v = 0,$ $50 \text{ ms} < t$
 $p = 0,$ $t < 0$
 $p = 96t \text{ W},$ $0 \leq t \leq 25 \text{ ms}$
 $p = 96t - 4.8 \text{ W},$ $25 \leq t \leq 50 \text{ ms}$
 $p = 0,$ $50 \text{ ms} < t$
 $w = 0,$ $t < 0$
 $w = 48t^2 \text{ J},$ $0 \leq t \leq 25 \text{ ms}$
 $w = 48t^2 - 4.8t + 0.12 \text{ J},$ $25 \leq t \leq 50 \text{ ms}$
 $w = 0,$ $50 \text{ ms} < t$
- 6.7 a) $-8.75e^{-2500t} + 18.75e^{-7500t} \text{ V}$
 b) $152.44 \mu\text{s}$
- 6.9 a) 2.77 ms
 b) 64.27 V
- 6.12 1007 W , absorbing
- 6.16 a) $250 \mu\text{J}$
 b) 19.31 mJ
- 6.18 a) $1.25 \mu\text{C}$
 b) 5 V
 c) $2 \mu\text{J}$
- 6.21 20 H
- 6.25 5 nF , with initial voltage of 10 V , positive at the bottom
- 6.27 32.19 ms
- 6.31 a) $54,031.25 \text{ nJ}$
 b) $44,031.25 \text{ nJ}$
 c) $10,000 \text{ nJ}$
 d) 18.51%
 e) 1.39 ms
- 6.35 a) $60 + 5780e^{-4t} - 5840e^{-5t} \text{ V}$
 b) 0 V
 c) $960 + 92,480e^{-4t} - 94,400e^{-5t} - 92,480e^{-9t} + 93,440e^{-10t} \text{ W}$
 d) 960 W
 e) $p_{5\Omega} = 720 \text{ W}$; $p_{20\Omega} = 180 \text{ W}$; $p_{60\Omega} = 60 \text{ W}$
- 6.39 a) 0.85
 b) 28 mH
 c) 7
- 6.44 $v(t) = \frac{1}{3}v_s(t) + v(0)$, so moving the button has no effect on the change in $v(t)$

Chapter 7

- 7.1 a) 25Ω
 b) 12.5 ms
 c) 312.5 mH
 d) 2.5 J
 e) 10.06 ms
- 7.3 33.33%
- 7.5 a) $i_1(0^-) = i_2(0^-) = 0.2 \text{ mA}$
 b) $i_1(0^+) = 0.2 \text{ mA}$; $i_2(0^+) = -0.2 \text{ mA}$
 c) $0.2e^{-10^6t} \text{ mA}, t \geq 0$
 d) $-0.2e^{-10^6t} \text{ mA}, t \geq 0^+$
 e) The current in the resistor can change instantaneously.
- 7.7 48.64%
- 7.9 a) 200 A
 b) 220 A
 c) $307.6 \mu\text{s}$ (6 mH , not 2 mH)

1014 ■ ANSWERS TO SELECTED PROBLEMS

- 7.12 a) 625 nJ
b) 625 nJ
- 7.14 a) $2e^{-25,000t}$ V, $t \geq 0^+$
b) 80 nJ
c) 59.9 μ s
- 7.19 a) 180.34 mH
b) 93.75 %
- 7.22 a) $i = 15e^{-125t}$ mA, $t \geq 0^+$ $v_1 = 60e^{-125t} + 15$ V, $t \geq 0$; $v_2 = -15e^{-125t} + 15$ V, $t \geq 0$
b) 5625 μ J
c) $w_{\text{trapped}} = 1125 \mu\text{J}$ $w_{\text{diss}} = 4500 \mu\text{J}$
- 7.25 a) 125×10^{-6} A/V
b) $180e^{-1000t}$ V
- 7.28 a) $10e^{-5000t}$ mA, $t \geq 0^+$
b) $(-\frac{20}{3}e^{-5000t} + \frac{320}{3})$ V, $t \geq 0$
c) 2560 μ J
- 7.31 $-312.5e^{-500t}$ μ A, $t \geq 0^+$
- 7.36 80.47 ms
- 7.39 a) $V_s = 80$ V; $R = 20 \Omega$; $I_o = 8$ A; $L = 0.5$ H
b) 17.33 ms
- 7.42 $3.67 + 6.33e^{-250t}$ A, $t \geq 0$
- 7.44 $-60 + 90e^{-2000t}$ V, $t \geq 0$
- 7.47 a) $-480e^{-10t}$ V, $t \geq 0^+$
b) $4e^{-10t} + 4$ A, $t \geq 0$
c) $6e^{-10t} + 6$ A, $t \geq 0$
- 7.55 356.4 ms
- 7.60 a) $4 - 4e^{-20t}$ A, $t \geq 0$
b) $80e^{-20t}$ V, $t \geq 0^+$
c) $2.4 - 2.4e^{-20t}$ A, $t \geq 0$
d) $1.6 - 1.6e^{-20t}$ A, $t \geq 0$
- e) Yes, the final values of i_o , i_1 , and i_2 are consistent with conservation of flux linkage
- 7.63 6.63 V
- 7.67 0 A
- 7.72 $v_o = 100$ V, $0 \leq t \leq 250$ ms $v_o = 100e^{-1000(t-0.25)}$ V, 250 ms $\leq t \leq \infty$
- 7.76 a) $v_o = 0$, $t < 0$ $v_o = 200e^{-32,000t}$ V, $0 < t \leq 50 \mu\text{s}$ $v_o = -159.62e^{-32,000(t-50 \times 10^{-6})}$ V, $50 \mu\text{s} \leq t \leq \infty$
b) $v_o(50^- \mu\text{s}) = 40.38$ V
 $v_o(50^+ \mu\text{s}) = -159.62$ V
c) $i_o(50^- \mu\text{s}) = i_o(50^+ \mu\text{s}) = 19.95$ mA
- 7.79 173.23 μ s
- 7.83 27 ms
- 7.87 25 ms
- 7.94 a) 25 μ s
b) 25 μ s
c) 25 μ s
d) 25 μ s
e) 3.5 mA
f) 0.5465 mA
g) 8.86 V
- 7.100 a) 8.55 flashes per minute
b) 558.74 k Ω
- Chapter 8**
- 8.2 a) $3.79 \sin 3.16t$ V
b) 0.5 Hz
c) 3.79 V
- 8.4 a) $R = 10$ k Ω ; $C = 12.5$ nF; $D_1 = -5 \times 10^5$; $D_2 = 25$ V
b) $(25,000t - 7.5)e^{-4000t}$ mA
- 8.6 a) 12.5 k Ω
b) $(25 \times 10^4 t - 25)e^{-5000t}$ V
c) 11.16 V
d) 49.79 %
- 8.10 a) -5000 rad/s; $-20,000$ rad/s
b) overdamped

- c) 7812.5Ω
 d) $(-8000 + j6000) \text{ rad/s}$; $(-8000 - j6000) \text{ rad/s}$
 e) 6250Ω
- 8.15 $45e^{-8000t} \cos 6000t - 60e^{-8000t} \sin 6000t \text{ V}$
 8.20 $-140e^{-2000t} + 200e^{-8000t} \text{ V}$
 8.24 $v_o = 0$ for $t \geq 0$, so the circuit goes directly into steady-state when the switch is closed
 8.27 $12e^{-800t} \cos 600t + 16e^{-800t} \sin 600t \text{ V}$
 8.29 $40 - 40e^{-5000t} \cos 5000t - 40e^{-5000t} \sin 5000t \text{ V}$
 8.32 $50e^{-40t} - 50e^{-160t} \text{ V}$
 8.35 $60e^{-10t} \sin 70t \text{ mA}$
 8.37 a) $20e^{-1000t} - 5e^{-4000t} \text{ mA}$
 b) $80e^{-1000t} - 5e^{-4000t} \text{ V}$
 8.44 a) $5000t e^{-250t} + 20e^{-250t} \text{ V}$
 b) $100 - 12,500te^{-250t} - 100e^{-250t} \text{ mA}$
 8.48 a) 300 V
 b) $-12,000 \text{ V/s}$
 c) $300e^{-80t} \cos 60t - 200e^{-80t} \sin 60t \text{ V}$

Chapter 9

- 9.1 a) $2000\pi \text{ rad/s}$
 b) $10 \cos(2000\pi t + 54^\circ) \text{ A}$
- 9.4 a) 2000 Hz
 b) $150 \cos(4000\pi t - \frac{\pi}{3}) \text{ V}$
- 9.8 169.71 V
- 9.11 a) 50 Hz
 b) 0°
 c) -90°
 d) 40Ω
 e) 127.32 mH
 f) $j40 \Omega$
- 9.14 $1.5 \cos(5000t + 36.87^\circ) \text{ mA}$
- 9.17 5000 rad/s
- 9.21 a) $L = 0.2 \text{ H}, 0.8 \text{ H}$
 b) for $L = 0.2 \text{ H}$, $i_g = 40 \cos 10,000t \text{ mA}$ for $L = 0.8 \text{ H}$, $i_g = 20 \cos 10,000t \text{ mA}$
- 9.24 a) 8000 rad/s

- b) $5 \cos 8000t \text{ V}$
- 9.29 a) $5/\underline{72^\circ} \Omega$
 b) i_g lags v_g by $50 \mu\text{s}$
- 9.31 $50 \cos(5000t - 106.26^\circ) \text{ V}$
- 9.34 $31.62 \cos(8000t - 71.57^\circ) \text{ V}$
- 9.39 $\mathbf{I}_N = 6.4 - j4.8 \text{ A}$; $Z_N = 50 - j25 \Omega$
- 9.41 $\mathbf{V}_{Th} = 60/\underline{-36.87^\circ} \text{ V}$; $Z_{Th} = 8.64 + j11.52 \Omega$
- 9.43 $\mathbf{V}_{Th} = 15/\underline{36.87^\circ} \text{ V}$; $Z_{Th} = 96 + j72 \Omega$
- 9.47 $15 + j5 \text{ V}$
- 9.54 $9.49 \cos(40,000t - 18.43^\circ) \text{ A}$
- 9.58 $i_a = 22.02 \cos(10,000t - 50.53^\circ) \text{ A}$
 $i_b = 24.02 \cos(10,000t + 50.74^\circ) \text{ A}$
- 9.63 30Ω
- 9.68 $800 + j600 \Omega$
- 9.72 a) $2.15 \cos(10^5 t - 21.80^\circ) \text{ V}$
 b) 4.64 V

Chapter 10

- 10.1 a) $P = 2404.16 \text{ W (abs)}$; $Q = 2404.16 \text{ VAR (abs)}$
 b) $P = 155.29 \text{ W (abs)}$; $Q = -579.56 \text{ VAR (del)}$
 c) $P = -427.53 \text{ W (del)}$; $Q = -1174.62 \text{ VAR (del)}$
 d) $P = -307.82 \text{ W (del)}$; $Q = 845.72 \text{ VAR (del)}$
- 10.4 a) 60 V (rms)
 b) 300 W
- 10.6 80Ω
- 10.8 $P = 56.25 \text{ mW}$; $Q = -70.3125 \text{ mVAR}$; $|S| = 90.044 \text{ mVA}$
- 10.10 a) $\text{pf}_1 = 0.96$ lagging; $\text{rf}_1 = 0.28$; $\text{pf}_2 = 0.80$ leading; $\text{rf}_2 = -0.60$; $\text{pf}_3 = 0.6$ leading; $\text{rf}_3 = -0.8$
 b) $\text{pf} = 0.74$ leading; $\text{rf} = -0.67$
- 10.13 a) 160 W
 b) -40 W
 c) 60 W
 d) -80 VAR
 e) generate

1016 ■ ANSWERS TO SELECTED PROBLEMS

- f) 0.6 leading
g) -0.8
- 10.16 a) 492.37 V(rms)
b) 102.31 μs
c) lags by 2.21° or 102.31 μs
- 10.19 a) $72 - j24 \Omega$
b) 0.9487 leading
- 10.22 0.2727 leading
- 10.24 a) 414.72 W
b) 501.4 Ω
c) 1671.33 Ω
d) 37.02 W
e) 8.93 %
- 10.28 a) 129.15 V(rms)
b) 240 W
c) 1188.36 μF
d) 126.49 V(rms)
e) 221.184 W
- 10.31 a) 9 W
b) 20 Ω
c) 17.31 W; yes
d) 18.75 W
e) $R_o = 30 \Omega$; $L_o = 9 \text{ mH}$
f) yes
- 10.34 a) $30 + j10 \text{ k}\Omega$
b) 16.875 mW
- 10.37 a) 312.5 W
b) 10 %
- 10.39 a) -1700 kVAR
b) deliver
c) 0.3328 leading
d) 625 A(rms)
e) 520.83 A(rms)
- 10.43 612.5 W
- 10.46 a) $140 \angle 0^\circ \text{ V(rms)}$
b) 280 W
- c) 9.72 %
- 10.54 $20 + j0 \Omega$
- 10.57 a) 100 W
b) 44.44 %
c) 225 W
- 10.60 a) $a_1 = 5$; $a_2 = 40$
b) 800 mW
c) 4 V(rms)
- 10.65 $R_1 = R_2 = R_3 = 8 \Omega$
- Chapter 11**
- 11.3 a) 0 A
b) $226.99 \angle 116.48^\circ \text{ V}$
c) $387.79 \angle 86.48^\circ \text{ V}$
d) unbalanced
- 11.6 a) 32.84 A(rms)
b) 12,845.94 V(rms)
- 11.10 $3.93 \angle -122.69^\circ \text{ A}$
- 11.14 a) $\mathbf{I}_{AB} = 92 \angle -36.87^\circ \text{ A}$; $\mathbf{I}_{BC} = 92 \angle -156.87^\circ \text{ A}$;
 $\mathbf{I}_{CB} = 92 \angle 83.13^\circ \text{ A}$
b) $\mathbf{I}_{aA} = 159.35 \angle -66.87^\circ \text{ A}$;
 $\mathbf{I}_{bB} = 159.35 \angle -186.87^\circ \text{ A}$;
 $\mathbf{I}_{cC} = 159.35 \angle 53.13^\circ \text{ A}$;
c) $\mathbf{I}_{ba} = 92 \angle -36.87^\circ \text{ A}$; $\mathbf{I}_{cb} = 92 \angle -156.87^\circ \text{ A}$;
 $\mathbf{I}_{ac} = 92 \angle 83.13^\circ \text{ A}$
- 11.18 a) $651 + j246 \text{ kVA}$
b) 99.54 %
- 11.20 a) 138.46 A(rms)
b) 0.892 lagging
- 11.22 6990.62 V
- 11.24 a) 468.91 A
b) 66.2 kVAR
- 11.27 a) 4551.4 V
b) 97.96 %
- 11.32 a) 7776 VAR
b) 7776 VAR
- 11.37 a) $W_{m1} = 14,296.61 \text{ W}$; $W_{m2} = 29,261.53 \text{ W}$