

$$P_{-1.13} \quad a) \quad P = +vi = -12(30) = -360.$$

The power flow is thus from B to A, and car A has the "dead" battery.

$$b) \quad W = \int_0^t P dx = \int_0^t 360 dx = 360t = 360 \times 60 \\ = 21.6 \text{ kJ}$$

$$P_{-1.15} \quad a) \quad P = vi = 30e^{-500t} - 30e^{-1500t} - 40e^{-1000t} \\ + 50e^{-2000t} - 10e^{-3000t}$$

$$P(1\text{ms}) = 3.1 \text{ mW}$$

$$b) \quad W(t) = \int_0^t P(x) dx$$

$$= \int_0^t (30e^{-500x} - 30e^{-1500x} - 40e^{-1000x} \\ + 50e^{-2000x} - 10e^{-3000x}) dx$$

$$= 21.67 - 60e^{-500t} + 20e^{-1500t}$$

$$+ 40e^{-1000t} - 25e^{-2000t} + 3.33e^{-3000t} \quad \mu\text{J}$$

$$W(1\text{ms}) = 1.24 \mu\text{J}$$

$$c) \quad W_{\text{total}} = 21.67 \mu\text{J}$$

$$P_{1.21} \quad a) \quad p = v i$$

$$= 400 \times 10^3 t^2 e^{-800t} + 700t e^{-800t} + 0.25 e^{-800t}$$

$$= e^{-800t} [400,000 t^2 + 700t + 0.25]$$

$$\frac{dP}{dt} = e^{-800t} [800,000t + 700]$$

$$+ (-800) e^{-800t} [400,000t^2 + 700t + 0.25]$$

$$= (3,200,000t^2 - 2400t - 5) (-100 e^{-800t})$$

$$\therefore \frac{dP}{dt} = 0 \Rightarrow 3,200,000t^2 - 2400t - 5 = 0$$

so P_{\max} occurs at $t = 1.68 \text{ ms}$.

$$b) \quad P_{\max} = e^{-800(0.00168)} [400,000(0.00168)^2$$

$$+ 700(0.00168) + 0.25] = 666 \text{ mW}$$

$$c) \quad W = \int_0^t P(x) dx$$

$$= \int_0^t 4 \times 10^5 x^2 e^{-800x} dx + \int_0^t 700x e^{-800x} dx + \int_0^t 0.25 e^{-800x} dx$$

$$= \frac{4 \times 10^5 e^{-800x}}{-512 \times 10^6} [64 \times 10^4 x^2 + 1600x + 2] \Big|_0^t +$$

$$\frac{700 e^{-800x}}{64 \times 10^4} [-800x - 1] \Big|_0^t + 0.25 \frac{e^{-800x}}{-800} \Big|_0^t$$

When $t = \infty$, all upper limits go to zero. Thus,

$$W = \frac{4 \times 10^5 (2)}{512 \times 10^6} + \frac{700}{64 \times 10^4} + \frac{0.25}{800} = 2.97 \text{ mJ}$$

P- 2.6 The interconnection is valid because it does not violate KCL or KVL.

$$i_o = -25 \text{ A}; \quad 6i_{\Delta} = -150 \text{ V}$$

$$-200 + 50 - (-150) = 0$$

P- 2.9 The interconnection is valid because it does not violate KCL or KVL.

$$P_{\text{v-source}} = (100 - 60)(5) = 200 \text{ W}$$

P- 2.12 (a)
$$V_o = 8i_a + 14i_a + 18i_a = 40(20) = 800 \text{ V}$$

$$800 = 10i_o$$

$$i_o = \frac{800}{10} = 80 \text{ A}$$

b)
$$i_g = i_a + i_o = 20 + 80 = 100 \text{ A}$$

c)
$$P_g (\text{delivered}) = 100(800) = 80,000 \text{ W}$$

$$= 80 \text{ kW}$$