

P9.31


$$\bar{Z}_0 = 600 - j \frac{10^6}{5000(0.25)} = 600 - j800 \Omega$$

$$\bar{Z}_T = 300 + j2000 + 600 - j800 = 900 + j1200 \Omega = 1500 \angle 53.13^\circ \Omega$$

$$\bar{V}_o = \frac{\bar{Z}_0}{\bar{Z}_T} \bar{V}_g = \frac{1000 \angle -53.13^\circ}{1500 \angle 53.13^\circ} (75 \angle 0^\circ) = 50 \angle -106.26^\circ \text{ V}$$

$$v_o(t) = 50 \cos(5000t - 106.26^\circ) \text{ V.}$$

P9.35

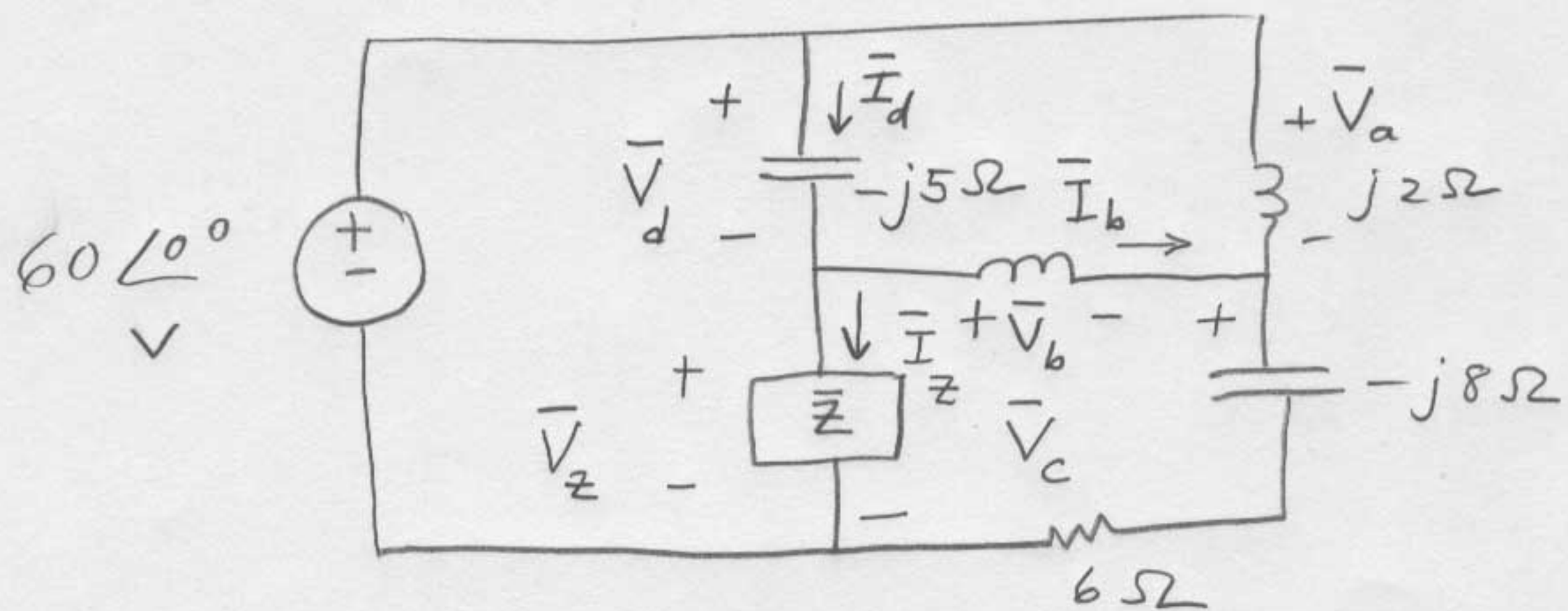

$$\bar{V}_a = j2 \bar{I}_a = j2(-j5) = 10 \angle 0^\circ \text{ V}$$

$$\bar{V}_c = 60 \angle 0^\circ - \bar{V}_a = 50 \angle 0^\circ \text{ V}$$

$$\bar{I}_c = \frac{\bar{V}_c}{6 - j8} = \frac{50 \angle 0^\circ}{10 \angle -53.13^\circ} = 5 \angle 53.13^\circ = 3 + j4 \text{ A}$$

$$\bar{I}_b = \bar{I}_c - \bar{I}_a = 3 + j4 - (-j5) = 3 + j9 = 9.49 \angle 71.57^\circ \text{ A.}$$

$$\bar{V}_b = j5 \bar{I}_b = j5(3 + j9) = -45 + j15 \text{ V}$$

$$\bar{V}_z = \bar{V}_b + \bar{V}_c = -45 + j15 + 50 + j0 = 5 + j15 \text{ V}$$


$$\bar{V}_d + \bar{V}_z = 60 \angle 0^\circ \quad \therefore \bar{V}_d = 60 - 5 - j15 = 55 - j15 \text{ V}$$

$$\bar{I}_d = \frac{V_d}{-j5} = 3 + j11 \text{ A}$$

$$\bar{I}_z = \bar{I}_d - \bar{I}_b = 3 + j11 - 3 - j9 = j2 \text{ A}$$

$$\bar{Z} = \frac{\bar{V}_z}{\bar{I}_z} = \frac{5 + j15}{j2} = 7.5 - j2.5 \Omega$$

P 9.42

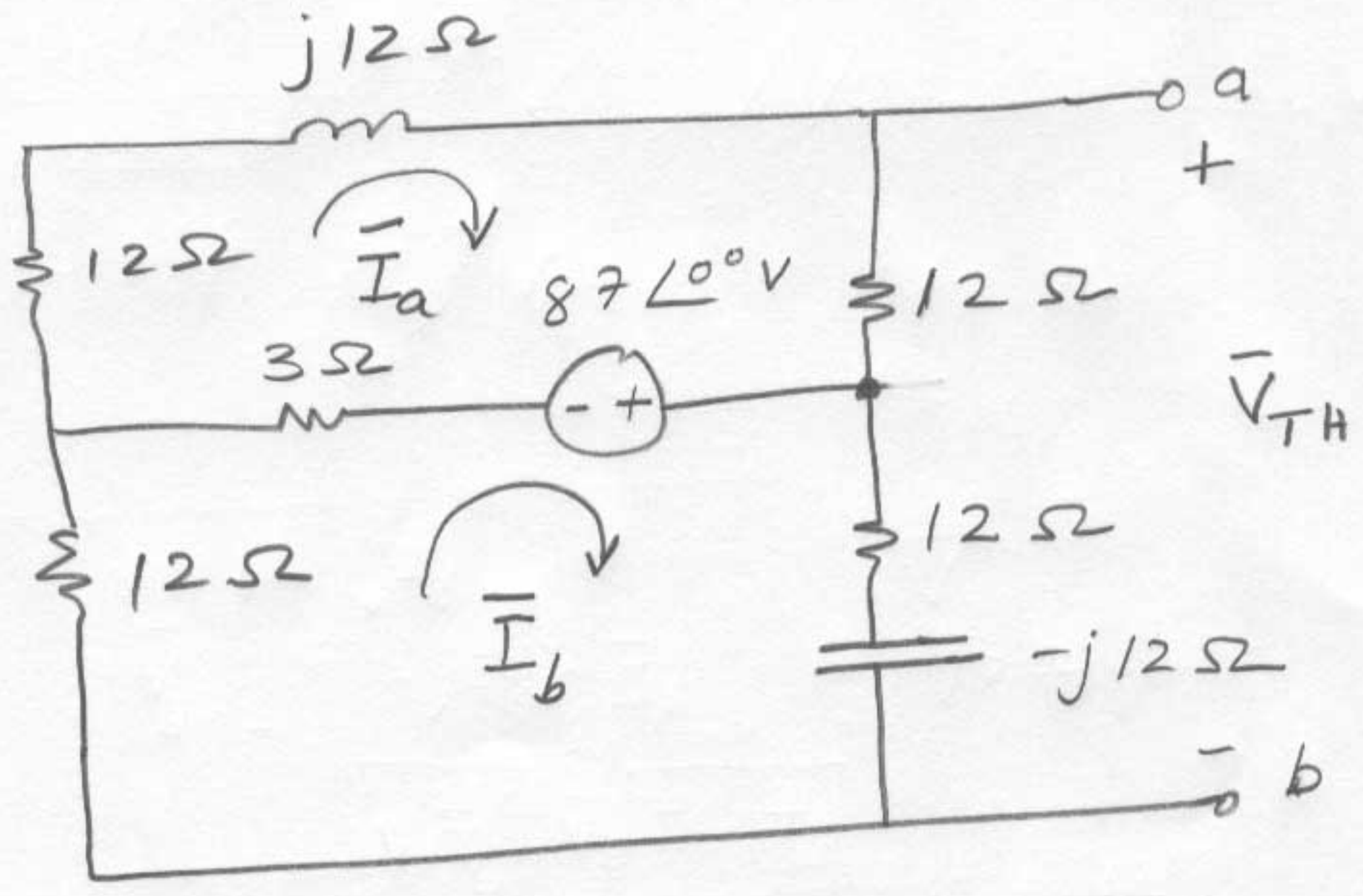

$$(27 + j12)\bar{I}_a - 3\bar{I}_b = -87\angle 0^\circ \quad (1)$$


$$-3\bar{I}_a + (27 - j12)\bar{I}_b = 87\angle 0^\circ \quad (2)$$

solving (1) & (2) \Rightarrow

$$\bar{I}_a = -2.4167 + j1.21, \quad \bar{I}_b = 2.4167 + j1.21$$

$$\bar{V}_{TH} = 12\bar{I}_a + (12 - j12)\bar{I}_b = 14.5\angle 0^\circ \text{ V}$$

Short circuit test:

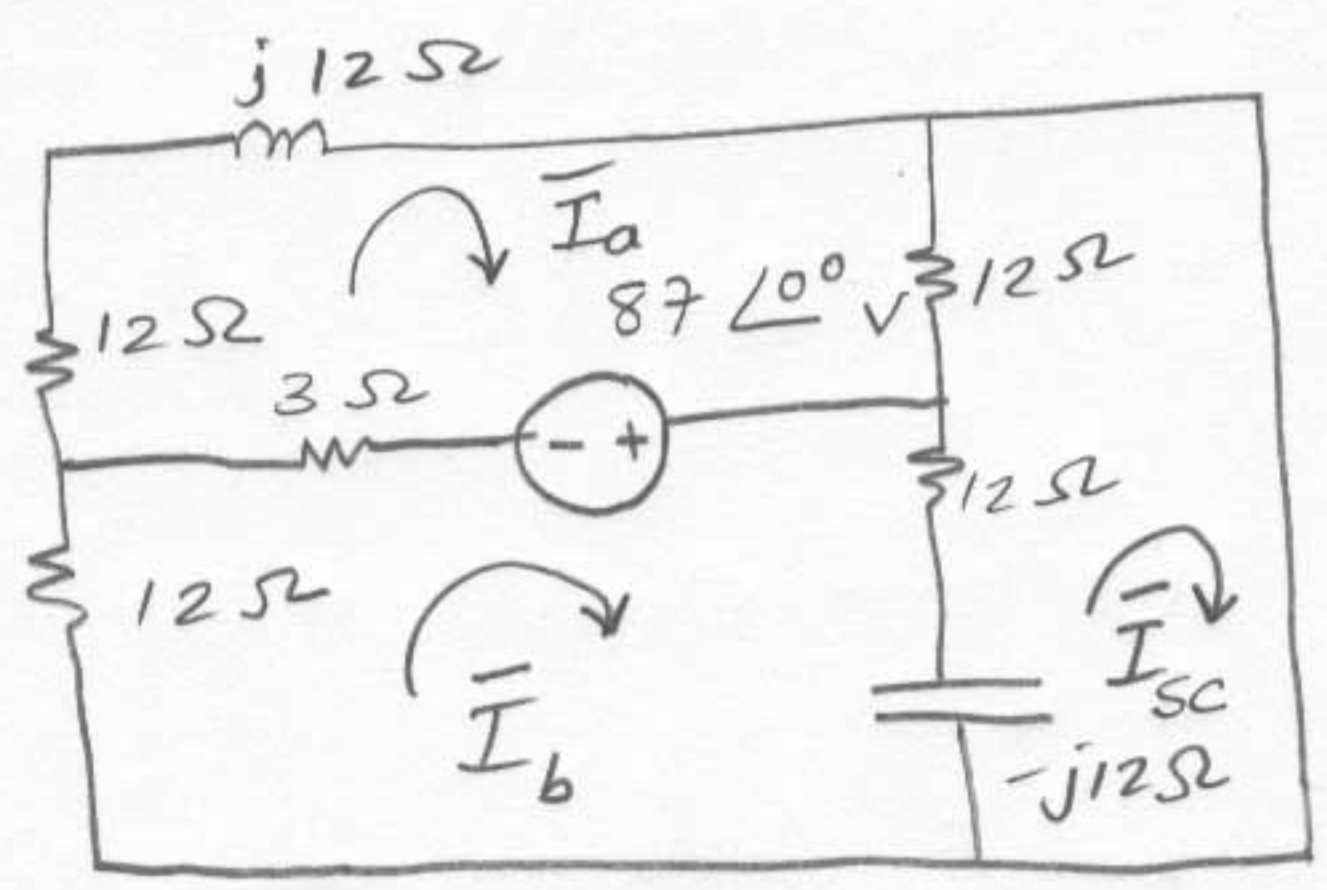

$$(27 + j12) \bar{I}_a - 3\bar{I}_b - 12\bar{I}_{sc} = -87 \quad (1)$$

$$-3\bar{I}_a + (27 - j12) \bar{I}_b - (12 - j12) \bar{I}_{sc} = 87 \quad (2)$$

$$-12\bar{I}_a - (12 - j12) \bar{I}_b + (24 - j12) \bar{I}_{sc} = 0 \quad (3)$$

solving (1) - (2) - (3) \Rightarrow

$$\bar{I}_{sc} = 1 \angle 0^\circ$$

$$\therefore \bar{Z}_{TH} = \frac{\bar{V}_{TH}}{\bar{I}_{sc}} = \frac{14.5 \angle 0^\circ}{1 \angle 0^\circ} = 14.5 \Omega$$


p 9.50

$$j\omega L = j5000(0.4 \times 10^{-3}) = j2 \Omega$$


$$\frac{1}{j\omega C} = -j \frac{10^6}{5000(50)} = -j4 \Omega$$

$$\bar{V}_{g1} = 10 \angle 53.13^\circ = 6 + j8 \Omega$$
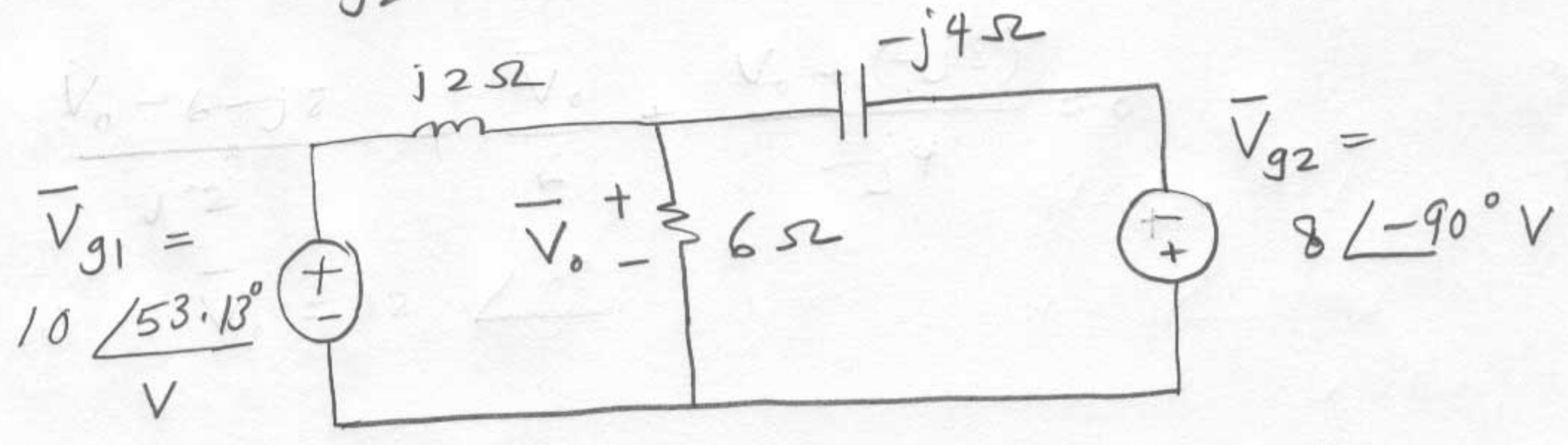
$$\bar{V}_{g2} = 8 \angle -90^\circ = -j8 \Omega$$



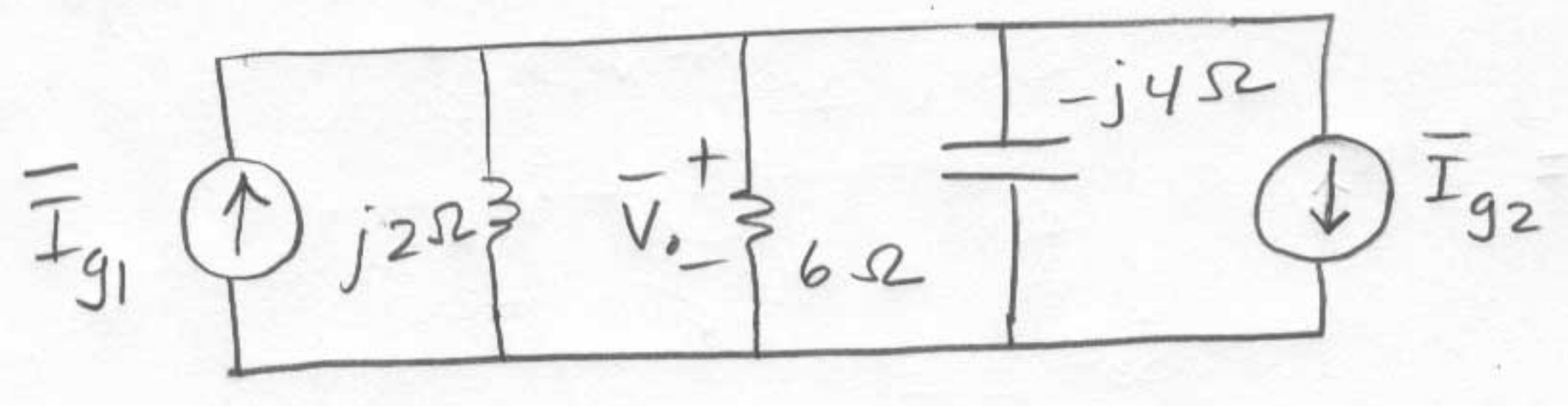Making two source transformations \Rightarrow




$$\bar{I}_{g1} = \frac{10 \angle 53.13^\circ}{j2} = 5 \angle -36.87^\circ = 4 - j3 \text{ A}$$

4/4

$$\bar{I}_{g2} = \frac{8 \angle -90^\circ}{-j4} = 2 \angle 0^\circ = 2 \text{ A}$$

$$\bar{Y} = \frac{1}{j2} + \frac{1}{6} + \frac{1}{-j4} \text{ (S)} = \frac{1}{6} - j\frac{1}{4} \text{ (S)}$$
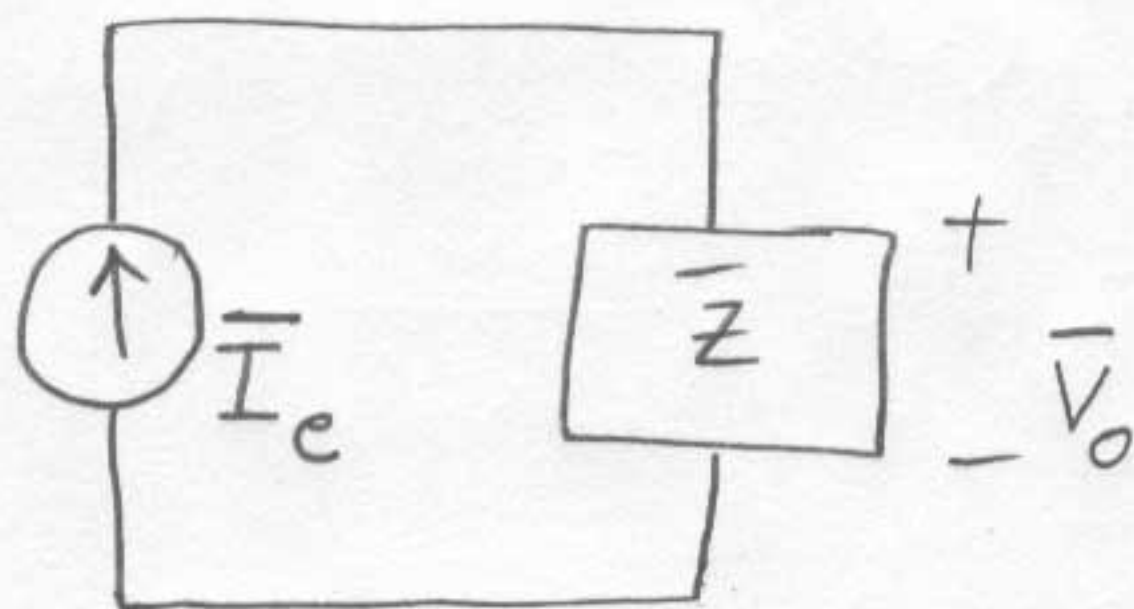
$$\bar{Z} = \frac{1}{\bar{Y}} = \frac{1}{\frac{1}{6} - j\frac{1}{4}} = 1.85 + j2.77 \text{ } \Omega$$



$$\bar{I}_e = \bar{I}_{g1} - \bar{I}_{g2} = 4 - j3 - 2 = 2 - j3 \text{ A}$$

$$\therefore \bar{V}_0 = \bar{Z} \bar{I}_e = (1.85 + j2.77)(2 - j3) = 12 \angle 0^\circ$$

$$v_0(t) = 12 \cos 5000t \text{ V}$$