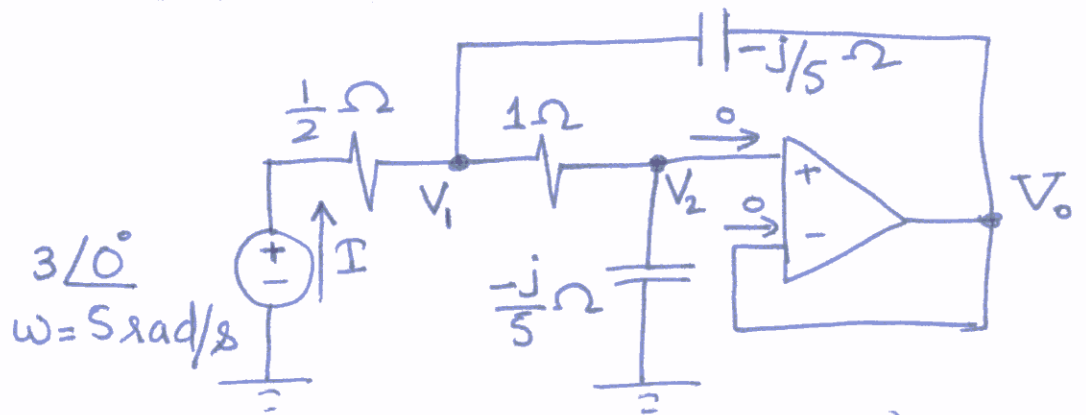


# Homework #2 Solution

Q1 (a)



$V_2 = V_0$  (because of op amp characteristics).

Nodal at  $V_1$   $2(V_1 - 3) + \frac{V_1 - V_2}{1} + (V_1 - V_0)(5j) = 0$

$$\Rightarrow 2V_1 - 6 + V_1 - V_0 + 5jV_1 - 5jV_0 = 0$$

$$\Rightarrow (3 + 5j)V_1 - (1 + 5j)V_0 = 6 \quad \text{--- ①}$$

Nodal at  $V_2$   $\frac{V_2 - V_1}{1} + (V_2)(5j) = 0$

$$\Rightarrow V_0 - V_1 + 5jV_0 = 0 \Rightarrow V_1 = (1 + 5j)V_0$$

Substitute in eq ①

$$\text{①} \Rightarrow (3 + 5j)(1 + 5j)V_0 - (1 + 5j)V_0 = 6$$

$$\Rightarrow (3 + 20j - 25 - 1 - 5j)V_0 = 6 \Rightarrow (-23 + 15j)V_0 = 6$$

$$\Rightarrow V_0 = \frac{6}{-23 + 15j} = \frac{6}{27.4 \angle 146.9} \Rightarrow V_0 = 0.22 \angle -146.9 = -0.18 - j0.12$$

(b) Impedance seen by voltage source =  $\frac{3 \angle 0^\circ}{I}$ .

~~Apply KCL at  $V_1 \Rightarrow I = \frac{V_1 - V_2}{1} + (V_1 - V_0)(5j)$~~

~~$\Rightarrow I = V_1 - V_0 + 5jV_1 - 5jV_0$~~

~~$= (1 + 5j)V_0 - V_0 + 5j(1 + 5j)V_0 - 5jV_0$~~

$$I = (3 \angle 0^\circ - V_1)2 = (3 - (1 + 5j)V_0)2$$

$$= [3 - (1 + 5j)(-0.18 - j0.12)]2 = [3 - (0.18 - j1.08 + 0.6)]2$$

$$= (2.58 + j1.08)2 = 5.16 + j2.16 = 5.59 \angle 22.71$$

$$\therefore Z = \frac{3 \angle 0^\circ}{5.59 \angle 22.71} = 0.537 \angle -22.71^\circ$$

Q2  $T = 3 \text{ sec.}$

$0 < t < 1$   $f(t) = t$


$1 < t < 2$   $f(t) = +2$

$2 < t < 3$   $f(t) = -1$

$$\begin{aligned} \therefore f_{\text{rms}} &= \sqrt{\frac{1}{3} \left[ \int_0^1 t^2 dt + \int_1^2 2^2 dt + \int_2^3 (-1)^2 dt \right]} \\ &= \sqrt{\frac{1}{3} \left[ \frac{1}{3} t^3 \Big|_0^1 + 4t \Big|_1^2 + t \Big|_2^3 \right]} \\ &= \sqrt{\frac{1}{3} \left[ \frac{1}{3} + 4 + 1 \right]} = \sqrt{\frac{16}{9}} = \frac{4}{3} = 1.77 \end{aligned}$$

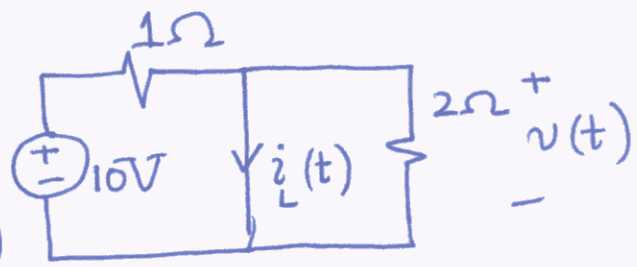
Q3 For  $t < 0$

$i_L(t) = \frac{10}{1} = 10 \text{ A}; \text{ for } t \leq 0$   
 $v(t) = 0$  (because short ckt)



For  $0 < t < 2$

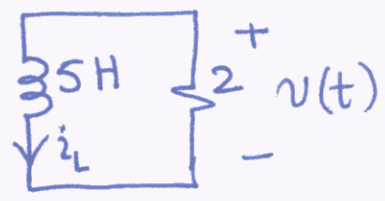
$\tau = L/R = \frac{5}{2}$  ;  $i_L(0) = 10 \text{ A}$   
 $i_L(t) = i_L(0) e^{-t/\tau} = 10 e^{-2t/5}$   
 $v_L(t) = v(t) = L \frac{di_L}{dt} = -20 e^{-2t/5}$



At  $t = 2 \text{ sec}$   $i_L(t) = 4.49 \text{ A}$


For  $t > 2$

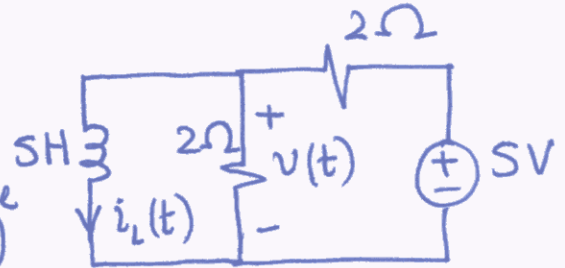$i_L(t) = F + (I - F) e^{-\frac{t-2}{\tau}}$   
 $i_L$  final value =  $\frac{5}{2} \text{ A}$ . (inductor behave as short ckt)  
 $i_L$  initial value =  $i_L(2) = 4.49 \text{ A}$ .



$\tau = L/R_{\text{eq}} = 5/1 = 5 \text{ sec.}$   
 $i_L(t) = \frac{5}{2} + (4.49 - \frac{5}{2}) e^{-\frac{t-2}{5}} = \frac{5}{2} + 2 e^{-\frac{1}{5}(t-2)}$  ; For  $t \geq 2$   
 $v_L(t) = v(t) = L \frac{di_L}{dt} = -2 e^{-\frac{1}{5}(t-2)}$  ; For  $t > 2$

Q4 (a)

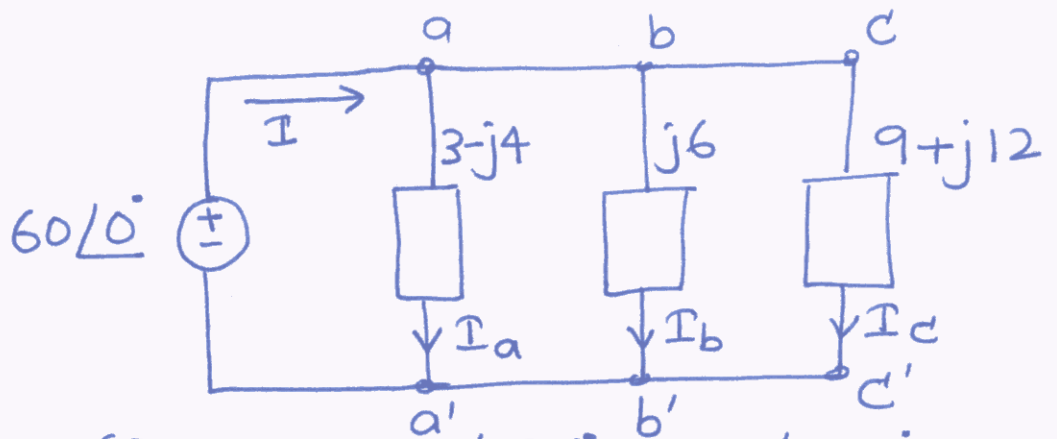

$$I_a = \frac{60}{3-j4} = \frac{60}{5 \angle -53.13^\circ} = \frac{60}{5} \angle 53.13^\circ = 12 \angle 53.13^\circ$$

$$I_b = \frac{60}{j6} = 10 \angle -90^\circ$$

$$I_c = \frac{60}{9+j12} = \frac{60}{15 \angle 53.13^\circ} = 4 \angle -53.13^\circ$$

For branch a-a'  $S = V I_a^* = (60 \angle 0^\circ)(12 \angle -53.13^\circ)$

$$\Rightarrow S = 720 \angle -53.13^\circ = 432 - j576 \text{ VA}$$

$$\therefore P = 432 \text{ W} ; Q = -576 \text{ VAR} ; \text{P.f.} = \cos(53.13^\circ) = 0.6$$

For branch b-b'  $S = V I_b^* = (60 \angle 0^\circ)(10 \angle -90^\circ)$

$$\Rightarrow S = 600 \angle -90^\circ = -j600 \text{ VA}$$

$$\therefore P = 0 \text{ W} ; Q = -600 \text{ VAR} ; \text{P.f.} = \cos(-90^\circ) = 0$$

For branch c-c'  $S = V I_c^* = (60 \angle 0^\circ)(4 \angle -53.13^\circ)$

$$\Rightarrow S = 240 \angle -53.13^\circ \Rightarrow S = 144 - j192 \text{ VA}$$

$$\therefore P = 144 \text{ W} ; Q = -192 \text{ VAR} ; \text{P.f.} = \cos(-53.13^\circ) = 0.6$$

(b)  $I = I_a + I_b + I_c \Rightarrow I = 12 \angle 53.13^\circ + 10 \angle -90^\circ + 4 \angle -53.13^\circ$


$$\Rightarrow I = 7.2 + j9.6 - j10 + 2.4 - j3.2$$

$$\Rightarrow I = 9.6 - j3.6 = 10.25 \angle -20.6^\circ$$

$$\therefore \text{P.f.} = \cos(\theta_V - \theta_I) = \cos(0 - (-20.6)) = 0.936$$

Since  $\theta_V - \theta_I = +ve$   $\therefore$  lagging  $\therefore$  inductive.

Q5

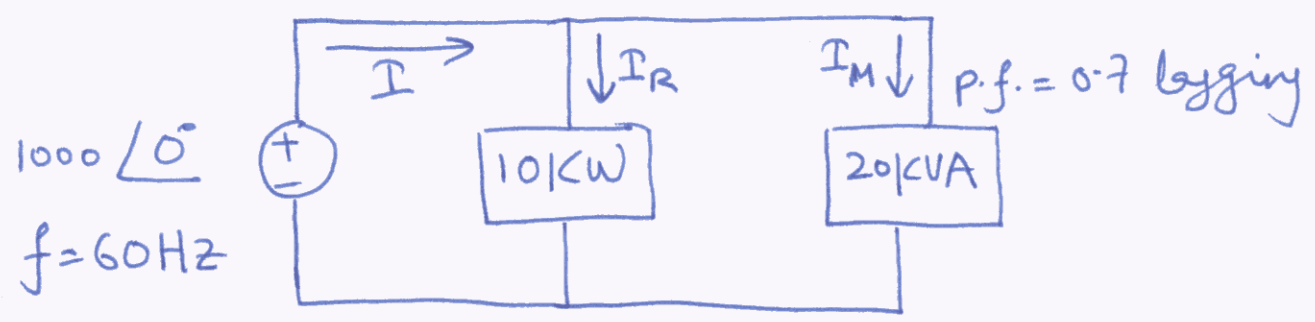

(a)  $P = VI \cos \theta \Rightarrow 10,000 = 1000 I_R \cdot 1 \Rightarrow |I_R| = 10\text{A}$   
 $\therefore I_R = 10 \angle 0^\circ$  ( $\because$  resistive  $\therefore \theta_I = \theta_V$ )

For motor  $|S| = |V| |I_M| = 20,000$   
 $\Rightarrow |I_M| = \frac{20,000}{1000} = 20\text{A}$

$\therefore I_M = 20 \angle -45.57^\circ$

$\therefore I = I_R + I_M = 10 + 20 \angle -45.57^\circ = 10 + 14j14.3$   
 $I = 24 - j14.3 \text{ A}$

(b) After connecting a capacitor in parallel

$I = (I_R + I_M) + I_C$   
 $= (24 - j14.3) + (j\omega C)(V) = (24 - j14.3) + (j \times 2\pi \times 60 C)$   
 (1000)

$I = 24 - j14.3 + j376991.11C$

$\Rightarrow I = 24 + j(376991.11C - 14.3)$

$\Rightarrow \theta_I = \tan^{-1} \left( \frac{376991.11C - 14.3}{24} \right)$

Since we want  $\cos(\theta_V - \theta_I) = 0.95$

$\Rightarrow \theta_V - \theta_I = +18.2^\circ \Rightarrow \theta_I = -18.2^\circ$

$\therefore \tan^{-1} \left( \frac{376991.11C - 14.3}{24} \right) = -18.2^\circ$

$\Rightarrow \boxed{C = 17 \mu\text{F}}$