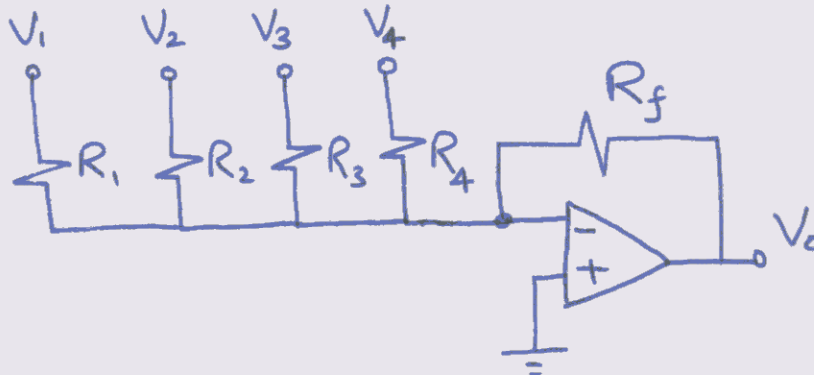


Homework # 1
EE201 (032)
Instructor: Noman Ali Tasadduq


- Q1. In the op amp circuit shown in the figure below,
- find an expression for the output voltage 'Vo'
 - Let $R_f=10k\Omega$, $R_1=10k\Omega$, $R_2=20k\Omega$, $R_3=40k\Omega$ and $R_4=80k\Omega$. Inputs V_1 to V_4 could have only two values, either 0 or 1 (binary input). If V_1 is the most significant bit (MSB) and V_4 is the least significant bit (LSB) draw a table with three columns, with the first column showing the binary input [$V_1V_2V_3V_4$], the second column showing the decimal equivalent value and the third column showing the value of output voltage (V_o) from equation of part (a). Obtain the output voltage for all the combination of binary inputs [0000],[0001],[0010],.....,[1111]
 - Can you guess from the table of part (b) what is the function performed by this op amp circuit.

(Notice that the resistor values are $R_4=2R_3=4R_2=8R_1$. This is called binary weighted ladder.)



- Q2. Your laboratory has available a large number of $10\mu\text{F}$ capacitors rated at 300V. To design a circuit you need a $40\mu\text{F}$ capacitor rated at 600V. How many $10\mu\text{F}$ capacitors rated at 300V are needed from the laboratory and how would you connect them to get a $40\mu\text{F}$ capacitor rated at 600V. Show the connection of capacitors clearly.

- Q3. Find V_o , if $V_s=12\text{mV}$.

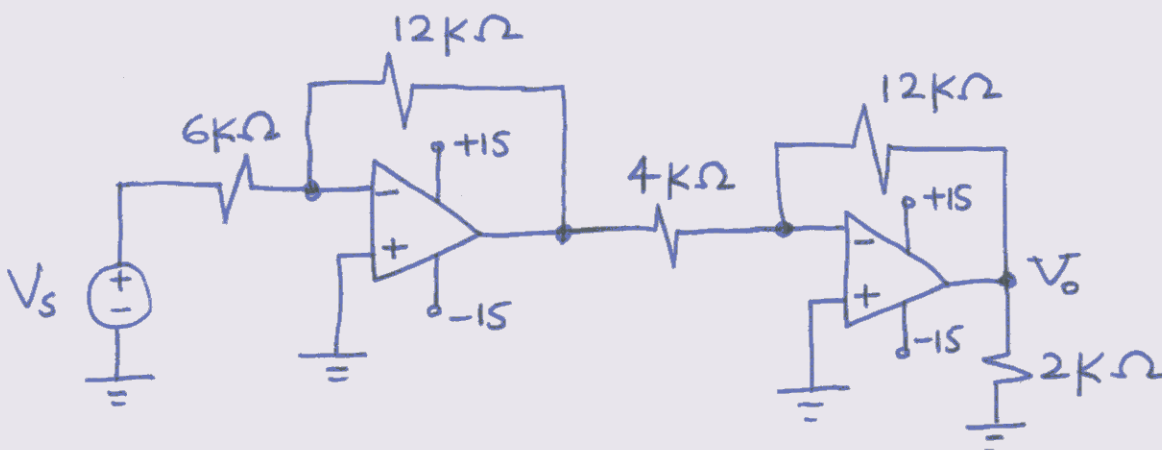

- Q4. A 10V dc voltage is applied to an op amp integrator with $R=50k\Omega$, $C=100mF$ at $t=0$. How long will it take for the op amp to saturate (non linear region) if the supply voltages are $\pm 12V$? Assume that the initial capacitor voltage was zero.
- Q5. The gap in the circuit will arc over whenever the voltage across the gap reaches 36kV (36000V). The initial current in the inductor is zero. The value of β is adjusted so that the Thevenin resistance seen by the inductor becomes $(-3k\Omega)$.
- (a) What is the value of β ?
- (b) How many microseconds after the switch has been closed will the gap arc over?

[What is Arcing: When electricity flows through the air from one pole of an electric circuit to another, or jumps from its source to ground without flowing through a desired circuit, it is said to arc. This phenomenon is often accompanied by visible flashes of light and a crackling noise. Lightning and static electricity shocks are well-known examples of arcing. In electrical generation, arcing is usually undesirable because an arc sends all electricity to ground without putting it to a practical use. However, deliberately-created high-intensity arcs of electricity have many practical applications ranging from welding to high-intensity lighting.]

