
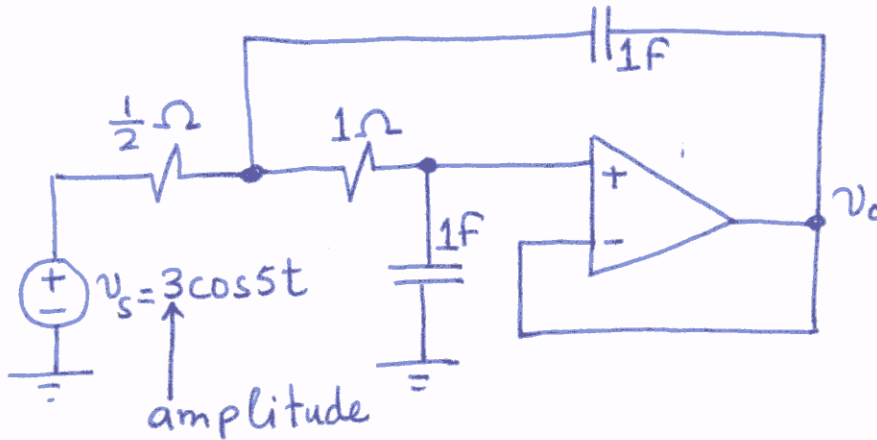


Homework # 2
EE201 (032)
Instructor: Noman Ali Tasadduq

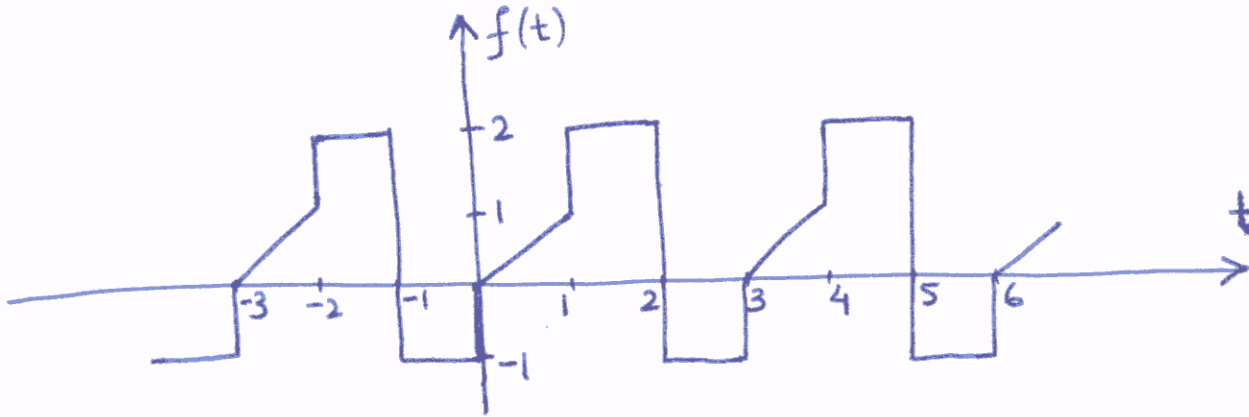
- Q1. In the op amp circuit shown in the figure below, find
 (a) $v_o(t)$ and
 (b) the impedance seen by the voltage source



- Q2. Find the rms value of the function shown in the figure below




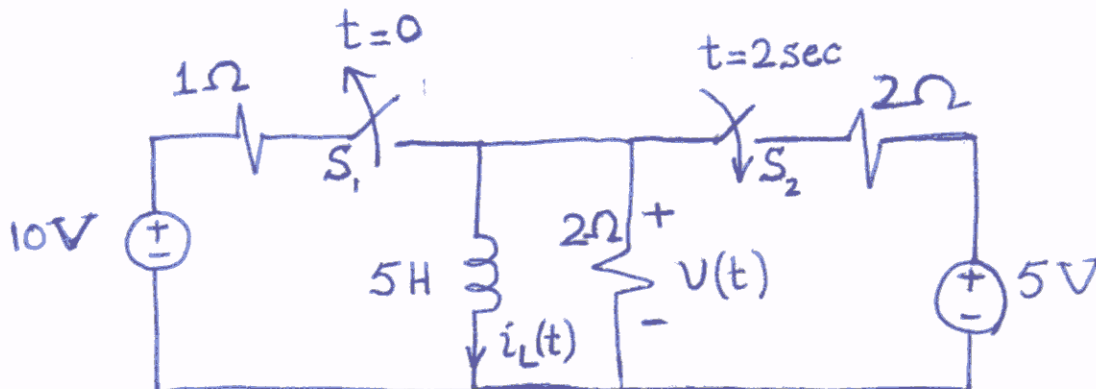- Q3. The switch S_1 is closed for a long time and is opened at $t = 0$ sec. Similarly the switch S_2 is open for a long time and is closed at $t = 2$ sec. Determine
 (a) $i_L(t)$ for all time
 (b) $v(t)$ for all time



Q4. For the network

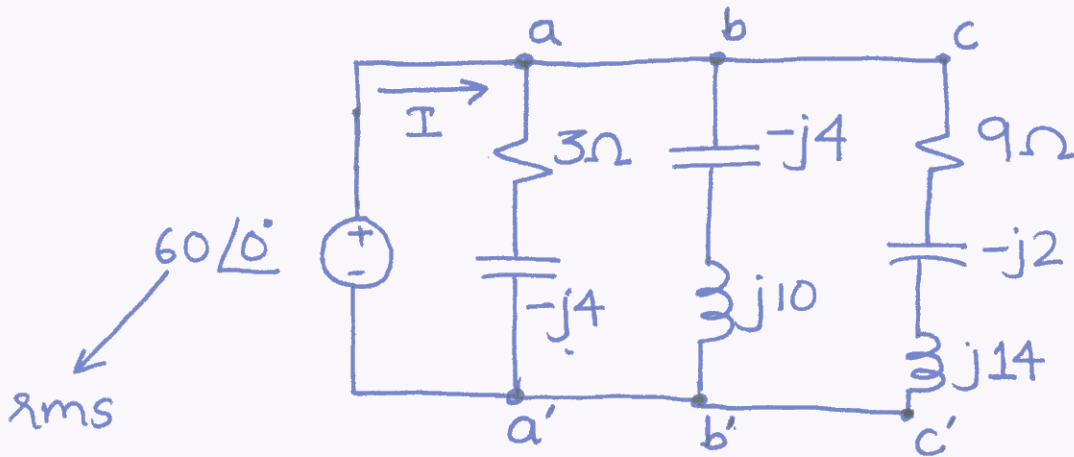- (a) Find complex power (S), average power (P), reactive power (Q) and power factor for each branch (a-a', b-b', c-c').
- (b) Find the total current 'I' and total power factor. Indicate if it is capacitive or inductive.



- Q5. A small industrial plant has a 10kW purely resistive heating load and a 20kVA inductive load of motor having a lagging power factor of 0.7. The loads are connected in parallel to a supply voltage of $1000 \angle 0^\circ$ (rms) at 60Hz.
- (a) Find the total current drawn from the supply
- (b) Determine the value of capacitor required to raise the power factor at input to 0.95.