




Problem 1:

[10 Marks]

For the diode circuit shown, the zener diode has $V_z = 3.6V$ and $r_z = 0 \Omega$. all diodes may be modeled by the constant voltage drop (CVD) model with $V_D = 0.7V$ when conducting in forward mode.

- Draw the voltage transfer characteristics (V_o versus V_i) to cover the input range $\pm 6V$. [5 Marks]
- If the input signal v_i is a triangular waveform as shown, sketch v_o versus time. [5 Marks]

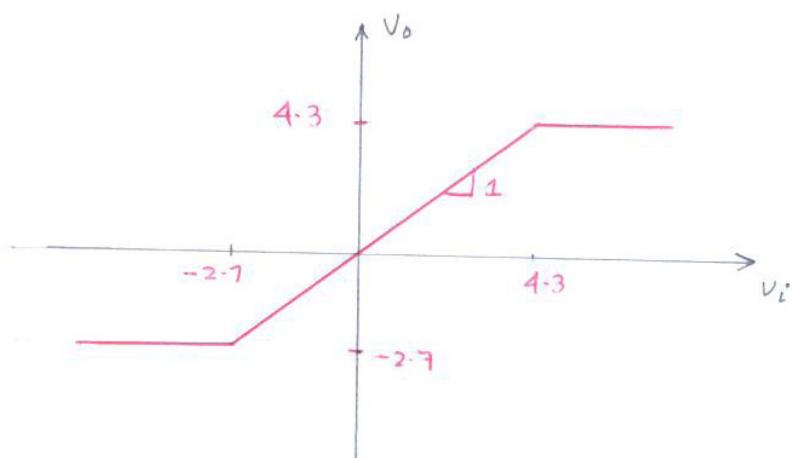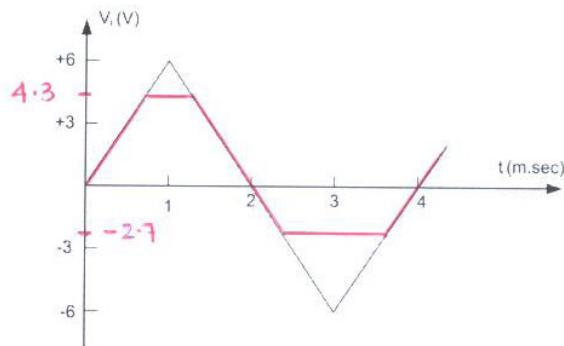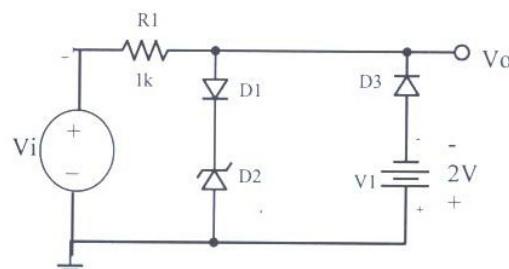Label all the critical voltage levels in your sketches.



In the positive cycle of v_i , D_3 is always OFF.

, D_2 turns ON at breakdown of $3.6V$

D_1 turn ON at $0.7V$

$$\text{so } V_o = V_{D_1} + V_{D_2} = 4.3$$

In the negative cycle of v_i , D_1 is always OFF.

, D_3 turns ON when the n-side becomes at $-2.7V$.


$$\text{so } V_o = V_{D_3} - 2 = -2.7V$$

Problem 2:

[10 Marks]

- a. For the DC power supply shown below, label the different building blocks.

[2 Marks]

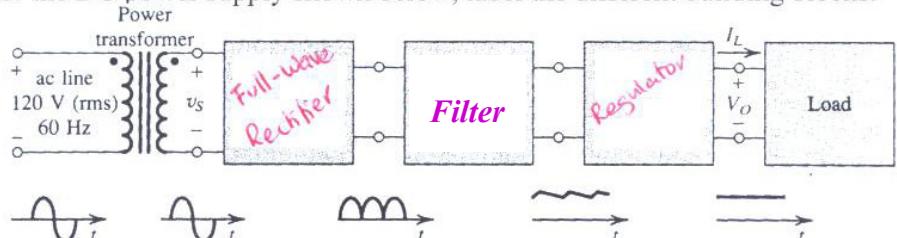

- b. It is required to design a rectifier circuit to provide an average voltage of $\approx 15.4\text{V}$ to a $1\text{k}\Omega$ load. The circuit operates from a 120V rms 60Hz household supply through a center-tapped transformer.

Available components:

[8 Marks]

- Silicon diodes that can be modeled by a constant voltage drop of 0.7V
- A center-tapped transformer with a turns ratio that can be adjusted to one of the following values: $1:5, 1:6, 1:7, 1:8$ or $1:10$

- Draw the rectifier circuit.
- Find the required turns ratios.
- What is the peak voltage and current at the load side.

(b)

$$v_{o(\text{ave})} \approx 2(V_p - V_{D0})/\pi = 15.4\text{V}$$

$$\Rightarrow V_p = 24.9\text{V}$$


$$\text{turns ratio} = \frac{120\sqrt{2}}{24.9\text{V}} = 6.7$$

$$\approx 7$$

$$\text{so } V_p = 24.2\text{V}$$

$$\begin{aligned} (c) \quad v_{o(\text{max})} &= 24.2\text{V} - 0.7 \\ &= 23.54\text{V} \end{aligned}$$

(a)

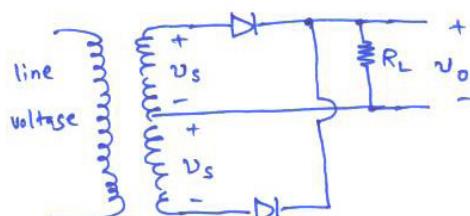

↙

$$I_{L(\text{max})} = \frac{23.54}{1\text{k}} = 23.54\text{mA}$$

↙

↙

Problem 3:

For the circuit shown below, the enhancement NMOS transistor parameters are: $V_t = 2V$, and $\mu_n C_{ox} = 200 \mu A/V^2$, $W/L = 20$.

- Design R_S so that $V_S = -2.5V$;
- Calculate drain current I_D , and voltage V_D .
- Find R_D that makes transistor at the edge of saturation mode.

From the circuit

$$V_G = 0$$

$$\text{Given } V_S = -2.5V$$


$$\text{so } V_{GS} = 2.5V$$

$$\begin{aligned} \text{Assume Saturation: } I_D &= K(V_{GS} - V_t)^2 \\ &= 2m(2.5 - 2)^2 \\ &= 0.5 \text{ mA} \end{aligned}$$

$$\Rightarrow V_D = 5 - 7K(0.5m)$$

$$= 1.5V$$
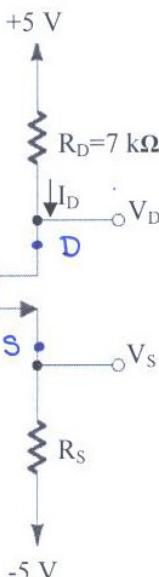
$$\begin{aligned} \text{check: } V_{DS} &= 4 > V_{GS} - V_t \\ &> 0.5 \end{aligned}$$



[10 Marks]

↙

↙

Assumption is OK

$$\text{so } R_S = \frac{-2.5 - (-5)}{0.5m} = 5k\Omega$$

$$\begin{aligned} \text{At the edge of saturation: } V_D &= V_G - V_t \\ &= -2V \end{aligned}$$

$$\Rightarrow R_D = \frac{5 - (-2)}{0.5m} = 14k\Omega$$

↙