

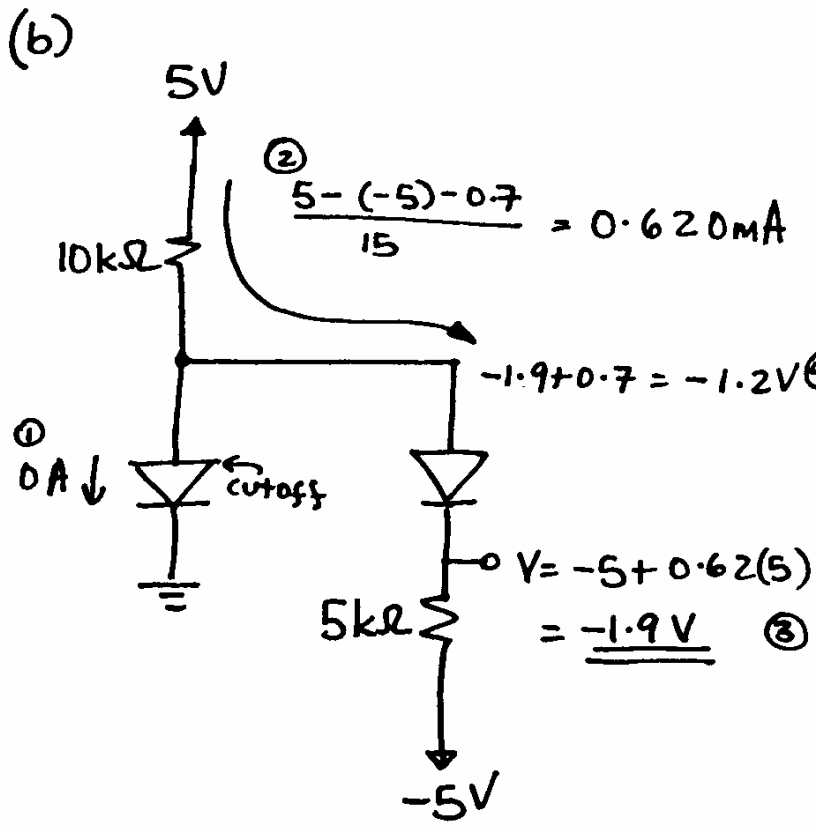


3.48

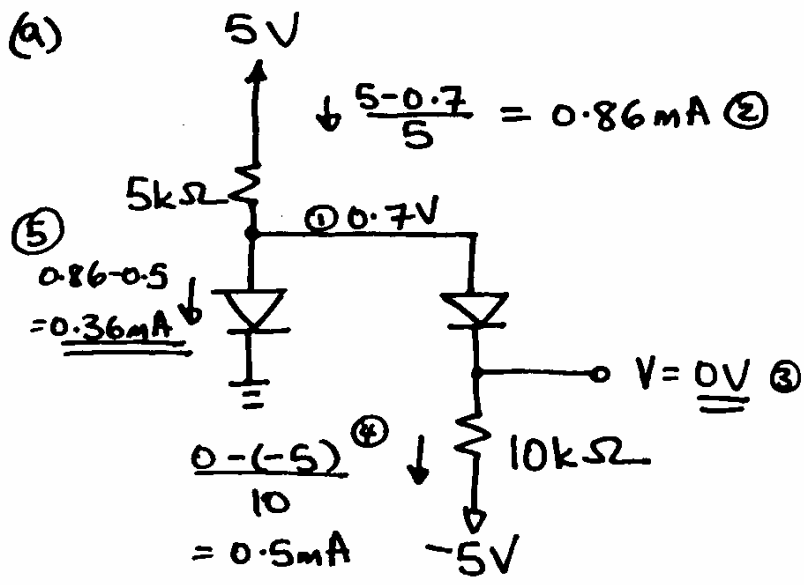

3.69

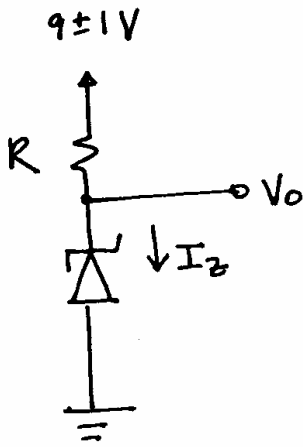

GIVEN PARAMETERS
 $V_z = 6.8V, r_z = 5\Omega,$
 $I_z = 20mA$

By knee
 $I_{zk} = 0.25mA$
 $r_z = 750\Omega$

$$\therefore R = \frac{9 - 0.68}{20} = \underline{\underline{110\Omega}}$$

FIRST DESIGN - 9V supply can easily supply current

Let $I_z = 20mA$ ~ well above knee

$$\begin{aligned} \text{Line Regulation} &= \frac{\Delta V_o}{\Delta V_s} = \frac{r_z}{r_z + R} \\ &= \frac{5}{5 + 110} \\ &= \underline{\underline{43.5 \frac{mV}{V}}} \end{aligned}$$

SECOND DESIGN ~ limited current from 9V supply

$$I_z = 0.25mA$$

$V_z = V_{zk} \approx V_{z0}$ - calculate V_{z0} from

$$V_z = V_{z0} + r_z I_{zk}$$




$$6.8 = V_{z0} + 5 \times 0.025$$

$$V_{z0} = 6.7V$$

$$\therefore R = \frac{9 - 6.7}{0.25} = \underline{\underline{9.2k\Omega}}$$

$$\begin{aligned} \text{LINE REGULATION} &= \frac{\Delta V_o}{\Delta V_s} = \frac{750}{750 + 9200} \\ &= \underline{\underline{75.4 \frac{mV}{V}}} \end{aligned}$$

3.77

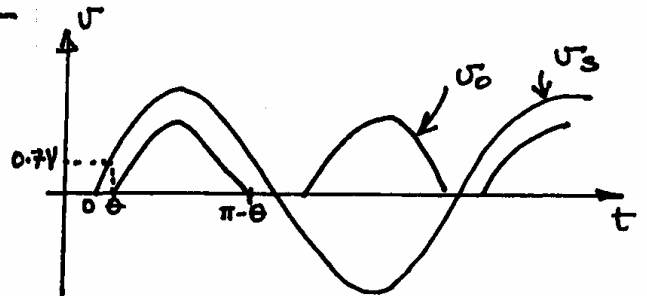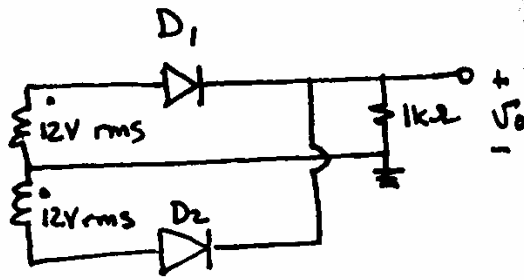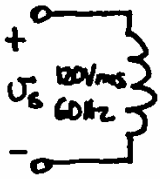

$$\hat{U}_o = 12\sqrt{2} - 0.7 = \underline{\underline{16.27V}}$$

$$\text{Conduction starts at } \theta = \sin^{-1} \frac{0.7}{12\sqrt{2}} = 0.0412 \text{ rad}$$





and ends at $\pi - \theta$. Conduction angle
 $= \pi - 2\theta = 3.06 \text{ rad}$ in each half
 cycle. Thus the fraction of a
 cycle for which one of the two
 diodes conduct $= \frac{2(3.06)}{2\pi} \times 100$
 $= \underline{\underline{97.4\%}}$

Note that during 97.4% of the cycle there will be conduction. However each of the two diodes conducts for only half the time, i.e. for 48.7% of the cycle.


$$U_{o, \text{avg}} = \frac{1}{\pi} \int_{\theta}^{\pi - \theta} 12\sqrt{2} \sin \phi - 0.7 \, d\phi$$

$$= \underline{\underline{10.12V}}$$
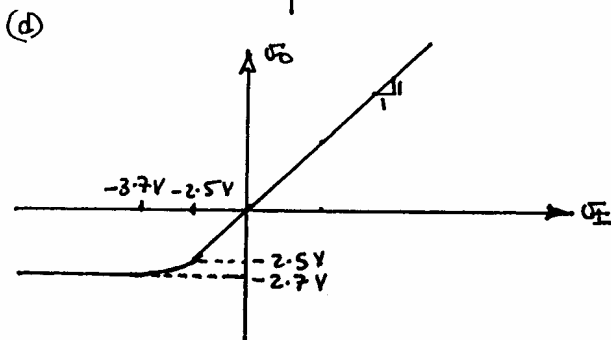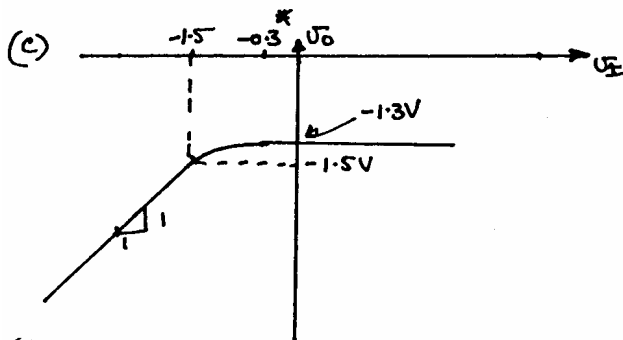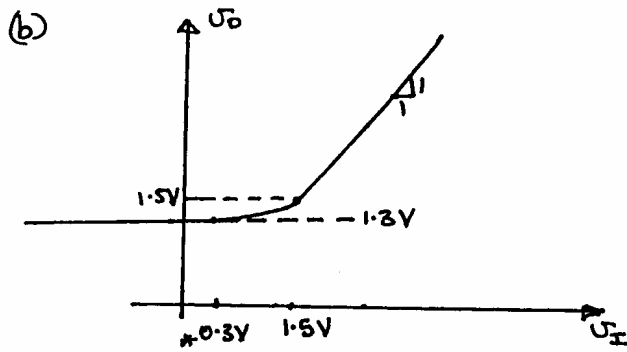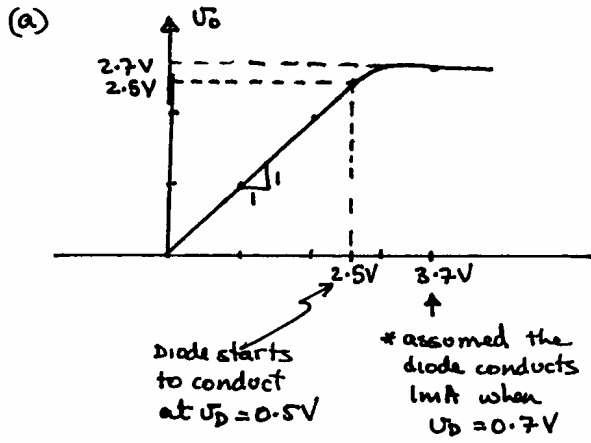
$$i_{D, \text{avg}} = \frac{10.12}{1k\Omega} = \underline{\underline{10.12 \text{ mA}}}$$




3.100

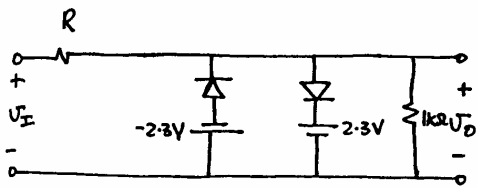

In the limiting region


$$\frac{U_O}{U_I} = \frac{1000}{1000+R} \geq 0.95$$
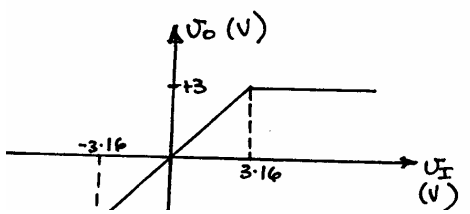
$$R \leq \underline{\underline{52.6 \Omega}}$$



$$\frac{2.2}{10 \times 10^3} = 20 \Omega \sim$$

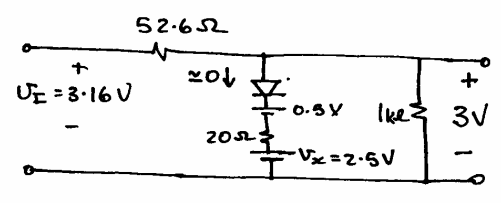At the verge of limiting in the positive direction we have :-



For $U_I = 10V$
 $U_O \approx 3 + 0.28(10 - 3.16)$
 $= \underline{\underline{4.9V}}$

For $U_I = -10V$
 $U_O = \underline{\underline{-4.9V}}$