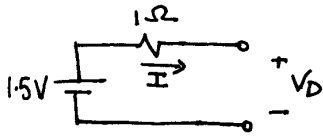


CHAPTER 3 - PROBLEMS

3.1



The diode can be reverse-biased and thus no current would flow, or forward-biased where current would flow.

(a) Reverse biased $I = 0A$ $V_D = 1.5V$

(b) Forward biased $I = 1.5A$ $V_D = 0V$

3.2

(a) Diode is conducting and thus has a 0V drop across it. Consequently

$$V = \underline{-3V}$$

$$I = \frac{3 - (-3)}{10k\Omega} = \underline{0.6mA}$$

(b) Diode is cut off.

$$V = \underline{3V} \quad I = \underline{0A}$$

(c) Diode is conducting



$$V = \underline{3V}$$

$$I = \frac{3 - (-3)}{10k\Omega} = \underline{0.6mA}$$


(d) Diode is cut off.

$$V = \underline{-3V} \quad I = \underline{0A}$$

3.3

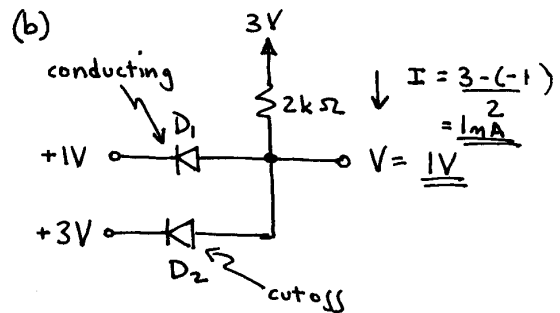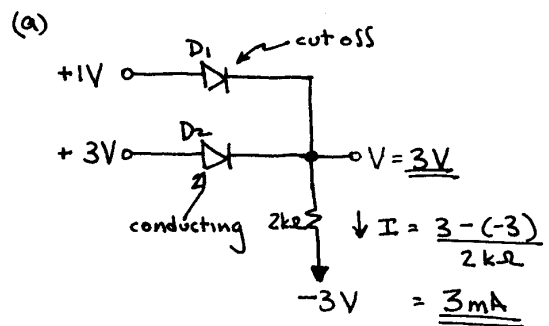


3.4

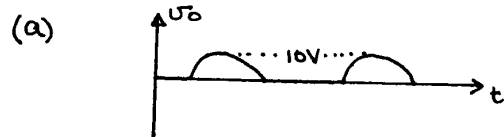

$$V_{pr} = \underline{10V} \quad V_{p-} = \underline{0V}$$

$$f = \underline{1kHz}$$

CHAPTER 3 PROBLEMS

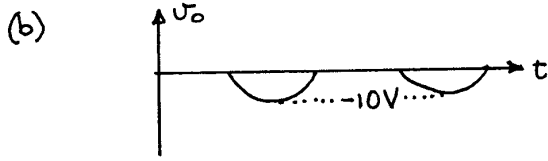


$$V_{p+} = \underline{0V} \quad V_{p-} = \underline{-10V}$$

$$f = 1\text{kHz}$$




$$V_o = \underline{0V}$$

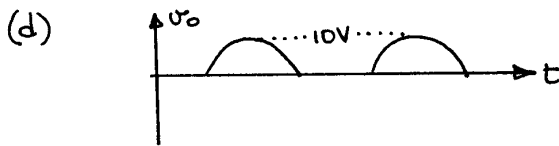Neither D_1 nor D_2 conducts so there is no output.




$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{0V} \quad f = 1\text{kHz}$$

Both D_1 and D_2 conduct when $V_i > 0$

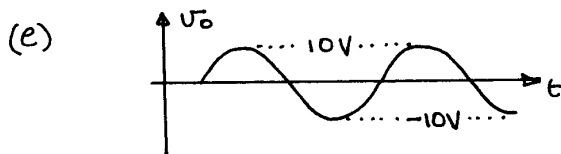


$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{-10V} \quad f = 1\text{kHz}$$

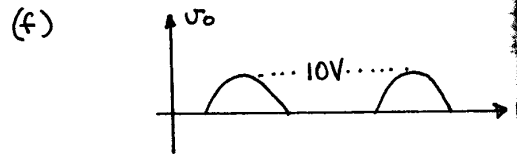D_1 conducts when $V_i > 0$ and D_2 conducts when $V_i < 0$. Thus the output follows the input.




$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{0V} \quad f = 1\text{kHz}$$

D_1 is cutoff when $V_i < 0$

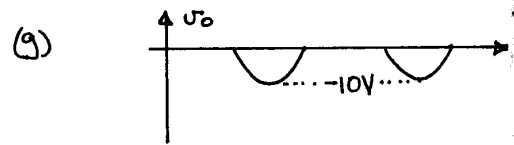


$$V_{p+} = \underline{0V} \quad V_{p-} = \underline{-10V} \quad f = 1\text{kHz}$$

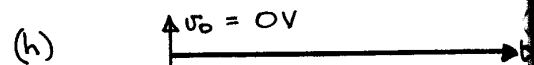D_1 shorts to ground when $V_i > 0$ and is cut off when $V_i < 0$ when the output follows V_i .




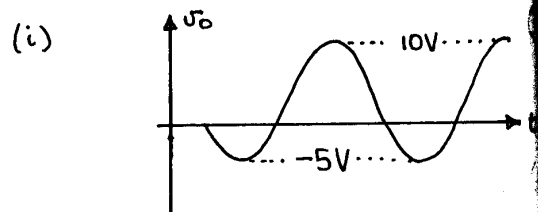
$V_o = \underline{0V}$ ~ The output is always shorted to ground as D_1 conducts when $V_i > 0$ and D_2 conducts when $V_i < 0$.




$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{-5V} \quad f = 1\text{kHz}$$

-When $V_i > 0$, D_1 is cutoff and V_o follows V_i .

3.9

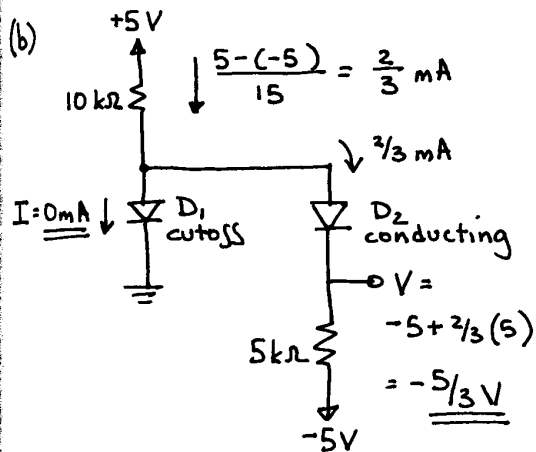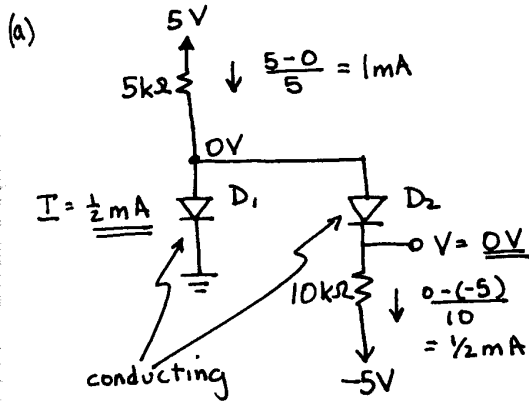


3.10

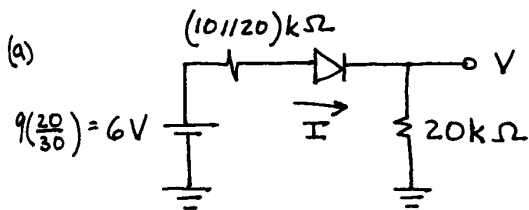

$$I = \frac{6}{(10||20) + 20} = \underline{\underline{0.225mA}}$$

$$V = \frac{20}{(10||20) + 20} \times 6 = \underline{\underline{4.5V}}$$

(b)

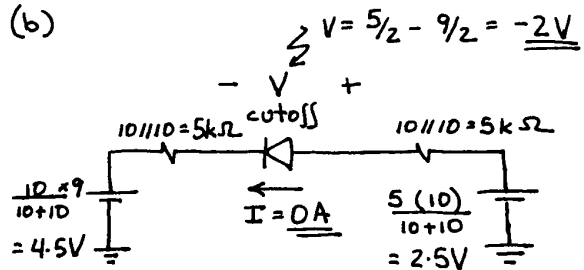


3.11

$$R \gg \frac{120\sqrt{2}}{50} \gg \underline{\underline{3.4k\Omega}}$$

The largest reverse voltage appearing across the diode is equal to the peak input voltage

$$120\sqrt{2} = \underline{\underline{169.7V}}$$

3.12

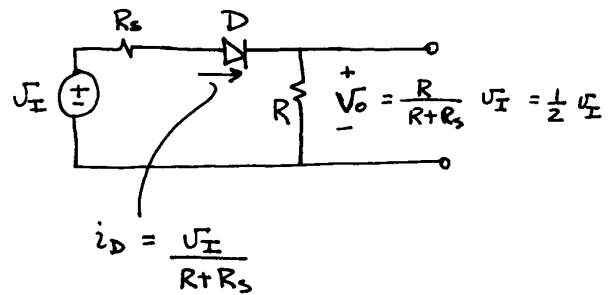

D starts to conduct when $V_I > 0$

