

# Key

Quiz # 4

Name:

ID#

- a) Find  $R$  in the current source shown below to have  $I_{REF} = 20\mu A$ , where  $(W/L)_1 = 10$ .  
 b) Design the  $(W/L)$  ratios so that have  $I_2 = 100\mu A$ ,  $I_3 = I_4 = 20\mu A$ , and  $I_5 = 40\mu A$   
 (PMOS transistors have  $k_p = 80\mu A/V^2$ ,  $V_{tp} = -0.6V$ )

a)

$R = ??$

$$I_{REF} = \frac{V_{GS1} + 1.5}{R} \Rightarrow R = \frac{V_{GS1} + 1.5}{I_{REF}}$$


From Sat. Equ.

$$I_{REF} = \frac{1}{2} k_p' \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{tp})^2$$

$$20\mu = \frac{1}{2} \cdot 80\mu \cdot 10 \cdot (V_{GS1} + 0.6)^2$$

$$V_{GS1} = -0.825V$$
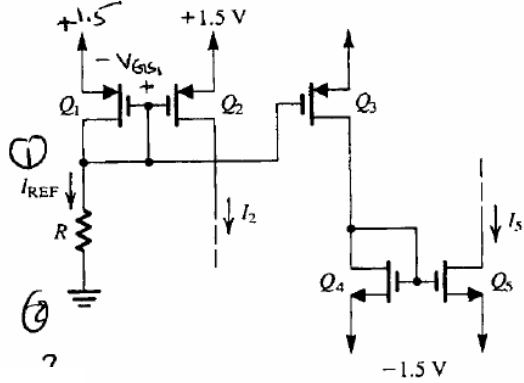
$$R = \frac{-0.825 + 1.5}{20\mu} = 33750\Omega$$



b) 
$$I_2 = \frac{(W/L)_2}{(W/L)_1} I_{REF} \Rightarrow \left(\frac{W}{L}\right)_2 = \frac{I_2}{I_{REF}} \left(\frac{W}{L}\right)_1$$

$$\left(\frac{W}{L}\right)_2 = \frac{100\mu}{20\mu} (10) = \underline{\underline{50}}$$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_1 = \underline{\underline{10}}$$

$$\left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_4 \quad \frac{I_5}{I_4} = \underline{\underline{20}}$$