

Name:

Key

ID #

Q1)

[35 points]

For the amplifier circuit shown, neglect  $r_o$ .

- (a) Drive an expression for the **midband voltage gain** ( $V_{out}/V_{sig}$ ). 9  
 (b) Drive an expression for the **low and high frequency poles**. 16  
 (c) Find the amplifier transfer function  $T(s) = V_{out}(s)/V_{sig}(s)$ . 4

Given that  $g_m = 0.5 \text{ mA/V}$ ,  $C_{C1} = C_{C2} = 1 \mu\text{F}$ ,  $C_{gs} = 1 \text{ pF}$  and  $C_{gd} = 0.5 \text{ pF}$ 

Find the values of :

- $\omega_L$  and  $\omega_H$  and the bandwidth BW. 4
- Voltage gain =  $(V_{out}/V_{sig})$  2

$$a) AM = \frac{R_E \parallel \frac{1}{g_m}}{(R_E \parallel \frac{1}{g_m}) + R_{sig}} \cdot \frac{R_L \parallel R_C}{\frac{1}{g_m}} = g_m (R_L \parallel R_C) \frac{R_E \parallel \frac{1}{g_m}}{(R_E \parallel \frac{1}{g_m}) + R_{sig}} \cdot 20 \text{ k}\Omega = 0.5 \times 10 \text{ k} \cdot \frac{1}{2} = 2.5 \text{ V}_V$$

b) Low freq. poles :

$$\omega_{C1} = \frac{1}{(R_{sig} + R_E \parallel \frac{1}{g_m}) C_g}$$

$$\omega_{C2} = \frac{1}{C_{C2} (R_C + R_L)}$$


$$\text{High freq. poles : } \omega_{Cgs} = \frac{1}{C_{gs} (R_{sig} \parallel R_E \parallel \frac{1}{g_m})}$$

$$\omega_{Cgd} = \frac{1}{C_{gd} (R_C \parallel R_L)}$$

$$\underline{T(s)} = AM \frac{s}{s + \omega_H} \cdot \frac{1}{1 + \frac{s}{\omega_L}}$$

$$\text{where } \omega_H = \frac{1}{C_{gs} + C_{gd}} \quad ; \quad \omega_L \approx \omega_{Ceq} = 500 \text{ rad/sec}$$
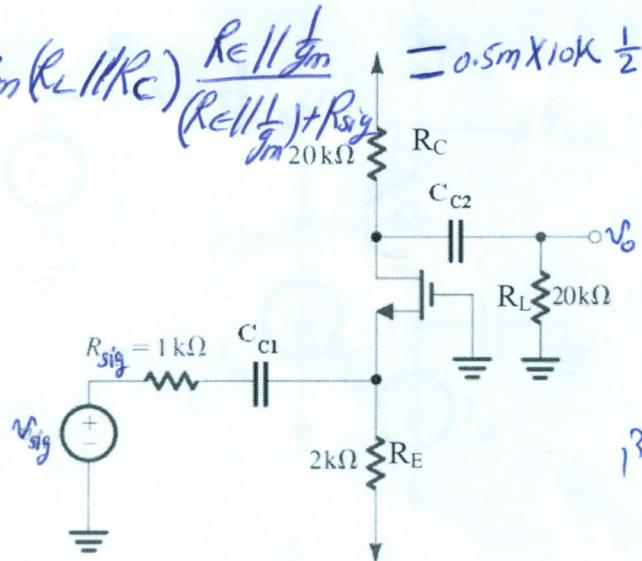
$$= \frac{1}{5 \times 10^{-10} + 5 \times 10^{-9}} = 1.818 \times 10^8 \text{ rad/sec} \Rightarrow BW = \omega_H - \omega_L \approx \omega_H$$



Q2)

[35 points]



For the amplifier circuit shown below,

(d) Drive an expression for the **midband voltage gain**  $A_M = V_{out}/V_{sig}$ . 10(e) Drive an expression for the **low corner frequency**  $\omega_L$ . 5(f) Drive an expression for the upper corner frequency  $\omega_H$ . 20

$$d) A_M = \frac{r_{\pi_2} || R_o}{R_s || r_{\pi_2} + \frac{1}{g_m}} \left[ -g_m r_o (R_c || R_o) \right]$$

$$e) \omega_L = \frac{1}{C \left( r_e + \frac{g_m || R_o}{B+1} \right)}$$

$$f) \omega_H = ??$$

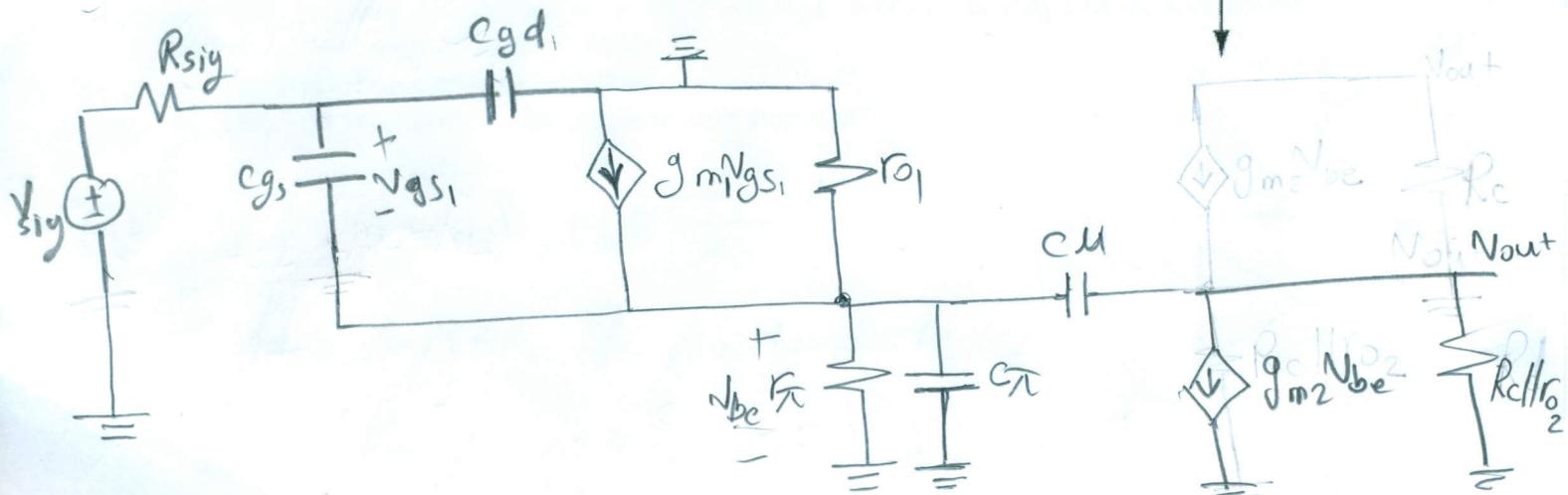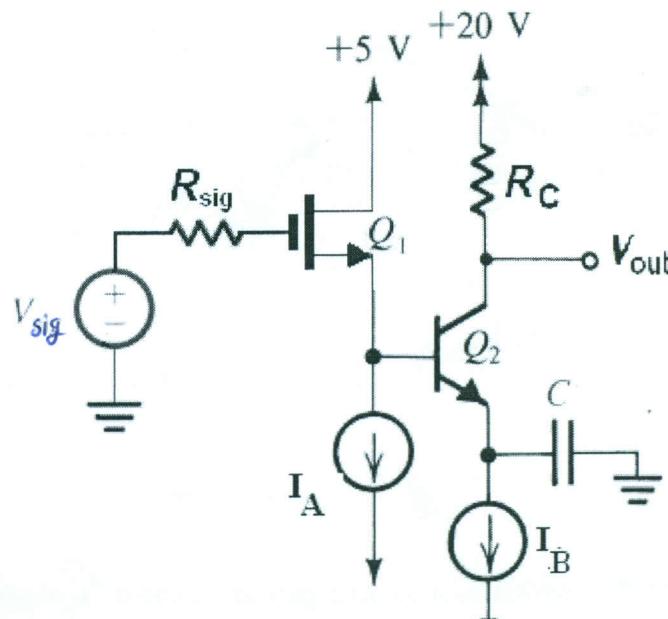

$$\omega_{c_{gd}} = \frac{1}{C_{gd} R_{sig}}$$

$$\omega_{c_{eq}} = \frac{1}{C_{\pi} + C_{\mu} \left( 1 + g_m R_c || R_o \right) \left( R_c || R_o \right)}$$

$$\omega_{c_{gs}} = \frac{R_{sig} + R_o || R_{\pi}}{1 + g_m (R_o || R_{\pi})}$$

$$\omega_H = \frac{1}{C_{gd} + C_{cgs} + C_{ceq} + C_{c2}}$$


$$\omega_{c_2} = \frac{1}{C_{\mu} \left( 1 + \frac{1}{g_m R_c || R_o} \right) (R_c || R_o)}$$

Q3)

[30 points]

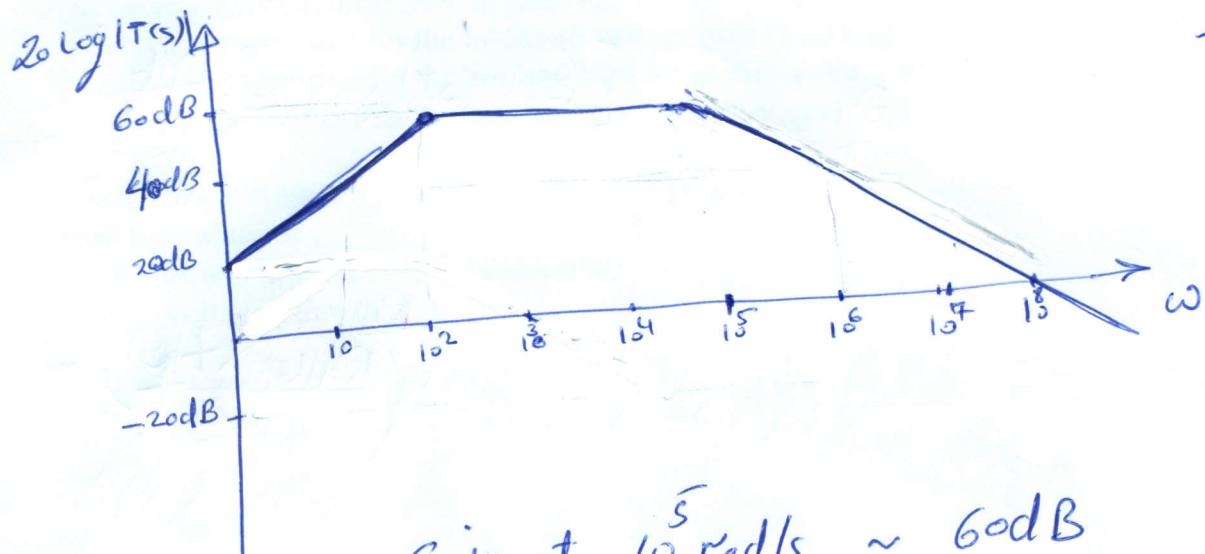- a) Sketch Bode plots for the **magnitude** of the transfer function and estimate the gain in dB at  $10^5$  rad/s

$$T(s) = \frac{10s}{(1+s/10^2)(1+s/10^5)}$$



- b) Non-inverting amplifier with gain of 30v/v employs an opamp having a dc gain of 100dB and unity-gain frequency of 10MHz, **find**:


- The 3-dB frequency of the opamp.
- The 3-dB frequency of the non-inverting amplifier

15

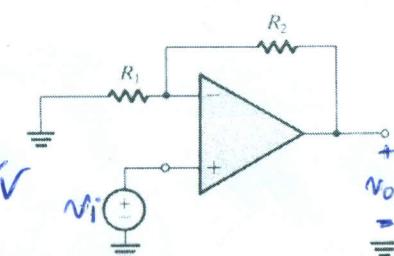(i) For opamp  $\omega_b = \frac{\omega_T}{A_0}$

$\omega_T = 10\text{ MHz}$  &  $A_0 = 100\text{dB} = 10^5 \text{ V/V}$

$$\omega_b = \frac{\omega_T}{A_0} = \frac{10\text{ MHz}}{10^5} = 100\text{ Hz}$$



(ii) for the closed loop sys.

$$f_{b_{CL}} = \frac{\omega_T}{A_{CL}} = \frac{10\text{ MHz}}{30} = 333.33\text{ kHz}$$