

Name: _____

ID # _____

Question #1: (5)

For the circuit shown below find the lower and upper corner frequencies f_L , f_H and midband gain. BJT parameters are: $\beta=100$, $C_\pi=20\text{pF}$, $C_\mu=4\text{pF}$ (ignore r_o and r_x), and $I_C=1\text{mA}$, $V_T=25\text{mV}$.


Lower Corner Frequency:

$$f_L = \frac{1}{2\pi R_{C_c} C_c}$$

$$R_{C_c} = R_s + [R_1 || R_2 || (\beta+1)(R_E + r_e)]$$

$$r_e = \frac{V_T}{I_C} = 25 \Omega$$
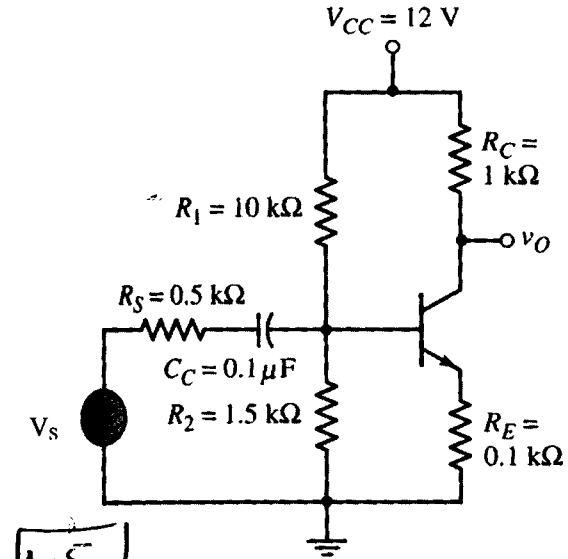
$$f_L = \frac{1}{2\pi \times 1682 \times 0.1 \times 10^{-6}} = 946 \text{ Hz}$$




1.5

Upper Corner Frequency:

$$f_{H1} = \frac{1}{2\pi R_{\pi_1} C_{\pi_1}}$$

$$R_x = R_s || R_1 || R_2 = 361 \Omega$$

$$R_{\pi_1} = r_\pi || \frac{R_x + R_E}{1 + \beta} = 89 \Omega ; f_{H1} = 89.4 \text{ MHz}$$

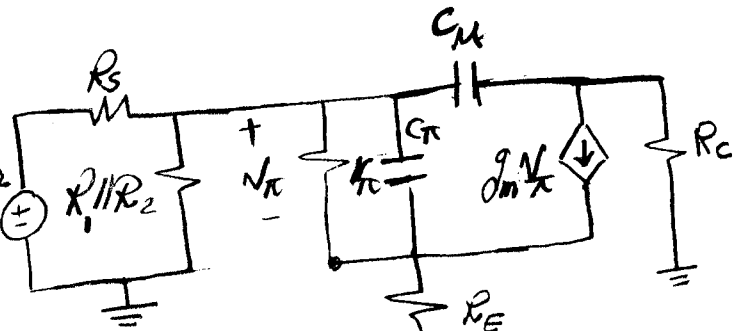


2

$$f_{H2} = \frac{1}{2\pi R_{C_1} C_1} ; R_{C_1} = R_s || R_1 || R_2 || [(\beta+1)(r_e + R_E)]$$

$$f_{H2} = 14 \text{ MHz}$$
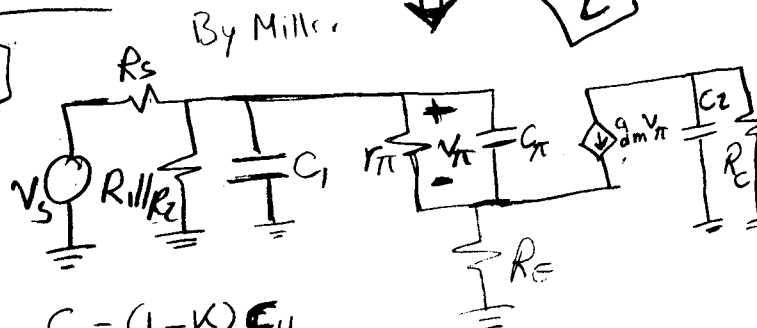
$$f_{H3} = \frac{1}{2\pi R_{C_2} C_2} = \frac{1}{2\pi R_C C_2} = 39.8 \text{ MHz}$$



$$C_1 = (1 - \kappa) C_\mu = \left(1 + \frac{g_m R_C}{1 + \beta \frac{R_E + r_e}{R_1}}\right) C_\mu = 9 C_\mu$$

$$C_2 = \left(1 - \frac{1}{\kappa}\right) C_\mu \approx C_\mu$$

$$f_H \approx 14 \text{ MHz}$$

$$R_i = R_1 || R_2 || (\beta+1)(R_E + r_e) = 1182 \Omega$$

$$\text{Midband Gain} = \frac{R_i}{R_i + R_s} \left(\frac{R_C}{R_E + r_e} \right) = -5.6$$

1.5

Question #2: (4)

For the circuit shown below, design the audio amplifier circuit such that the lower corner frequency f_L is 20Hz and midband gain. MOSFET $g_m = 1 \text{ mA/V}$ (ignore r_o).

find

$$f_{L1} = \frac{1}{2\pi R_{CE} C_E} \quad ; \quad R_{CE} = R_S \parallel \frac{1}{g_m} = 833 \Omega$$

$$f_{L1} = \frac{1}{2\pi \times 833 \times C_E} \quad \boxed{1}$$

$$f_{L2} = \frac{1}{2\pi R_C C_C} \quad ; \quad R_C = R_D + R_L = 16.7 \text{ k}\Omega$$


$$f_{L2} = \frac{1}{2\pi \times 4011 \times C_C} \quad \boxed{1}$$

Different approaches can be used here to design f_L . One way:

$$f_L = f_{L1} + f_{L2} = 16 + 4 \quad \Rightarrow \quad C_E = \frac{1}{2\pi \times 833 \times 16} = \underline{\underline{11.9 \mu\text{F}}}$$

$$C_C = \frac{1}{2\pi \times 4011 \times 4} = \underline{\underline{9.91 \mu\text{F}}}$$
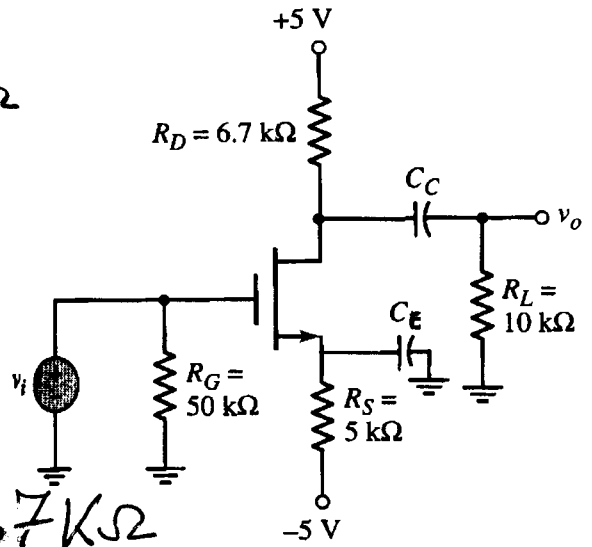
$$\text{Midband Gain} = -g_m (R_D \parallel R_L) = -4.01 \text{ V/V} \quad \boxed{1.5}$$





Question # 3: (6)



For the Cascode circuit shown below find the upper corner frequency f_H and midband gain. MOSFETs are identical and have the following parameters are: $g_{m1} = g_{m2} = 1 \text{ mA/V}$, $C_{gs} = 5 \text{ pF}$, $C_{gd} = 1 \text{ pF}$ (ignore r_o).

$$\begin{aligned} \text{Midband Gain} &= \frac{V_o}{V_i} = \frac{V_{gs1}}{V_i} \cdot \frac{V_{gs2}}{V_{gs1}} \cdot \frac{V_o}{V_{gs2}} \\ &= \frac{R_2 \parallel R_3}{R_i + R_2 \parallel R_3} \cdot \frac{g_{m1}}{g_{m2}} \cdot [-g_{m2}(R_D \parallel R_L)] \\ &= 0.97 (1) (-2.3) \approx -2.24 \text{ V/V} \end{aligned}$$

1.5

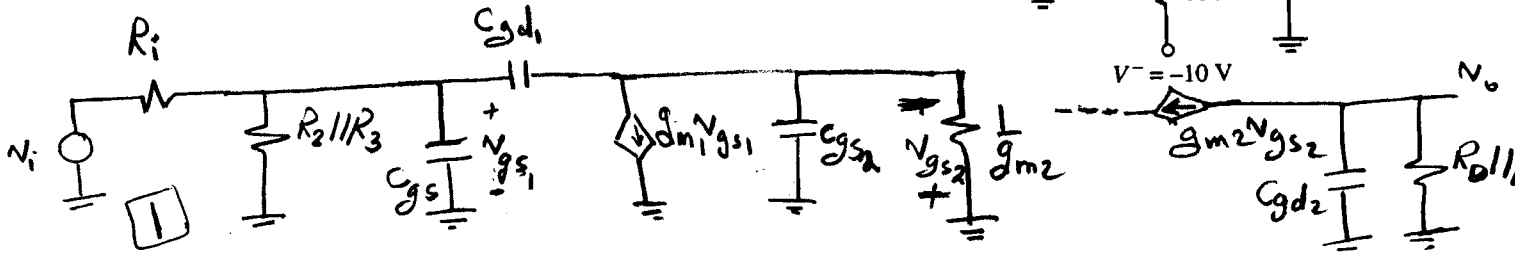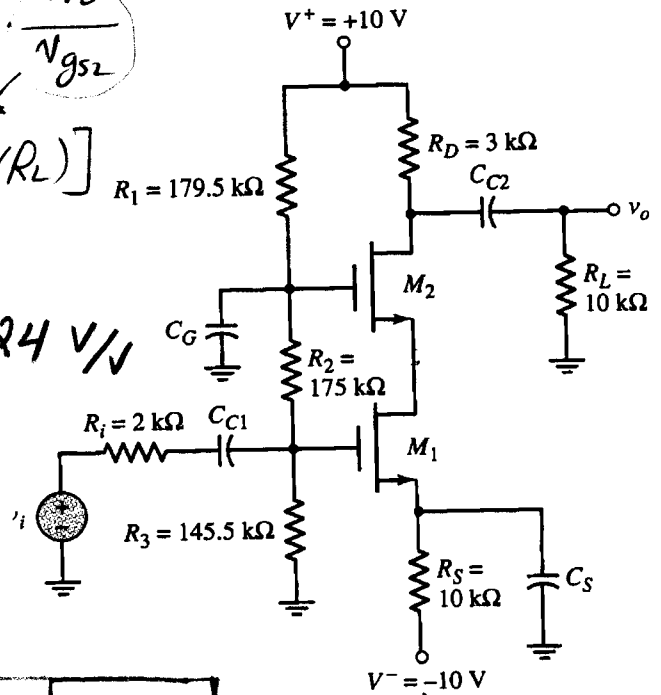

By Miller ↓

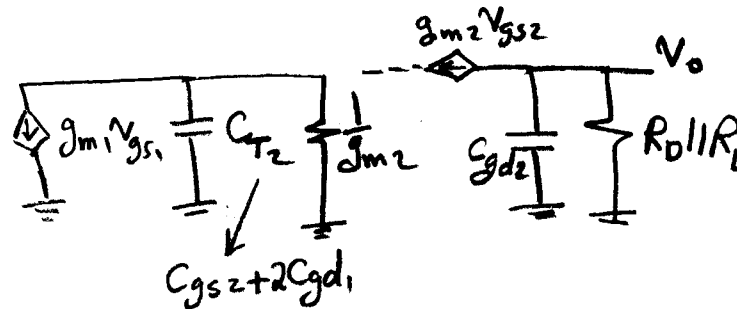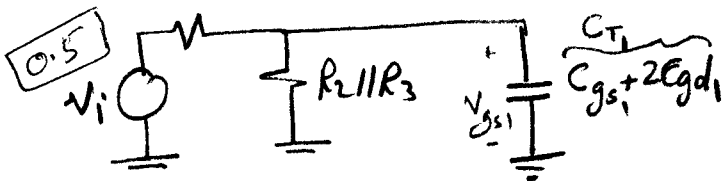

$$\omega_{H1} = \frac{1}{R_i C_{T1}} = \frac{1}{(R_i \parallel R_2 \parallel R_3)(C_{gs1} + 2C_{gd1})} = 73.226 \text{ M rad/s} \Rightarrow f_{H1} = 11.65 \text{ MHz}$$

$$\omega_{H2} = \frac{1}{R_{CT2} C_{T2}} = \frac{1}{\frac{1}{g_{m2}}(C_{gs2} + 2C_{gd1})} = 142.857 \text{ M rad/s} \Rightarrow f_{H2} = 22.73 \text{ MHz}$$

$$\omega_{H3} = \frac{1}{(R_D \parallel R_L) C_{gd2}} = 433.3 \text{ M rad/s} \Rightarrow f_{H3} = 68.9 \text{ MHz}$$

$$\omega_H \approx \frac{1}{\tau_1 + 2\tau_2 + 2\tau_3} \Rightarrow f_H \approx 6.928 \text{ MHz}$$