

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
FIRST SEMESTER 2012-2013 (S121)

Course Title:	Electronics II
Course Number:	EE 303

Exam Type:	Exam II
Date:	Thursday November 27, 2014
Time:	5:30PM-7:00PM

Student Name:

Key

Student ID:

GRADING		
Question 1	25	25
Question 2	20	20
Question 3	30	30
Question 4	25	25
Total:	100	100

Show all your work and results. Do not give more than one answer otherwise the wrong one will be considered.


Question No.1: (25 points)

For the amplifier circuit shown below, ignore r_o


- (a) Drive an expression for the **midband voltage gain** $A_M = V_o/V_i$.
 (b) Find all high frequency poles.

a) $\frac{V_o}{V_i} = \frac{R_{S1}}{R_{S1} + \frac{1}{g_m 1}} (-g_{m2} R_D)$

10

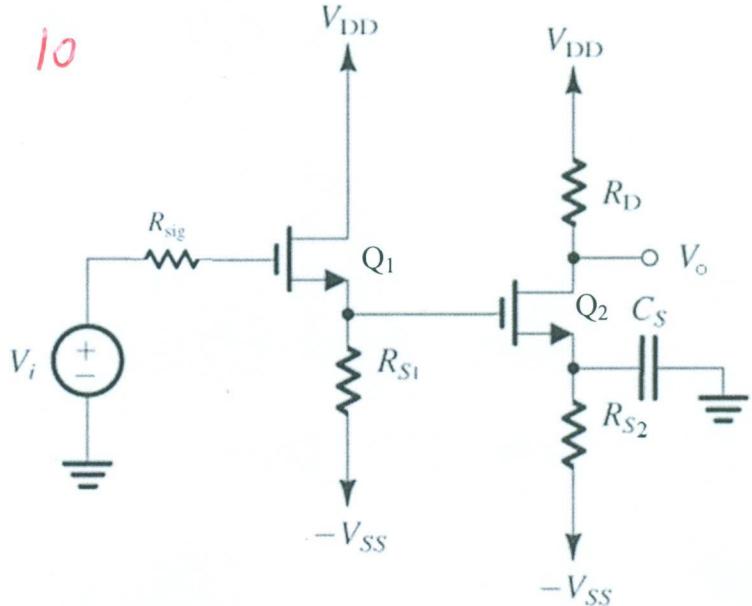

b) High freq. poles:

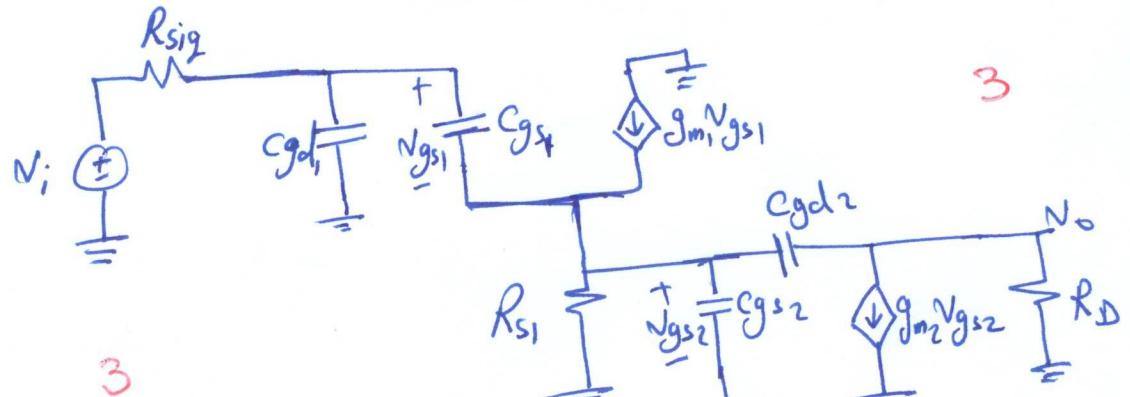

$$\omega_{H1} = \frac{1}{g_{ds1} R_{sig}}$$

3

$$\omega_{H2} = \frac{1}{C_{gs1} R_{gs1}} ; R_{gs1} = \frac{R_{sig} + R_{S1}}{1 + g_{m1} R_{S1}}$$

3

$$\omega_{H3} = \frac{1}{(C_{gs2} + C_1)(R_{S1} || \frac{1}{g_{m1}})} ; C_1 = C_{gd2}(1 + g_{m2} R_D)$$

$$\omega_{H4} = \frac{1}{C_2 R_D} ; C_2 = C_{gd2} \left(1 + \frac{1}{g_{m2} R_D}\right)$$


Question No.2: (20 points)

- i. Determine the type of the feedback configuration for an amplifier circuit to achieve the following objectives: [10 points]

- a) Low Input Resistance R_{in} and Low Output Resistance R_{out} *Shunt-Shunt* 5
b) Low Input Resistance R_{in} and High Output Resistance R_{out} *Shunt-Series* 5

- ii. Determine the type of the feedback configuration in the amplifier circuit shown below in the following cases: [10 points]

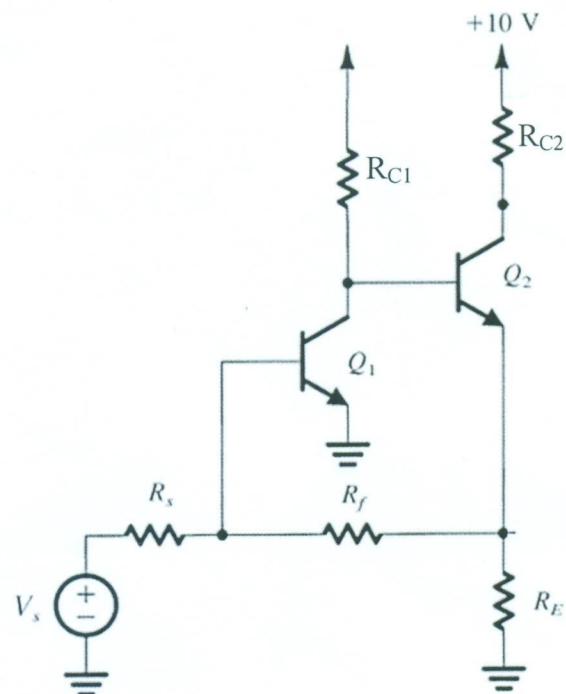- a) Feed back network B consists of resistor R_f : *shunt-shunt* 5
b) Feed back network B consists of resistor R_f and R_E : *shunt-series* 5



Question No.3: (30 points)


The following figure shows an amplifier circuit, ignore r_o

1. Determine: type of the feedback configuration, R_{11} , and R_{22} [6 points]
2. Sketch A circuit [6 points]
3. Drive expression for the open loop gain A. [8 points]
4. Drive expression for feedback factor B. [5 points]
5. Determine the closed loop gain (v_o/i_s) [5 points]


① Shunt-shunt 4

$$R_{11} = R_F \quad | \quad \textcircled{1}$$

$$R_{22} = R_F \quad | \quad \textcircled{2}$$

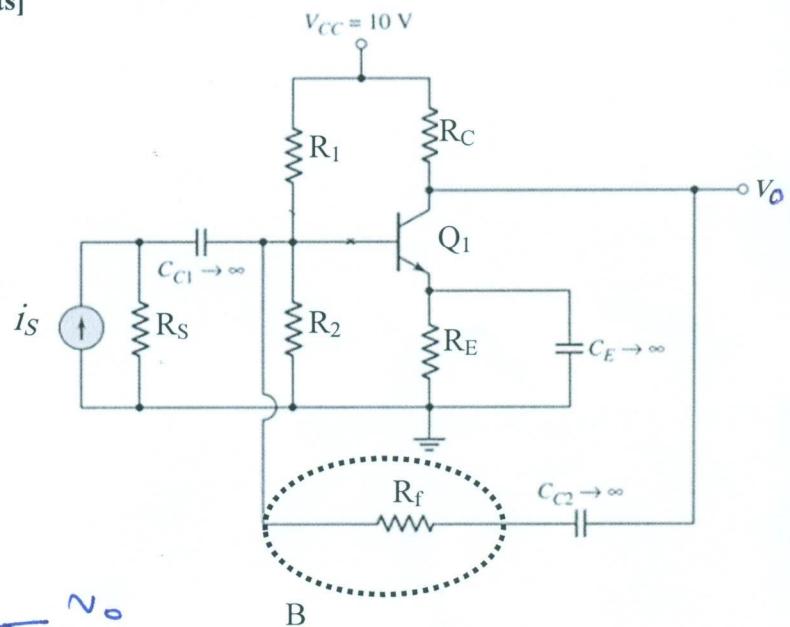


2) A: 6

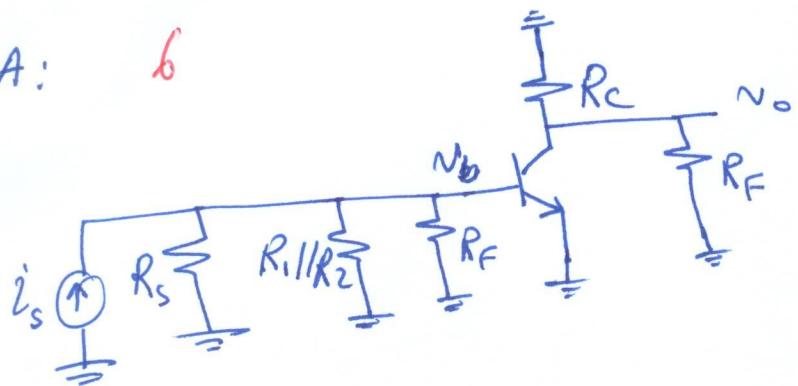

$$3) A = \frac{N_o}{i_s} = \frac{N_b}{i_s} \frac{N_o}{N_b} = (R_S || R_1 || R_2 || R_f || r_{e1}) \left(-\frac{R_F || R_C}{r_{e1}} \right) \quad 8$$

4) B:

$$B = \frac{i_1}{N_2} = -\frac{1}{R_F}$$

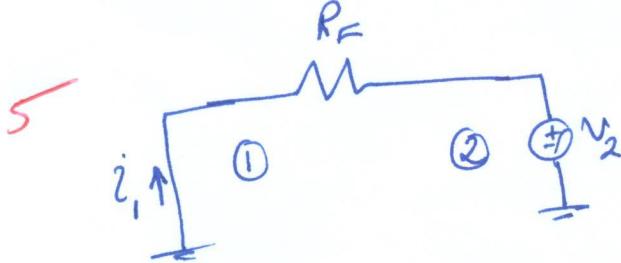

$$5) \text{ closed loop gain: } A_f = \frac{N_o}{i_s} = \frac{A}{1+AB}$$

Question No. 4: (25 points)

- i. Write a general transfer function $T(s)$ for a first order Low pass filter. [5 Points]

$$T(s) = \frac{a_0}{s + \omega_0} \quad 5$$

- ii. For the shown active filter circuit:

- a) Derive an expression for the transfer function $v_o(s)/v_i(s)$. [8 Points]
- b) What is the filter type? [4 Points]
- c) Find an expression for the pole frequency ω_0 . [4 Points]
- d) Find the dc and high frequency gains. [4 Points]

a) Node at (-):

$$\frac{N_1 - N_i}{R_1} + \frac{N_1 - N_o}{R_1} = 0 \quad ① \quad 2$$

$$N_1 = \frac{1}{2} N_i + \frac{1}{2} N_o \quad *$$

Node at (+)

$$\frac{N_1 - N_i}{R} + N_i SC = 0 \quad ② \quad 2$$

$$N_i [1 + SCR] - N_i = 0 \Rightarrow (\frac{1}{2} N_i + \frac{1}{2} N_o)(1 + SCR) - N_i = 0 \quad 2$$

$$N_i (-\frac{1}{2} + \frac{1}{2} SCR) + N_o (\frac{1}{2} + \frac{1}{2} SCR) = 0$$

$$\frac{N_o}{N_i} = \frac{1 - SCR}{1 + SCR} = - \frac{s - \frac{1}{CR}}{s + \frac{1}{CR}} \quad 2$$

b) All Pass first order filter - OpAmp RC 4

$$c) \omega_0 = \frac{1}{CR} \quad 4$$

$$d) DC Gain = +1, \text{ high freq gain} = -1 \quad 4$$

