

Key


Quiz # 3

Name:

ID#

The following figure shows a feedback amplifier, (ignore r_o for all transistors)

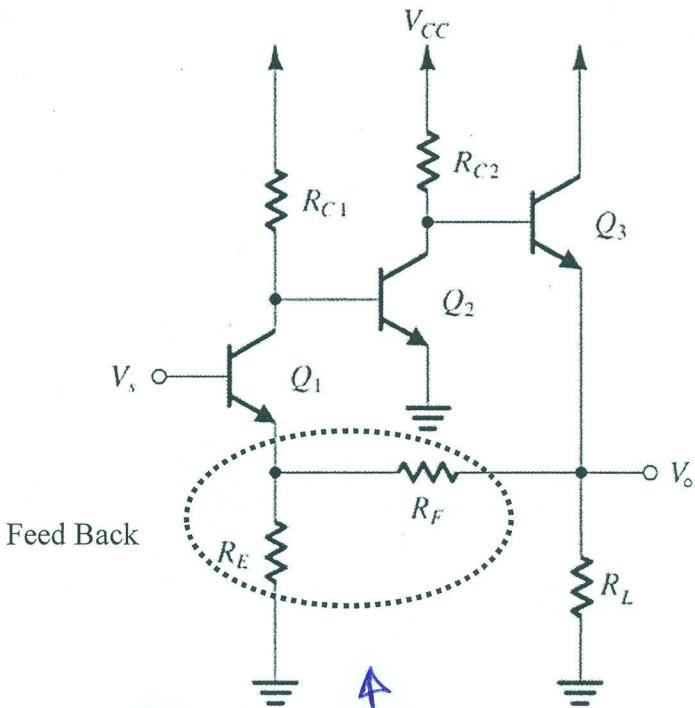
- a) Sketch A circuit. 4
- b) Find R_{11} and R_{22} 3
- c) Find A 3



$$\text{b) } R_{11} = R_E \parallel R_F$$

$$R_{22} = R_E + R_F$$

$$\text{a) } \underline{\underline{A}}$$

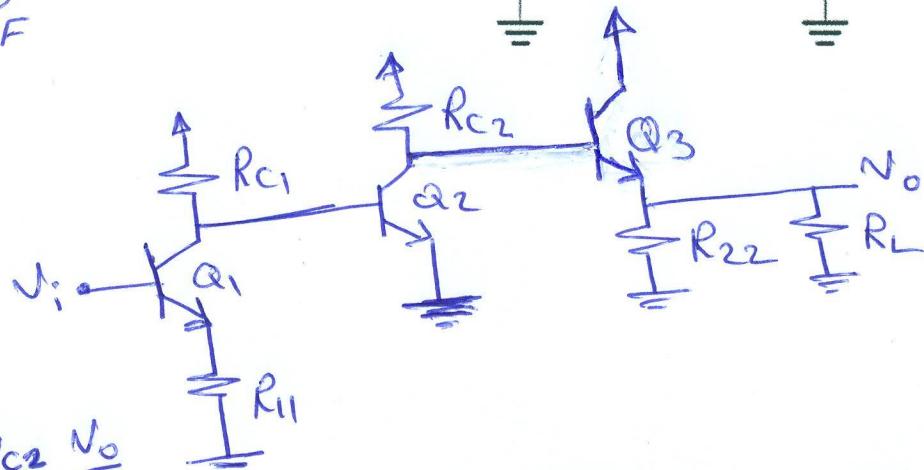

$$\text{c) } A = \frac{V_o}{V_i} = \frac{N_{C1}}{N_i} \frac{N_{C2}}{N_{C1}} \frac{N_o}{N_{C2}} \frac{R_{22}}{R_{L}}$$

$$A = \frac{V_o}{V_i} = \left(-\alpha_1 \frac{R_{C1} \parallel R_{C2}}{N_{E1} + R_{11}} \right) \frac{R_{C2} \parallel (\beta + 1)(N_{E3} + R_2 \parallel R_L)}{r_{e2}}$$